

Baluns & Common Mode Chokes

Bill Leonard N0CU

5 August 2017

Topics – Part 1

- A Radio Frequency Interference (RFI) Problem
- Some Basic Terms & Theory
- Baluns & Chokes
 - What is a Balun
 - Types of Baluns
 - Balun Applications
 - Design & Performance Issues
 - Voltage Balun
 - Current Balun
 - What is a Common Mode Choke
 - How a Balun/Choke works

Topics – Part 2

- Tripole
- Risk of Installing a Balun
- How to Reduce Common Mode currents
- How to Build Current Baluns & Chokes
 - Transmission Line Transformers (TLT)
 - Examples of Current Chokes
 - Ferrite & Powdered Iron (Iron Powder) Suppliers

Part 1

RFI Problem

- Problem:
 - Audio started coming thru speakers of audio amp:
 - When transmitting > 50W SSB
 - 20M & 40m (I didn't check any other bands)
 - No other electronics affected
 - Never had this problem before
 - Problem would come and go for no apparent reason

RFI Problem – cont'd

- Observations

- Intermittent: problem was freq dependent
- RF Power level dependent
- Rotating the 20 M beam appeared to have no effect
- No RFI with dummy load
- AC line filter had no effect
- Common Mode Choke on transmission line to house had no effect
- Caps (180 pF) on speaker terminals on audio amp made problem worse
 - **Caution:** don't use large caps (ie., 0.01 uF) with solid state amps => damage
- Disconnecting 4 of 5 speakers from the audio amp eliminated problem
 - The two speakers with the longest cables were picking up RF
 - Both of these speakers needed to be connected to the amp to have the problem
 - Length of cable to each speaker ~30 ft (~1/4 wavelength on 40M)
 - None of the other three speakers contributed to the problem

RFI Problem – cont'd

- Conclusions:
 - RF is getting into the audio amp via two speaker cables
 - The SSB modulation is being rectified and amplified in the audio amp
 - This is well documented as a common cause of RFI
 - Problem does not appear to be RF on AC power line
- Solution:
 - Two snap on ferrites on each of the two speakers leads solved problem
 - Properties of the ferrite unknown

RFI Problem – cont'd

- Remaining Questions:
 - What has changed (20+ years with no RFI problems)
 - What caused the frequency dependence
 - Why were two speakers needed to cause the problem
 - Is Common Mode Current still a possible problem
 - Transmission line
 - AC power line
 - Is my solution a true fix or only a band-aid

Questions to be Addressed

- When should a balun/choke be used
- What type of balun/choke should be used
 - How to build a balun/choke
- Where should they be installed
- What should be observed after one is installed

Questions to be Addressed



- When should a balun/choke be used
- What type of balun/choke should be used
 - How to build a balun/choke
- Where should they be installed
- What should be observed after one is installed

The answers to all of these questions are application dependent!

Some Basic Terms & Theory

Signal Line Types


- Unbalanced Line:
 - Single wire working against ground or a shield
 - Wire may, or may not, be shielded
 - Coax is a shielded unbalanced line
 - If unshielded, the wire **will radiate**
- Balanced Line:
 - Two collocated lines working against each other
 - Signal wires usually not shielded
 - Twin lead & ladder line are balanced lines
 - Ground is not part of the signal path
 - **No radiation** if signals on the line are also balanced
- Most antennas are neither perfectly balanced, nor perfectly unbalanced

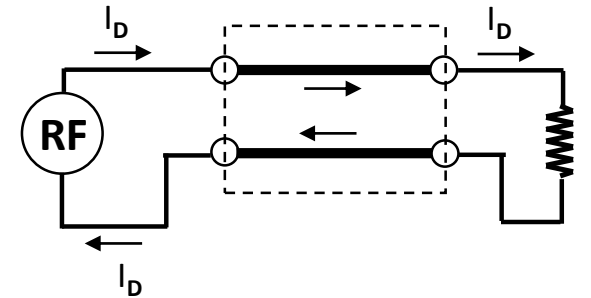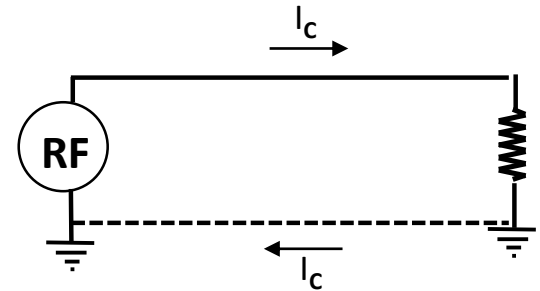


Balanced Signal

- Balanced signals have **both**:
 - Equal amplitude currents that are 180° out of phase
 - Equal amplitude voltages that are 180° out of phase
- Balanced RF signals on a balanced line => **~no radiation**
 - No radiation is unachievable
 - Requires perfect cancellation (theoretically impossible to achieve)
 - Wire line spacing < 1/10 wavelength is usually adequate for ham applications

Example: two wire transmission line

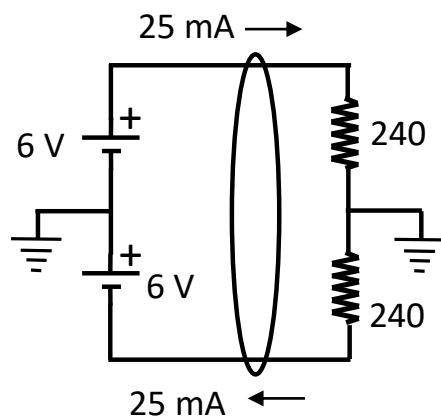

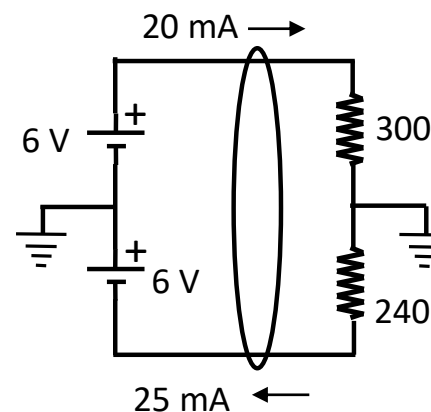Balanced Line
Balanced sources
Balanced loads
Balanced currents
No Common Mode Current




Balanced Line
Balanced sources
UNbalanced loads
UNbalanced currents
5 mA Common Mode Current

Signal Transmission Modes

- Two types of signal transmission modes


- **Differential (Transmission Line) Mode:**

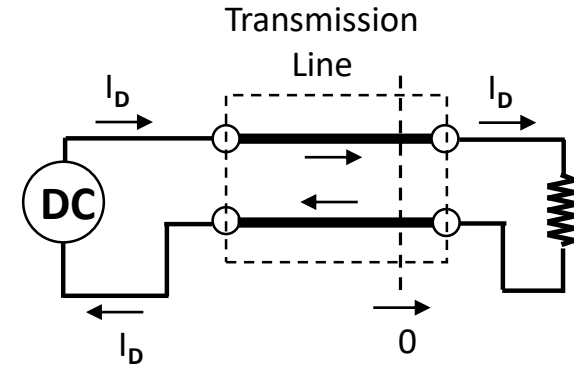- Signals are balanced
- Net line current = **Common Mode Current = 0**
- Radiation won't occur



- **Common Mode:**

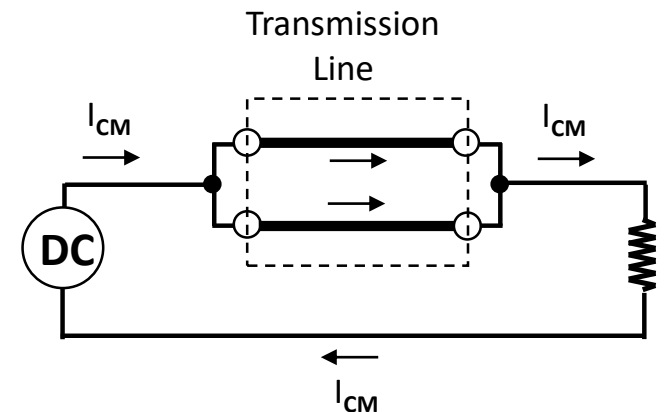- Signals are unbalanced
- Net line current = **Common Mode Current = I_{CM}**
- Radiation will occur




Common Mode Current

- Can cause significant operational problems
- Not always an issue that requires mitigation
 - If no Common Mode Current, installing a Balun/Choke will have no effect
- What can cause Common Mode Currents:
 1. Imbalanced line currents
 - Asymmetry in the antenna
 - Off center fed dipole
 - Sloping dipole
 - Dipole with elements going in different directions
 - Feedline not perpendicular to the antenna
 - Objects in the near field of the antenna
 - ***A Balun/Choke won't help with some of these problems***
 2. Ground loops
 3. Balanced to Unbalanced mismatch (Tripole)

Common Mode Current Example

- Coaxial transmission line:

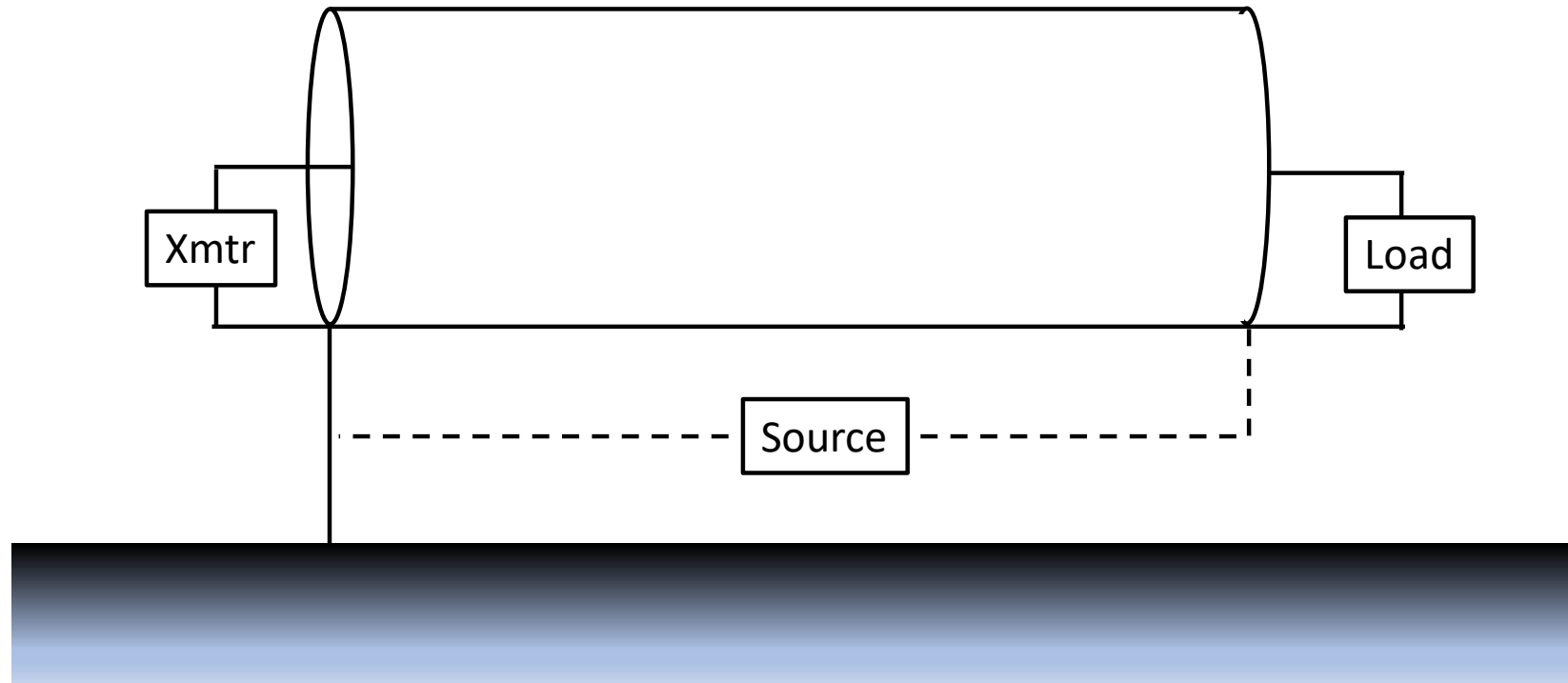


Source can be either noise or an RF signal

Problems Common Mode Currents Can Cause


- Distortion in antenna pattern and polarization
 - Reduce peak gain
 - Interference from unwanted signals
 - Increase noise
- Antenna SWR problems
 - Increase SWR
 - Shift the frequency of minimum SWR (resonance)
 - False readings on wattmeters and SWR bridges
 - Make SWR dependent on the length of coax
- RFI
 - Burning fingers/lips
 - Interference with consumer electronics (spouse + neighbors)
 - Trip transceiver and/or amplifier protection circuits
 - Distortion on audio (mics, speakers, etc)

Measured Performance

Without Balun

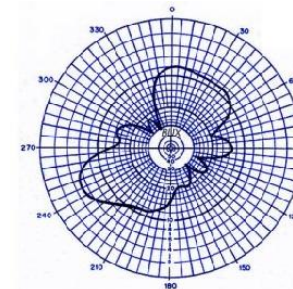

With Balun

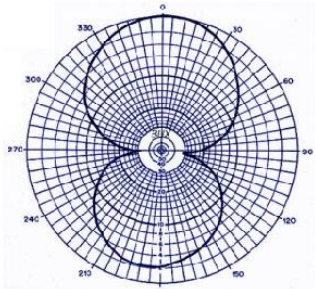

Half wave dipole

QST April 1980

Some ARRL Antenna Books are misleading

Baluns & Chokes

(Overview)

What is a Balun

- Bidirectional signal conversion device
 - Converts a **BAL**anced signal to an **UN**balanced signal, and vice versa
 - Outputs either equal **CURRENT** or equal **VOLTAGE** from each balanced port
 - Even with varying load impedances
 - A Balun may, or may not, reduce Common Mode Currents
- A Balun can be designed to do impedance transformations
 - The descriptor **n:1** defines impedance ratio
 - Common ratios: 1:1, 2:1, 4:1, 6:1, 9:1, 12:1
 - Note: 1:n is not the same as an n:1 (ie, 50:200 vs 50:12.5)
- 3 port power divider defined by:
 - $S_{12} = S_{21} = -S_{13} = -S_{31}$
 - $S_{11} = \text{Infinity}$
 - S_{23} & S_{32} (port to port balance): no constraint

Types of Baluns

- **Voltage Balun**
 - *Not the best choice* for most ham applications
- **Current Balun**
- **Current Choke**
 - A Current Balun that is designed to reduce Common Mode currents
 - AKA: Choke Balun, Common Mode Choke, Line Isolator, Feedline Current Isolator
 - Good Current Balun ⇔ Good Common Mode Choke
- **Unun**
 - "UNbalanced to UNbalanced" signal conversion device
 - Used with ground mounted verticals and to break up ground loops
- **Babal** (my name)
 - "Balanced to Balanced" signal conversion device => ???
 - ARRL Antenna book gives an example of this type of device

Balun Applications

- Signal conversion
- Impedance transformation (up or down)
- **Isolation of circuits (ie, reduce Common Mode Currents)**
 - Reduce/eliminate RFI
 - Improve antenna patterns and match
 - Eliminate ground loops
 - Both audio and RF
- Delay line with Common Mode Current rejection
- Phase inverter with Common Mode Current rejection

Unless stated otherwise, comments apply to Current Baluns/Chokes

Typical Balun Performance Specs

- Frequency Coverage*
 - System Impedance*
 - Impedance Transformation Ratio*
 - Maximum Power*¹
-
- Return Loss (SWR)*
 - Insertion Loss*
 - Common Mode Rejection Ratio (CMRR)
 - Choke “Impedance” is better spec for ham applications*
 - Both R & X are important
 - Phase Balance
 - Amplitude Balance
 - Balanced Port Isolation
 - DC/Ground Isolation
 - Group Delay Flatness

Usually
Spec'd



Frequently
Not
Spec'd

*Can be important in ham applications

1) Two problems with max power specs

- Duty cycle is not spec'd
- The important power limit:
 - Not spec'd
 - Can be much lower than spec'd limit

Design And Performance Issues

- Too many “Experts” who either don’t discuss, or don’t agree on:
 - Important performance requirements
 - Which Balun/Choke designs should be used?
 - Important “System” issues
 - Will adding a Balun/Choke help or hurt?
 - Will the Balun/Choke overheat?
- Most manufacturers:
 - Don’t provide specs for some critical parameters
 - Example: one popular manufacture’s specs:
 - Balun: 1:1 ratio, 1.8-30 MHz, 50 ohms, 2 KW/5 KW
 - Common Mode power limit is the most important, but is never spec’d
 - Not sure how it could be spec’d, or how meaningful it would be if it was published
 - **It is possible for a 100 watt transmitter to destroy a 2 KW Balun!**
 - Don’t offer much/any info on “System” issues

Design And Performance Issues

- Too many “Experts” who either don’t discuss, or don’t agree on:
 - Important performance requirements
 - Which Balun/Choke designs should be used?
 - Important “System” issues

How a Balun/Choke performs, and whether it will survive, is application dependent!

- Don’t provide specs for some critical parameters
 - Example: one popular manufacture’s specs:
 - Balun: 1:1 ratio, 1.8-30 MHz, 50 ohms, 2 KW/5 KW
 - Common Mode power limit is the most important, but is never spec’d
 - Not sure how it could be spec’d, or how meaningful it would be if it was published
 - **It is possible for a 100 watt transmitter to destroy a 2 KW Balun!**
- Don’t offer much/any info on “System” issues

Important System Issues

- “System” includes:
 - Load (antenna, etc)
 - Baluns & Chokes
 - Transmission line
 - Antenna tuners
 - ***Station RF ground (both impedance and location are important)***
- What is the risk of a Balun/Choke failing due to overheating
- Balun/Choke performance vs. load impedance
 - Manufacturer’s specs assume a 50 ohm resistive load
 - Some baluns/chokes are very sensitive to reactance

Voltage Balun


Voltage Balun

- Produces equal & opposite voltages at output ports
 - Used with voltage fed antennas (end fed half wave, long wire, etc)
- Currents are whatever is needed to generate equal output voltages
- **Requires magnetic coupling for Differential Mode signals**
 - Ferrite and powder iron materials commonly used
 - Core can be toroid, rod, binocular style
- Hams started using the voltage Balun in the mid '60s
 - **Not the best choice for most Ham applications**
 - Equal currents (not voltages) are usually required in Ham applications
 - More likely to fail due to heating of magnetics
 - Affected more by load impedance variations
 - Most commercial antenna tuners use a 4:1 voltage balun

Examples: Voltage Baluns & Ununs


1:1 Balun

50 ohm
UNBALANCED

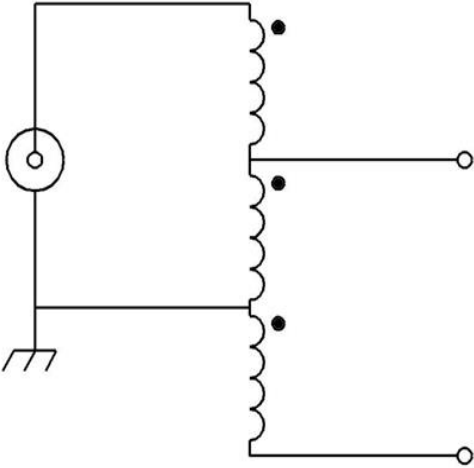


50 ohm
BALANCED

Balun/Unun

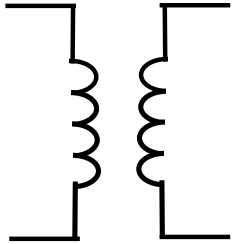

4:1 Balun


50 ohm
UNBALANCED

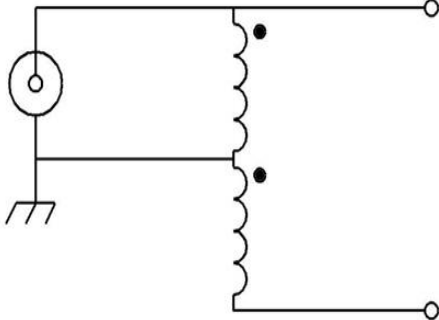

200 ohm
BALANCED



End Fed Halfwave Antenna

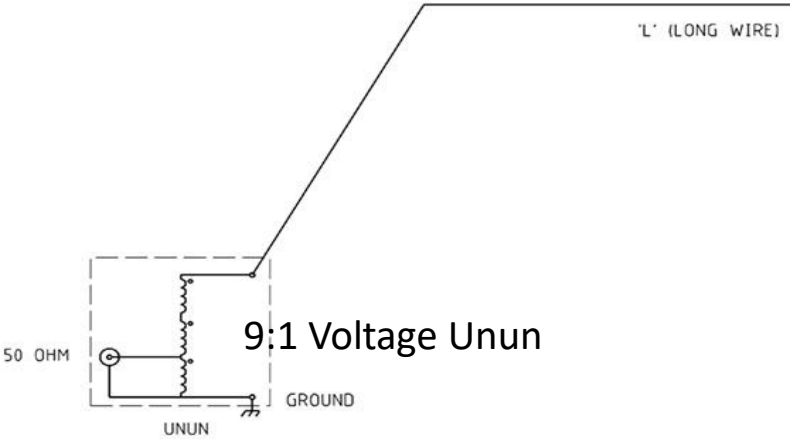



Current Balun

Current Balun


- Produces equal & opposite currents at output ports
- Voltages are whatever is needed to generate equal output currents
- A 1:1 Current Balun is also a Common Mode Choke
 - Exhibits high impedance to common mode signals
 - Little/no degradation of differential signals
- Magnetic coupling not required for Differential Mode signals => less loss/heating
- Best choice for most ham applications
 - Equal currents are required in most ham applications
 - Provides:
 - Better input to output isolation
 - Better power handling capability
 - Better output balance
 - Better tolerance to load variations
 - Lower loss

Examples: Current Baluns

1:1 Balun/Common Mode Choke

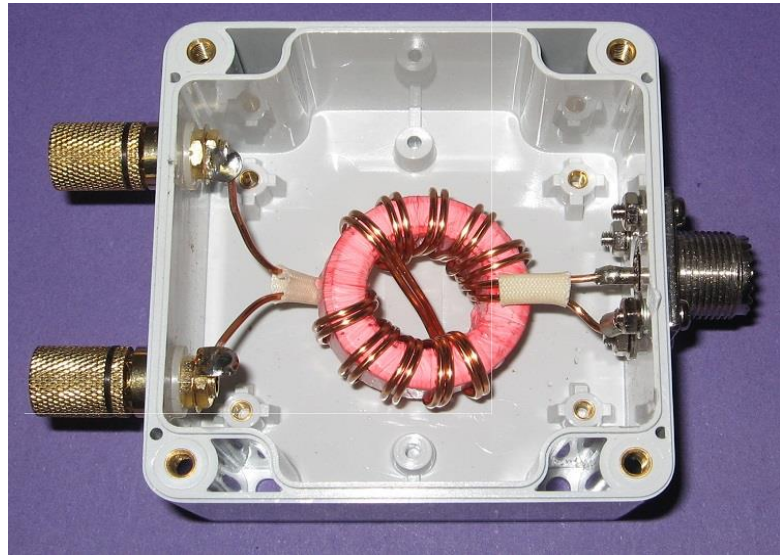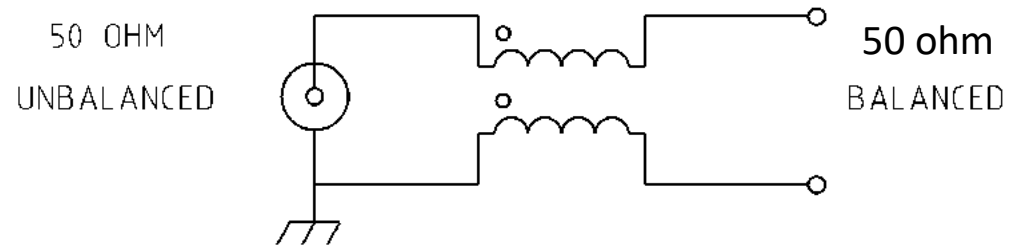

4:1 Balun

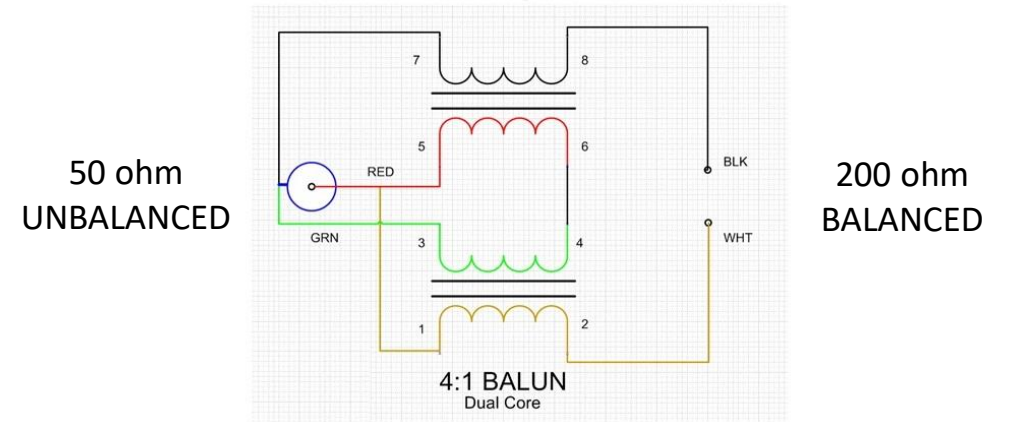


Common Mode Choke

What Is A Common Mode Choke

- Signal conversion/isolation device designed to provide:
 - Maximum Common Mode Current rejection
 - Minimum Differential (Transmission Line) Mode loss
- Can be built using:
 - Powder iron core coupling :
 - Low permeability: low loss, low inductance/turn, high Q, narrow bandwidth
 - Ferrite core coupling:
 - High permeability: high loss, high inductance/turn, low Q, wide bandwidth
 - Air coupling
 - Permeability = 1: low loss, low inductance/turn, very high Q, very narrow bandwidth
 - No coupling (coaxial half wave balun)
 - Low loss, very high Q, very narrow bandwidth


How A Common Mode Choke Works

Differential Mode Chokes

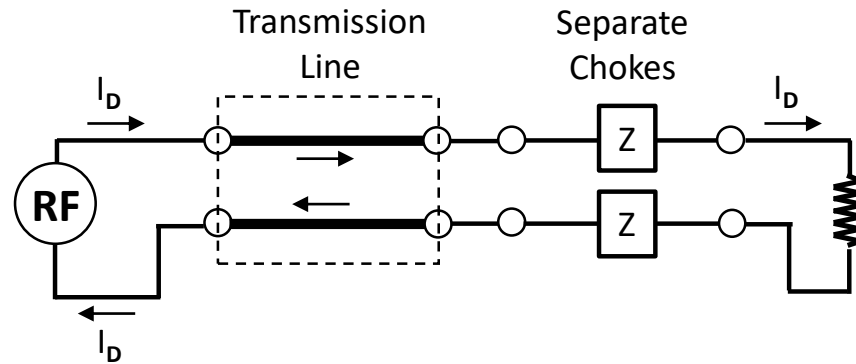


Individual Chokes yield High Z_{CM} **and** High Z_D

Common Mode Choke

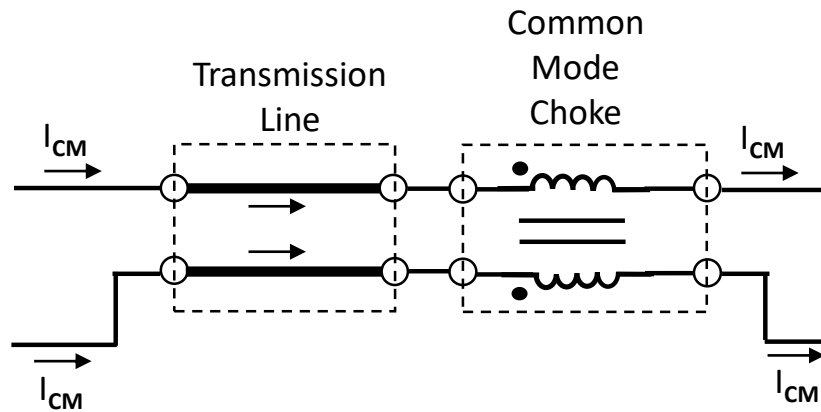


Toroidal Chokes to reduce:

Common Mode

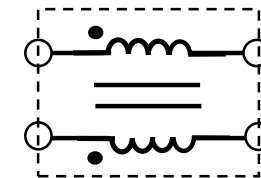


Differential Mode

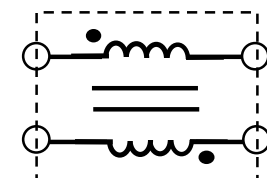

How A Balun/Common Mode Choke Works – cont'd


Common-Mode Chokes

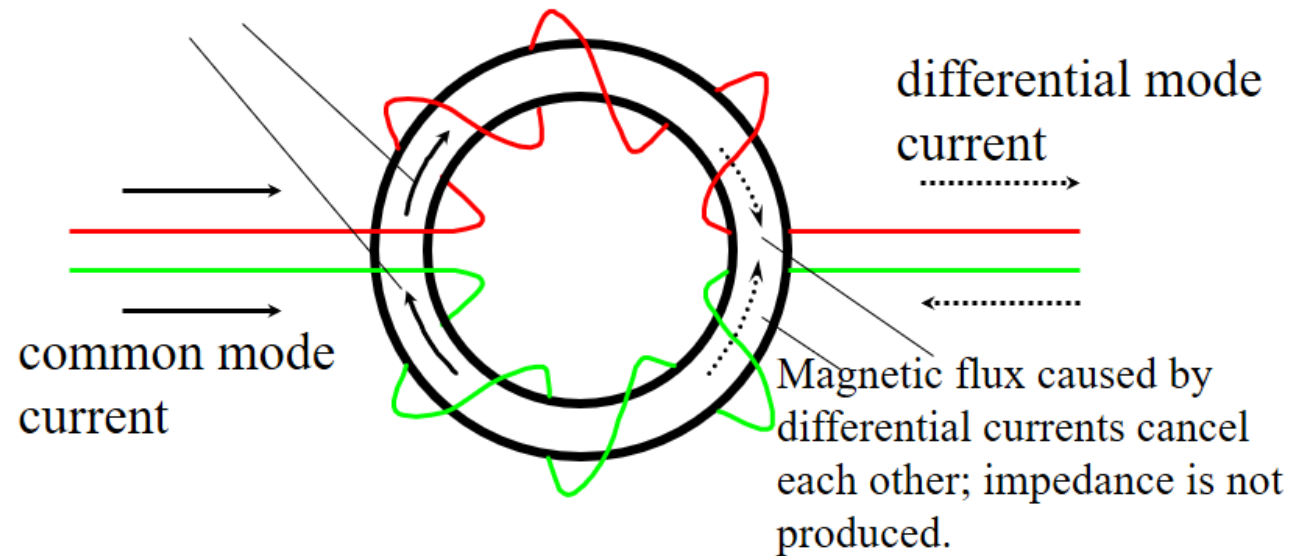Magnetic flux caused by common mode current adds up, producing an opposing impedance.



Impedance of a Balun/Choke

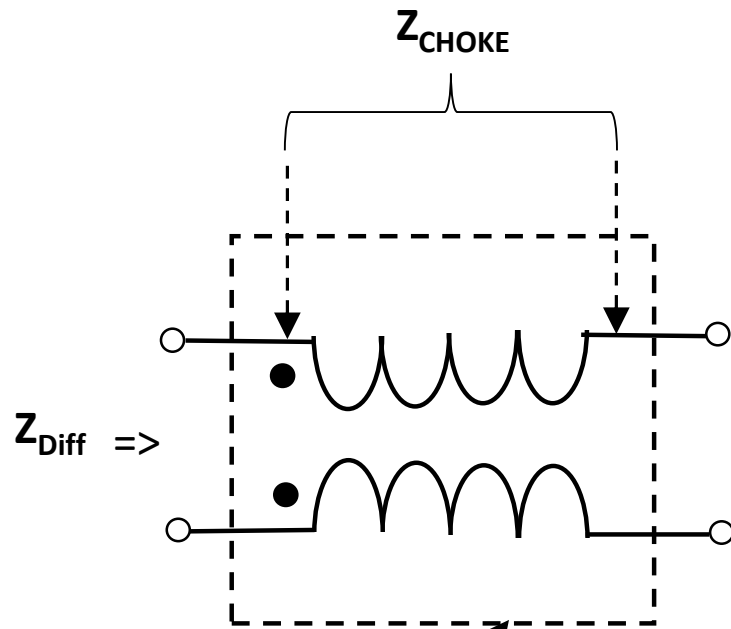
- Common Mode signal sees a choke
 - Z_{CHOKE} varies with
 - Frequency
 - Type of balun & design
- Differential signal only sees a transmission line
 - $Z_{\text{Diff}} \sim 0$
- Impedance can be:
 - Resistive and reactive
 - Mostly resistive
 - Mostly reactive
 - Inductive below **self resonant frequency (SRF)**
 - Capacitive above SRF




Transmission Line Transformer (TLT)

Self Resonance In Inductors

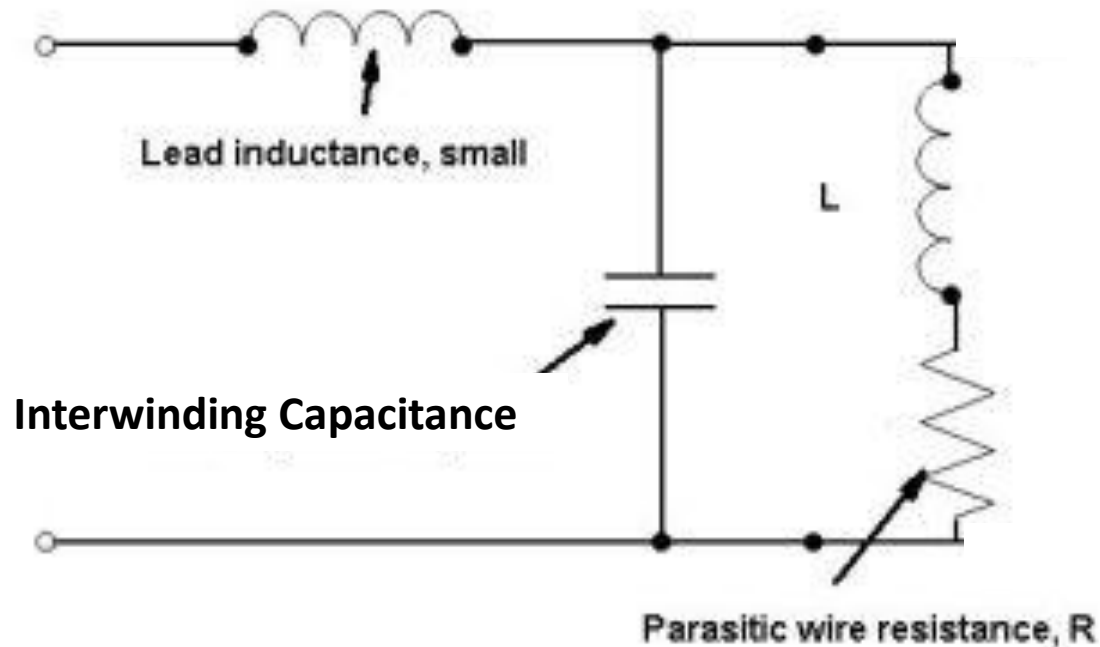Equivalent circuit of a wire-wound inductor



6.8 uH High Q Toroid Inductor

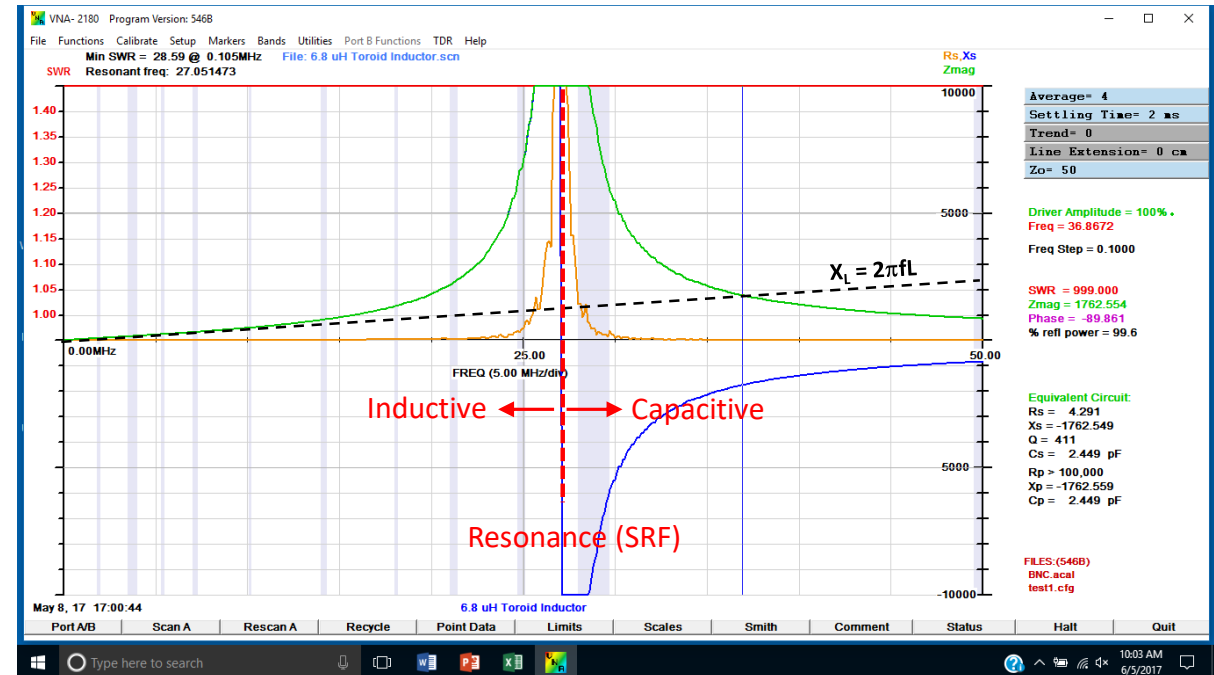

Examples: Current Chokes

Homebrew Sleeve Choke



Mostly resistive & Low Q

Homebrew Toroidal Choke



Mostly reactive & High Q


Examples: Current Chokes

Homebrew Sleeve Choke



Mostly resistive & Low Q

Homebrew Toroidal Choke

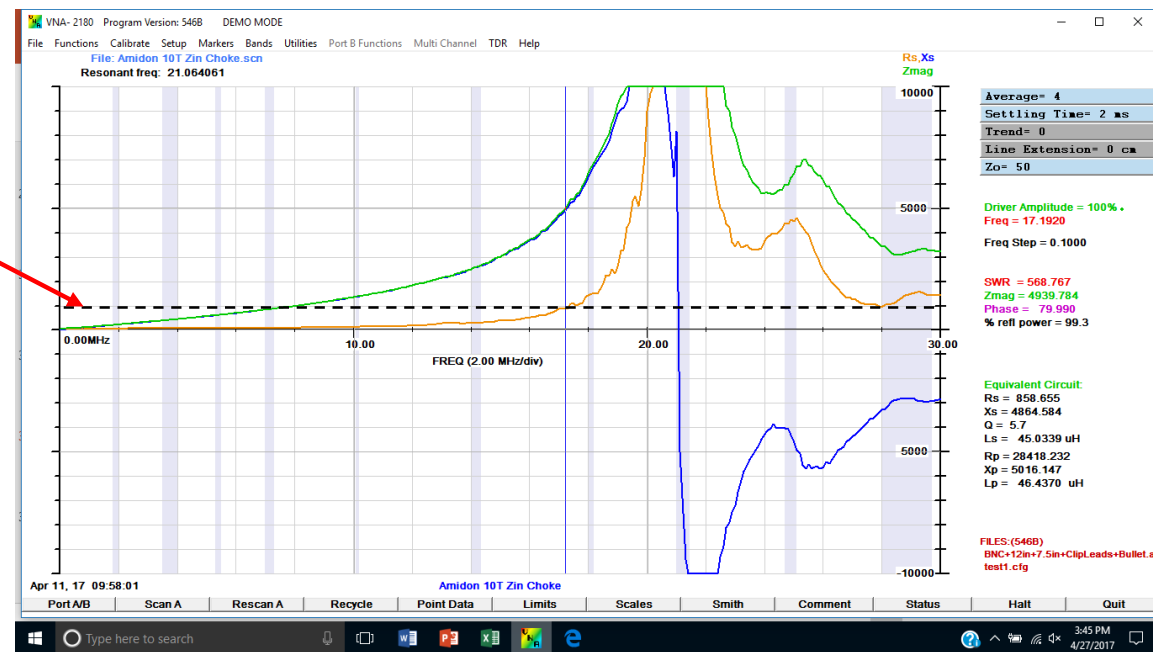


Mostly reactive & High Q

Common Mode Choke Impedance

- Should a Common Mode Choke be mostly resistive, or mostly reactive?
 - Resistive chokes **dissipate** the Common Mode energy
 - Example: $Z_{\text{choke}} = 100 + j0$
 - **Will always decrease** Common Mode Current
 - Difficult to achieve high resistances
 - **Choke's core can overheat, even if it is not saturated!**
 - Saturated core with low duty cycle may not overheat, but => nonlinear => **distortion**
 - Reactive chokes **reflect** the Common Mode energy (**if no System resonance**)
 - Example: $Z_{\text{choke}} = 0 + j100$
 - **System** resonance can **increase** Common Mode Current
 - This choke's core is not as likely to overheat
 - Is reflected Common Mode energy radiated by the antenna?
- Which is better?
 - Must look at "System" issues to answer

Common Mode Choke Impedances (G3TXQ)

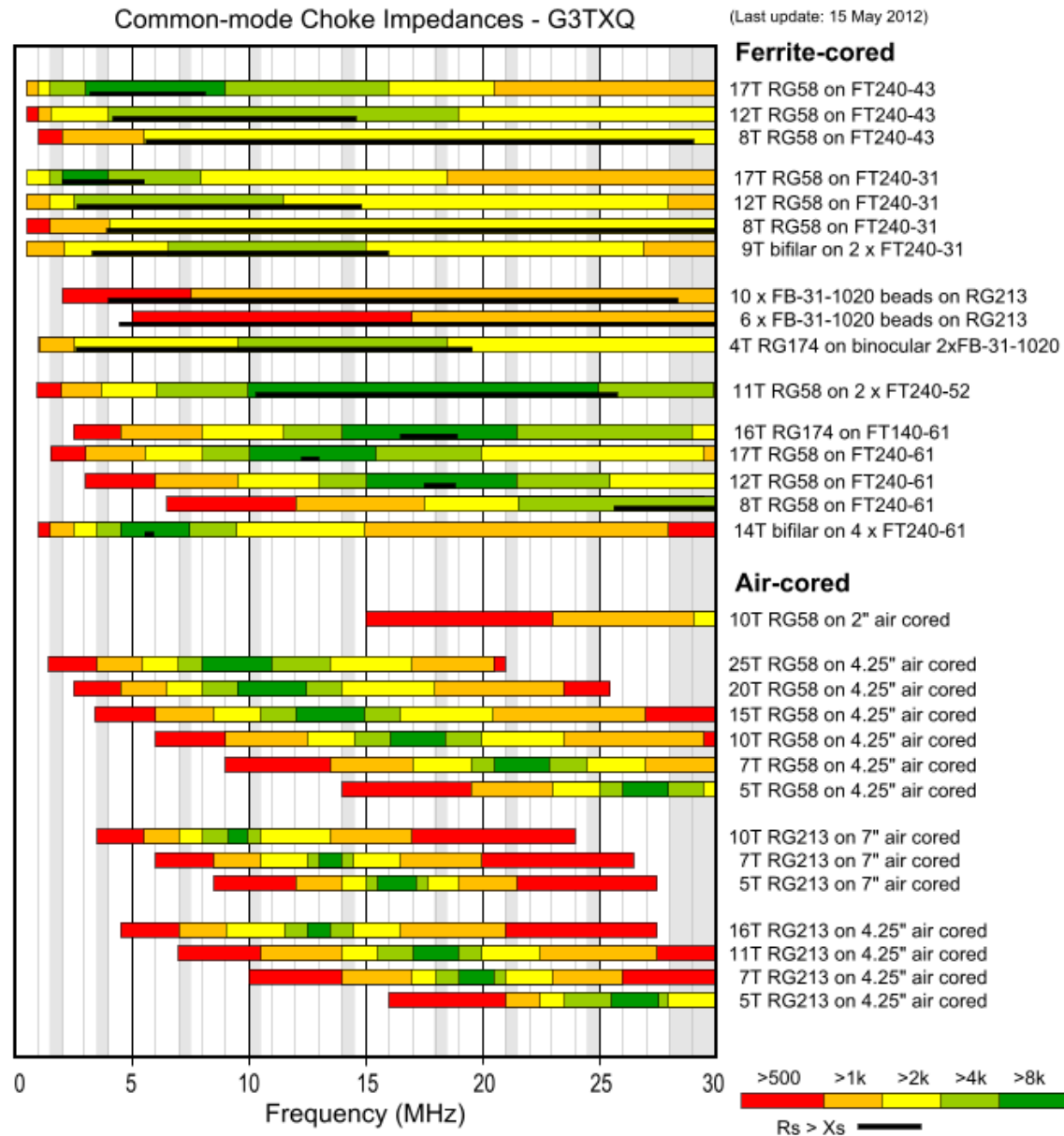

Topics – Part 2

- Tripole
- Risk of Installing a Balun
- How to Reduce Common Mode currents
- How to Build Current Baluns & Chokes
 - Transmission Line Transformers (TLT)
 - Examples of Current Chokes
 - Ferrite & Powdered Iron (Iron Powder) Suppliers