

# Baluns & Common Mode Chokes

Bill Leonard N0CU

2 September 2017

# Part 2

## Topics – Part 2

- Tripole
- Risk of Installing a Balun
- How to Reduce Common Mode currents
- How to Build Current Baluns & Chokes
  - Transmission Line Transformers (TLT)
  - Examples of Current Chokes
  - Ferrite & Powdered Iron (Iron Powder) Suppliers


# Sources of Common Mode Current

1. Balanced to Unbalanced signal mismatch
2. Asymmetry in antenna system
3. Pickup from external RF field


Tripole
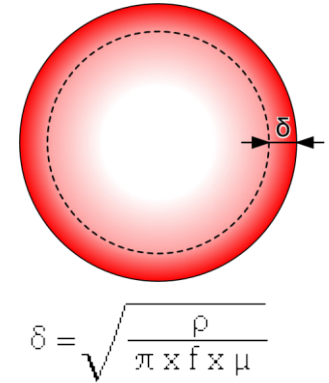
# Skin Effect

- Skin effect:
  - RF currents flow near the outer surface of a conductor
  - The cause of Skin Effect is electromagnetic induction
    - Can be explained by Maxwell's equations
  - Skin depth =  $\delta$ 
    - The higher the frequency, the smaller the skin depth
  - Example (copper):
    - At 14 MHz skin depth = 0.7 microinch
    - Typical coax shield = 20 microinch



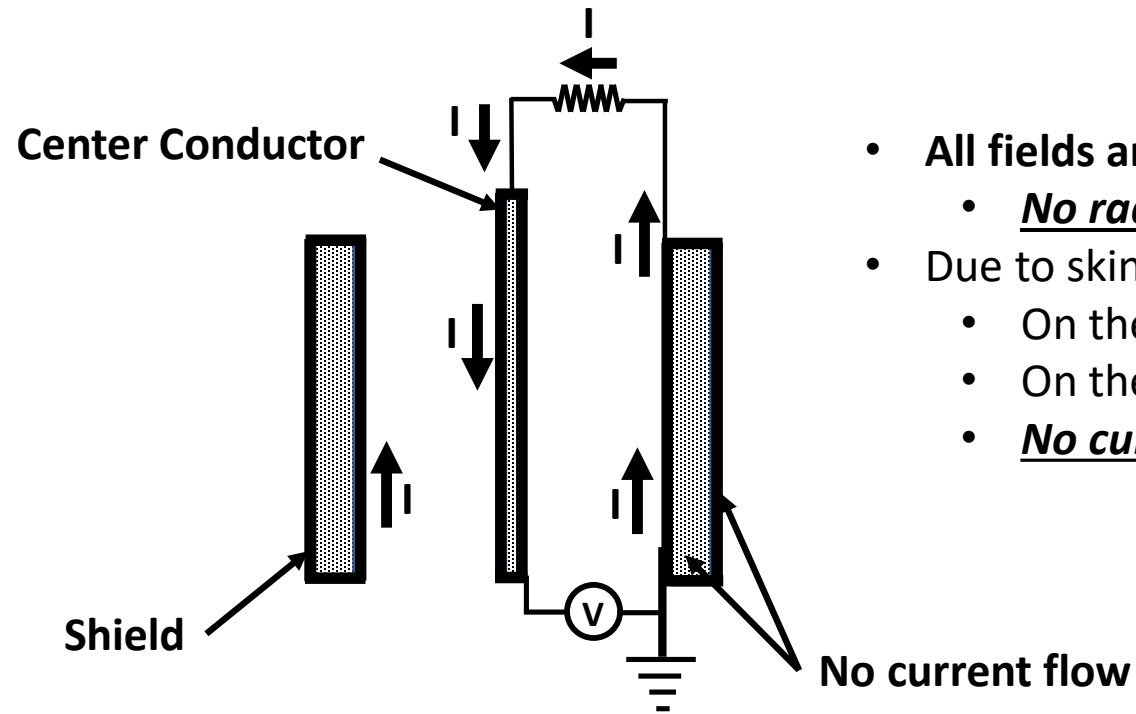
# Differential RF Current Flow In A Coaxial Cable




- All fields are contained between the shield and the center conductor
  - No radiation outside of an ideal cable
- Due to skin effect, Differential RF current flows:
  - On the outside of the center conductor, and
  - On the inside of the shield
  - No current on the outside of the shield
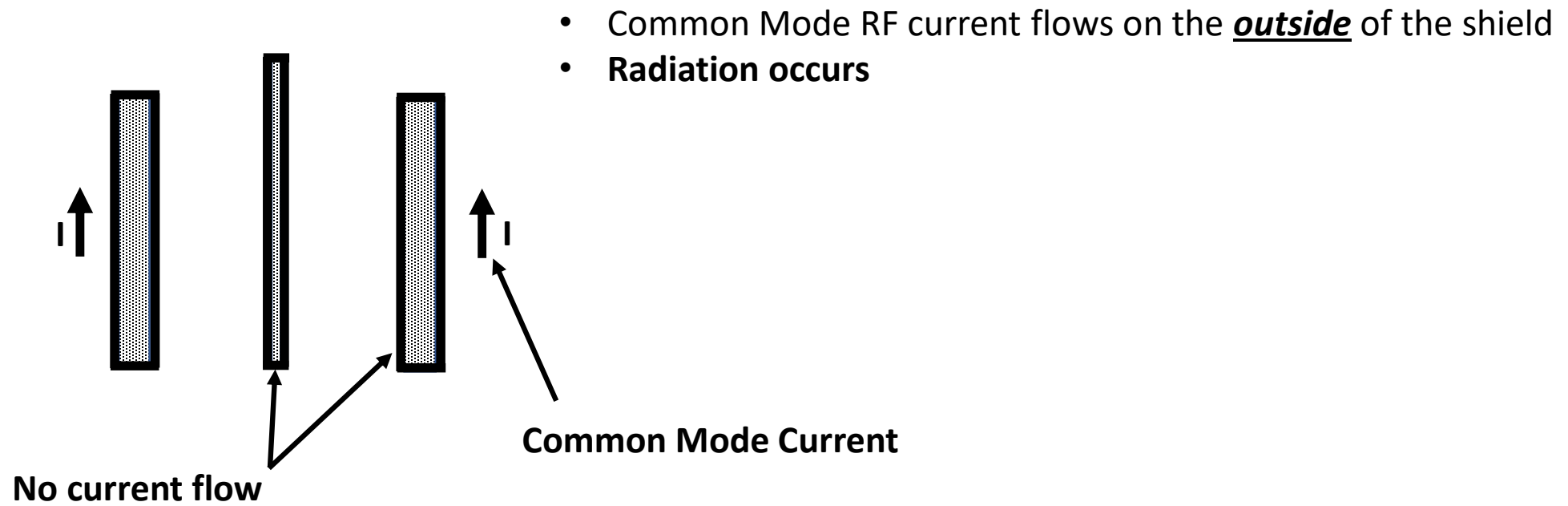
# Common Mode RF Current Flow In A Coaxial Cable







# Balanced Dipole Fed With Balanced Line

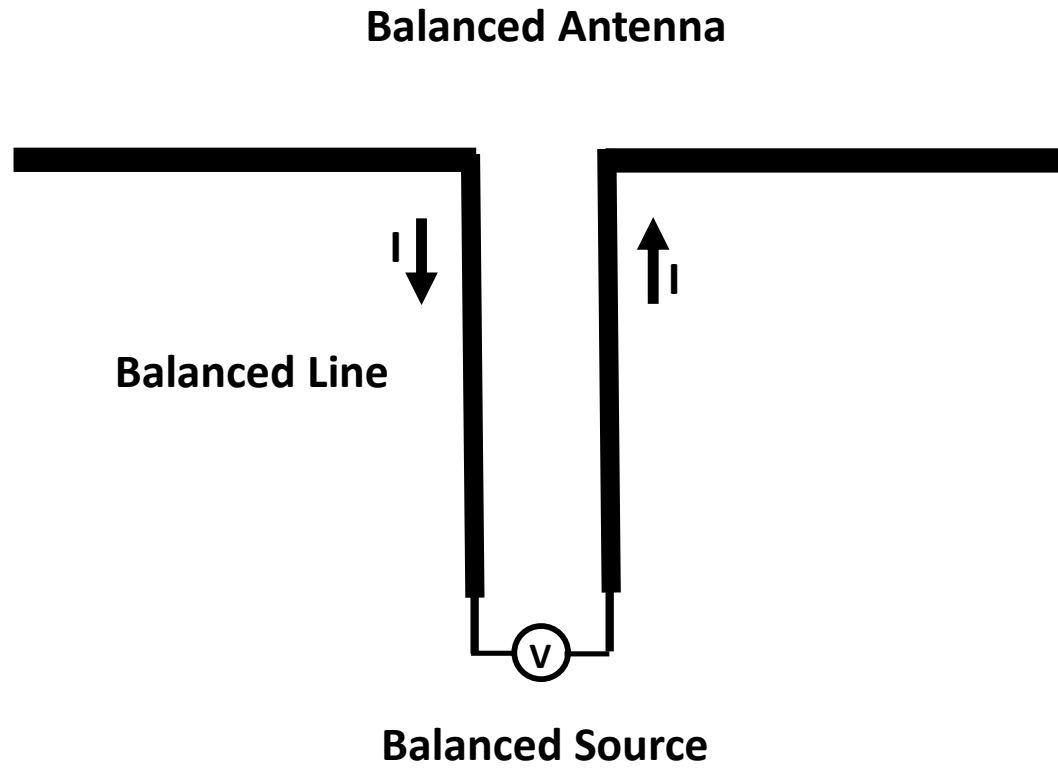

# Dipole Fed With Coax Without Balun

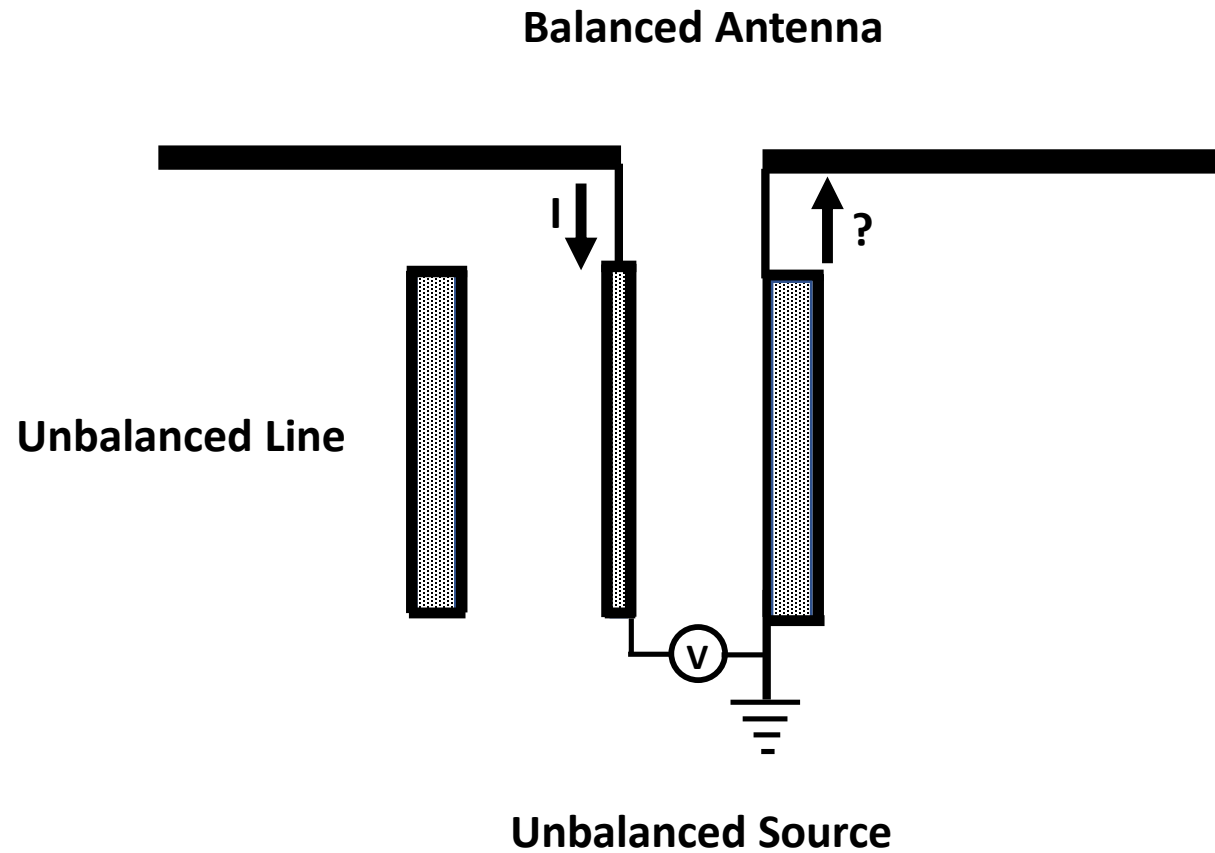

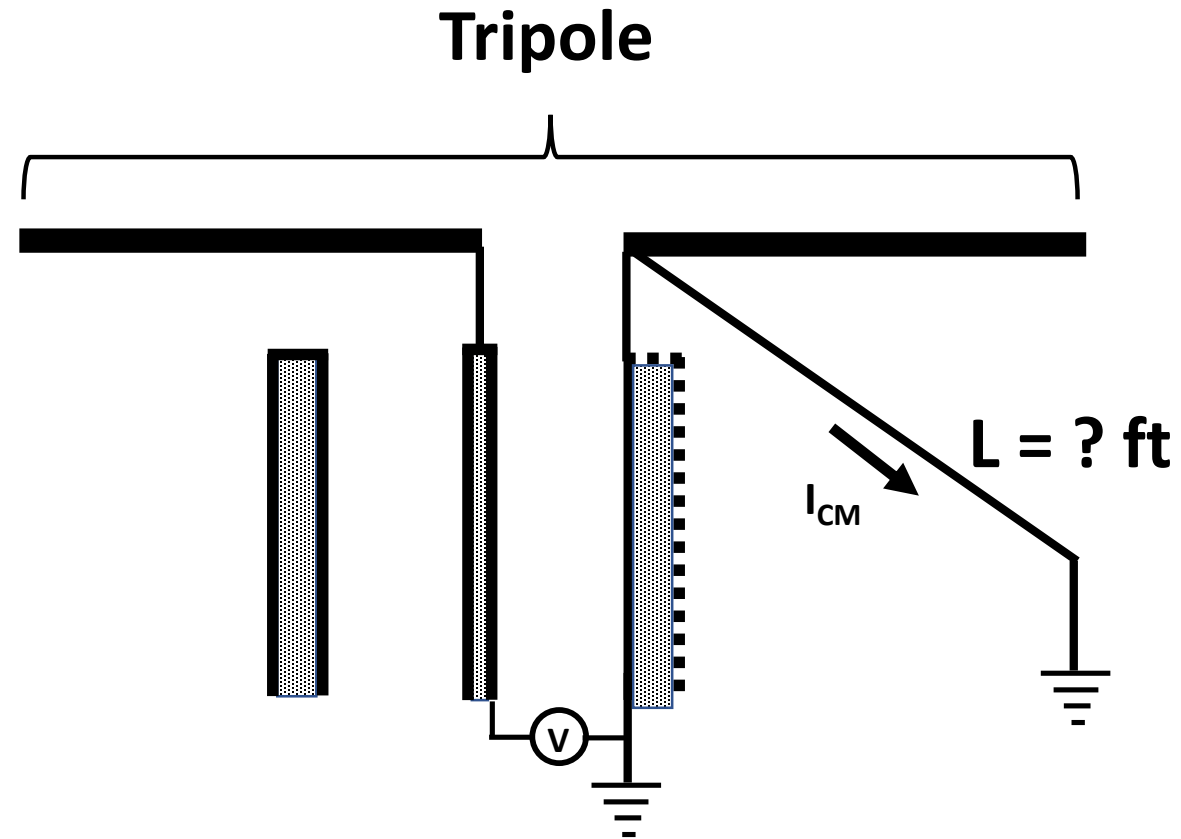
# Dipole Fed With Coax Without Balun – cont'd



Unbalanced Source
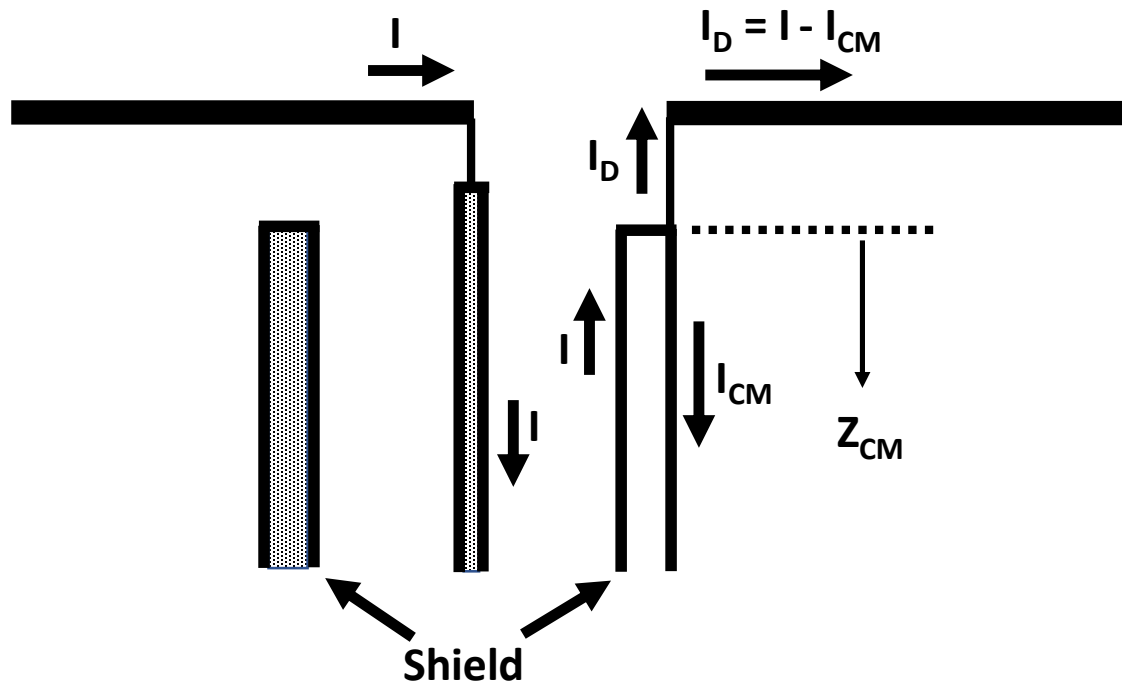
# What Is a Tripole?




- A coaxial cable connected directly to a half wave dipole = “Tripole”



- Due to skin effect:
  - **Differential RF current:**
    - Flows only :
      - On the outside of the center conductor
      - On the inside of the shield
    - Sees three conductors when it reaches the dipole
      - 1) Left dipole element
      - 2) Right dipole element
      - 3) Outside of the shield
    - Current splits into  $I_D$  &  $I_{CM}$
  - The Common Mode Impedance of the shield =  $Z_{CM}$ 
    - $Z_{CM}$  is a function of:
      - Frequency
      - Length of the coaxial cable
      - How the cable is terminated at the transmitter
      - Location of RF ground
      - RF characteristics of the ground

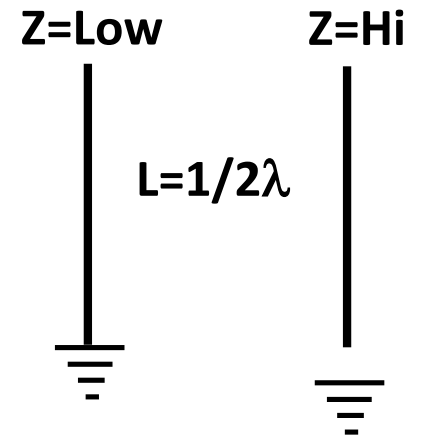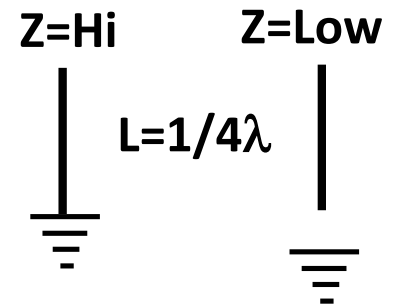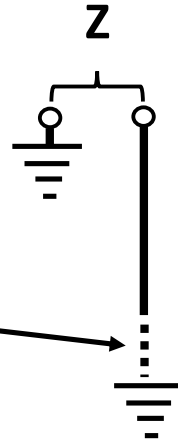
# RF Impedance of a Conductor

- RF impedance of a short wire conductor is usually inductance + resistance
  - Short is  $< 1/10$  wavelength
- RF impedance of a long wire conductor is a function of:
  - Frequency
  - Size
  - Length
  - Termination impedance
- $1/4\lambda$  inverts  $Z$ 
  - $1/4\lambda$  vertical antenna  $\Rightarrow Z = 32$  ohms
- $1/2\lambda$  replicates  $Z$ 
  - End fed  $1/2\lambda$  antenna  $\Rightarrow Z > 2000$  ohms




# Circuit Models for Balun/Choke

Circuit model for Balun and Coax Shield

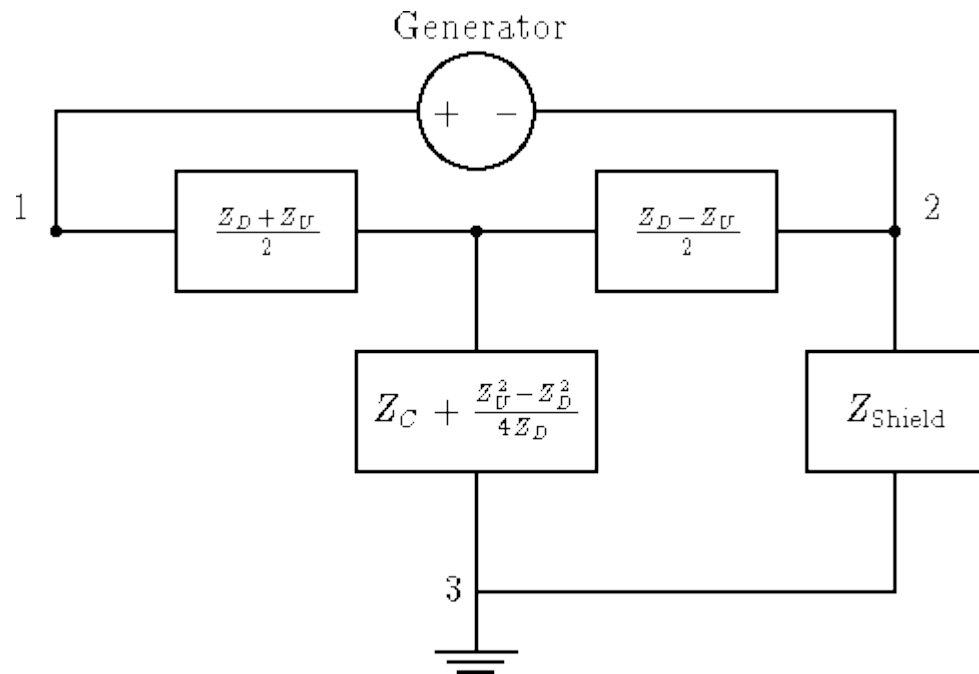


Simplified circuit model for Balun

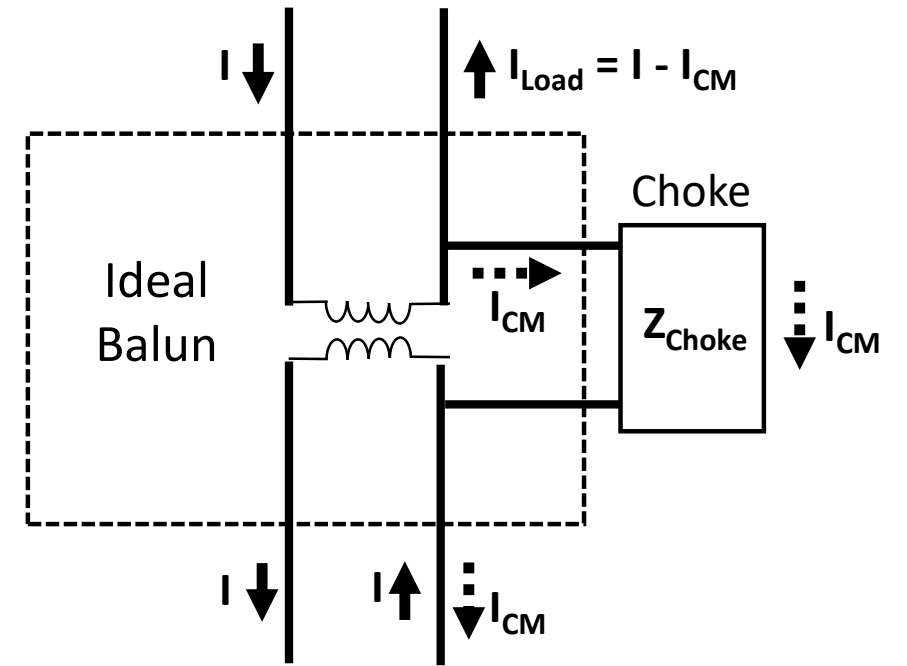


$$Z_{Choke} = R_{Choke} + jX_{Choke}$$

# Dipole With a Balun


## Ideal Balun

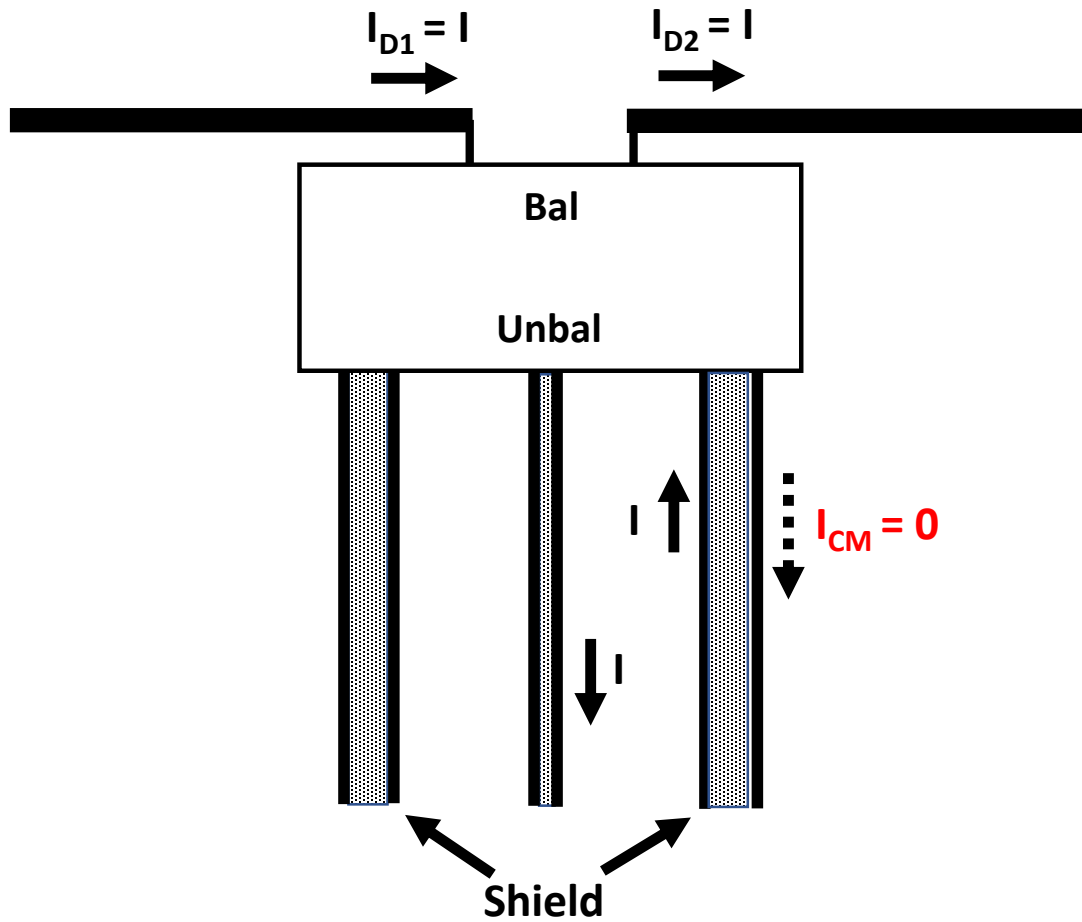

## Real Balun

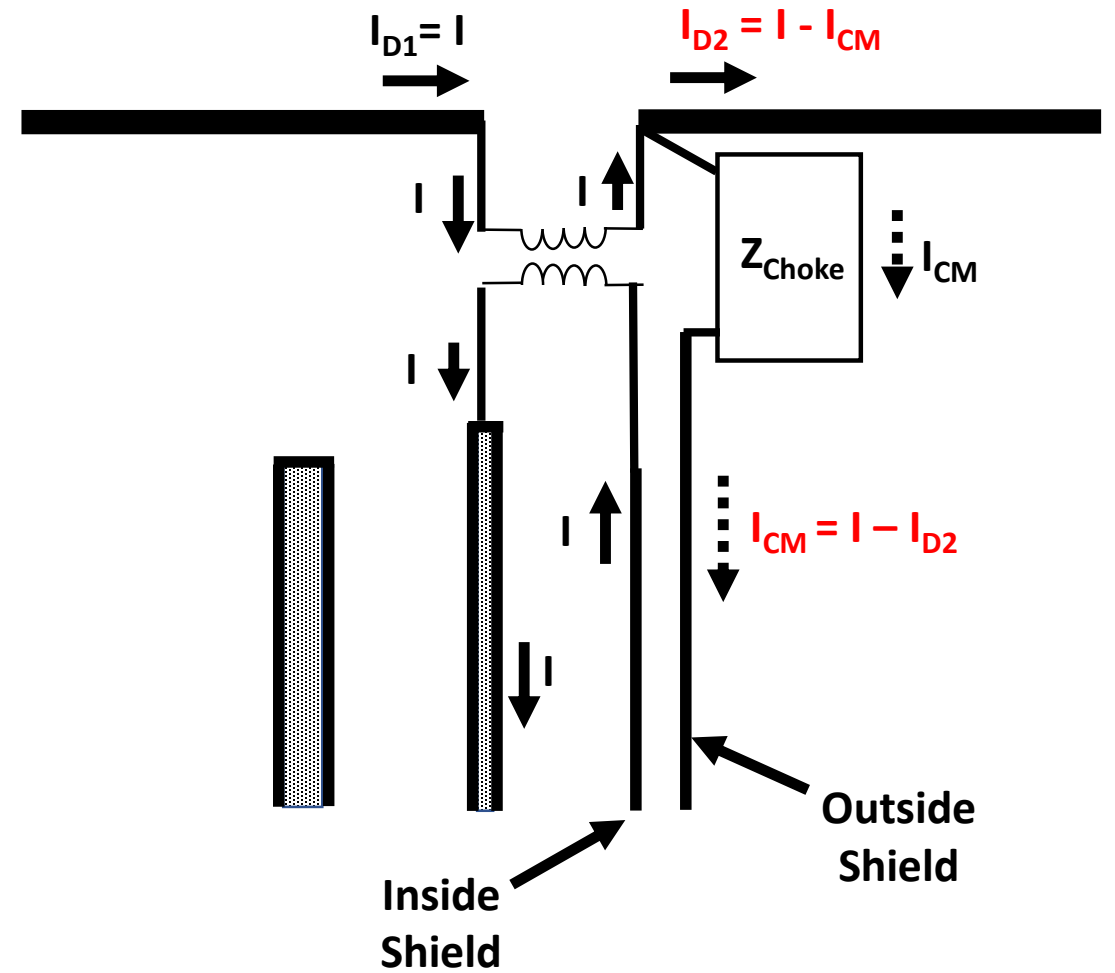


# Dipole With Real Balun – cont'd

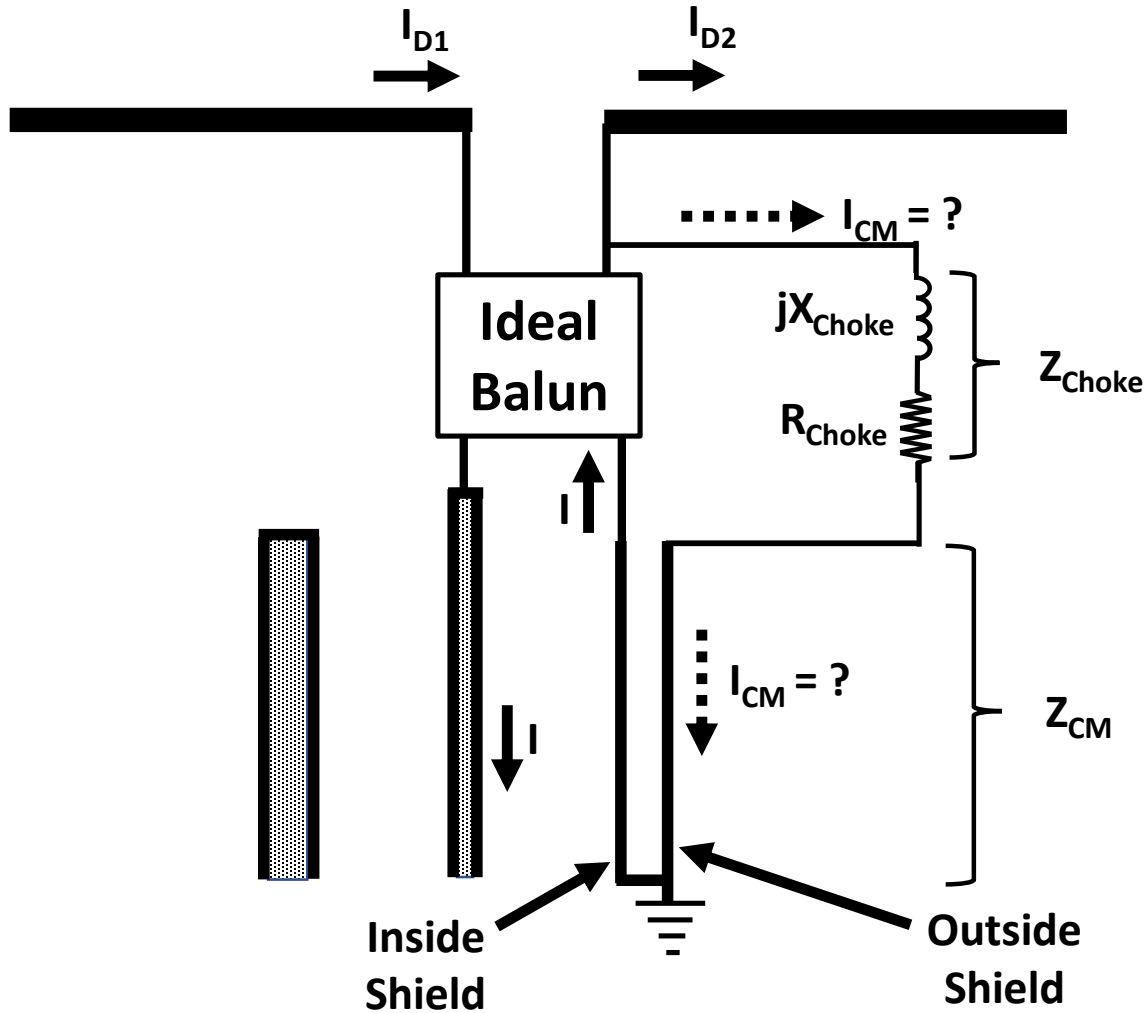



Only recently has the importance of  $Z_{CM}$  been understood.



# Dipole With Real Balun – cont'd

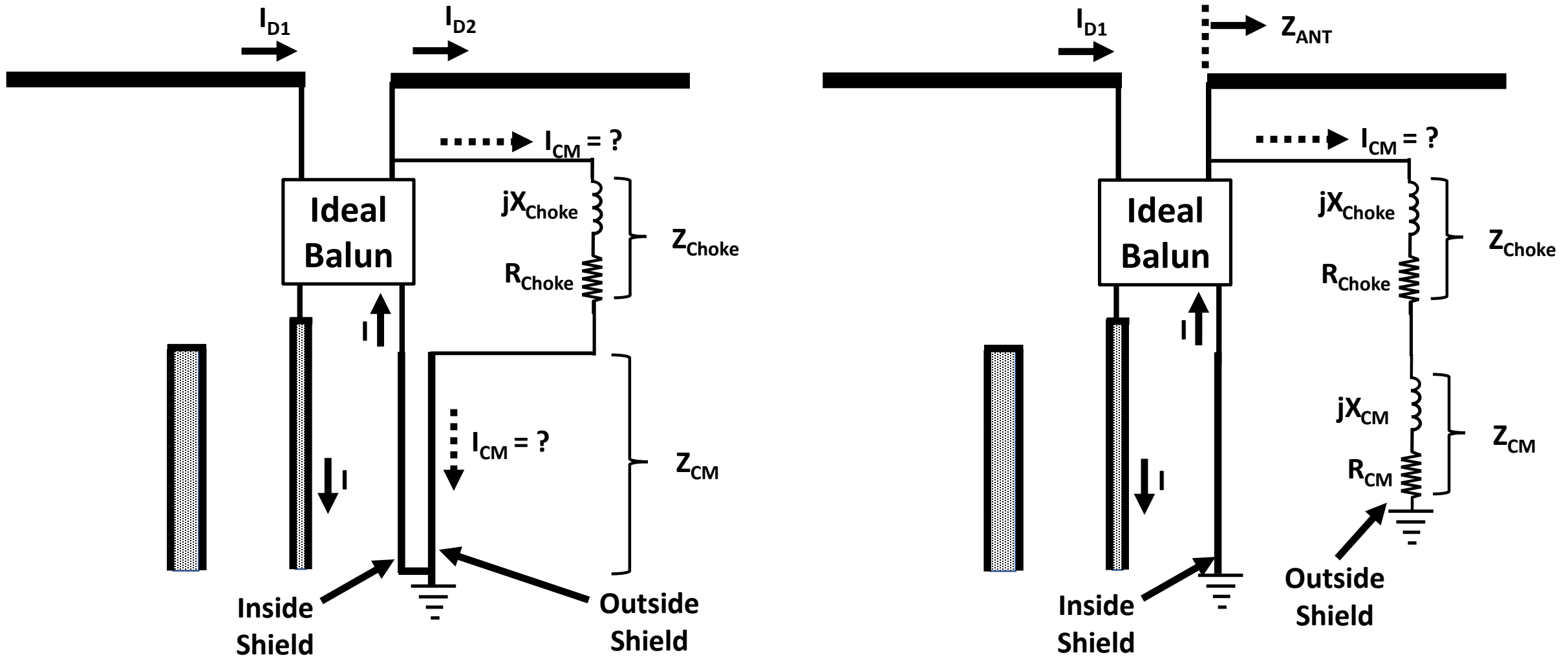

# Dipole With a Balun – Two Ideal Cases

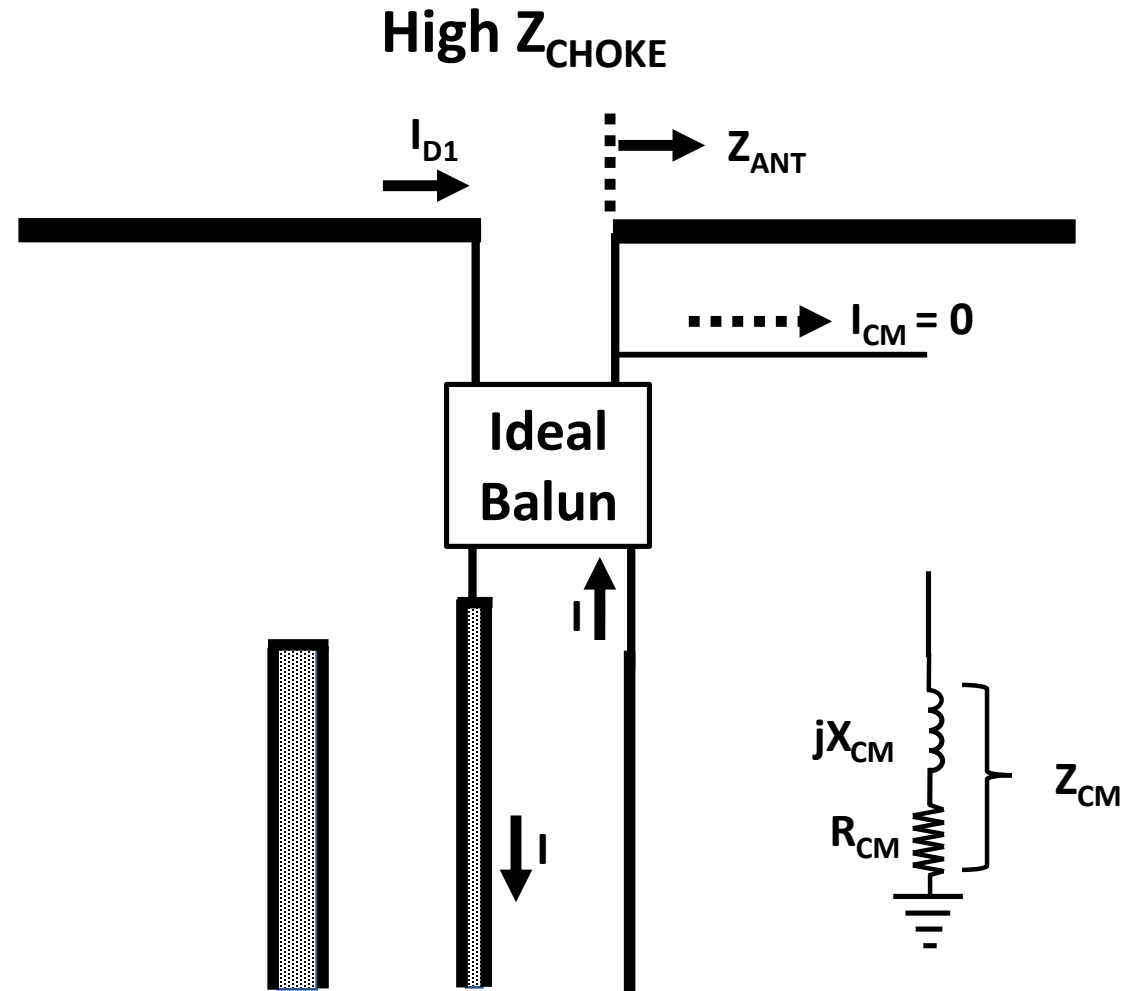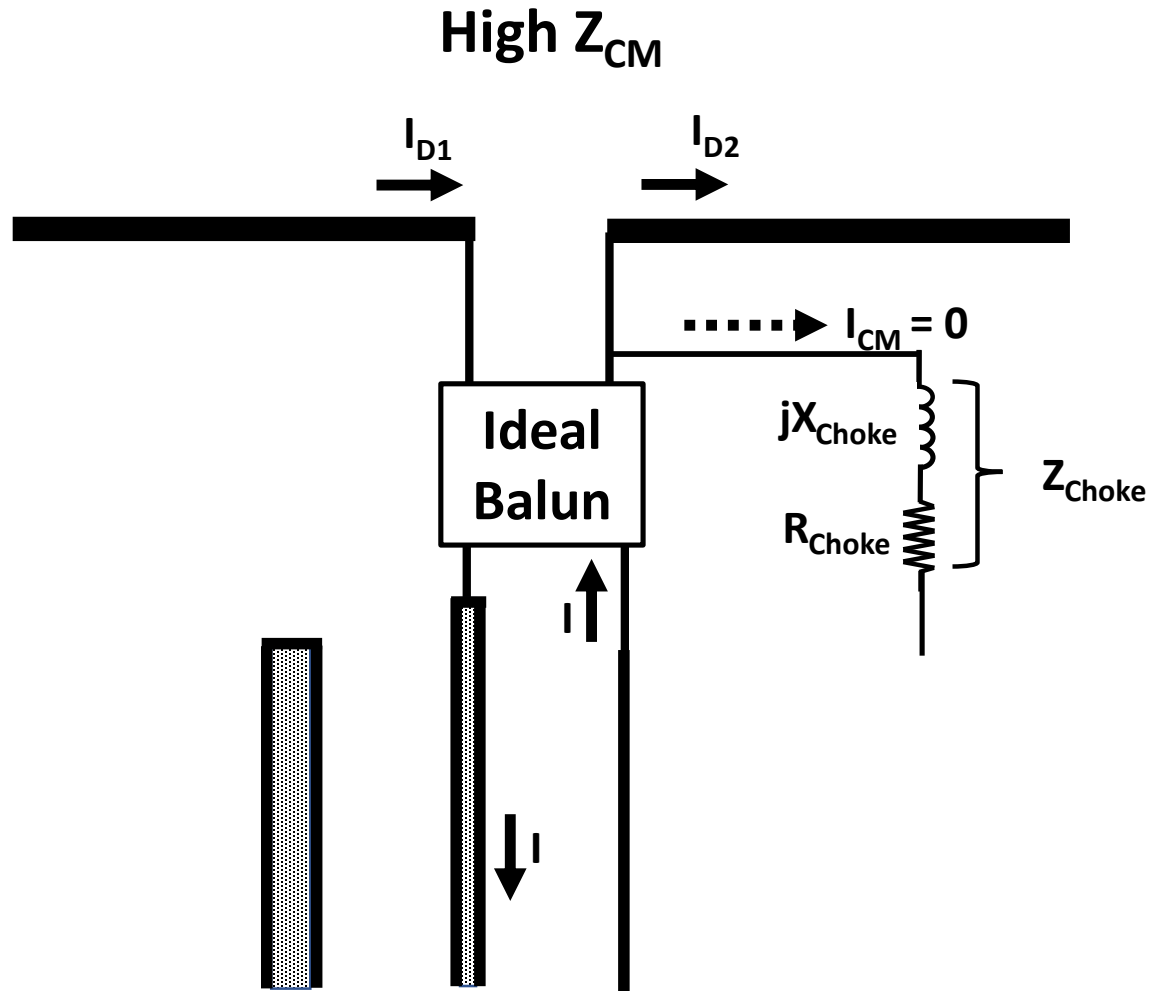


# Risk of Installing a Balun

# Risks of Installing a Balun

1. If you don't have a Common Mode Current problem, installing a Balun may create one, or make an existing one worse
  - Common Mode current problems can be hard to identify
2. Failure of the Balun due to overheating
3. Increased InterModulation Distortion (IMD) on transmit signal
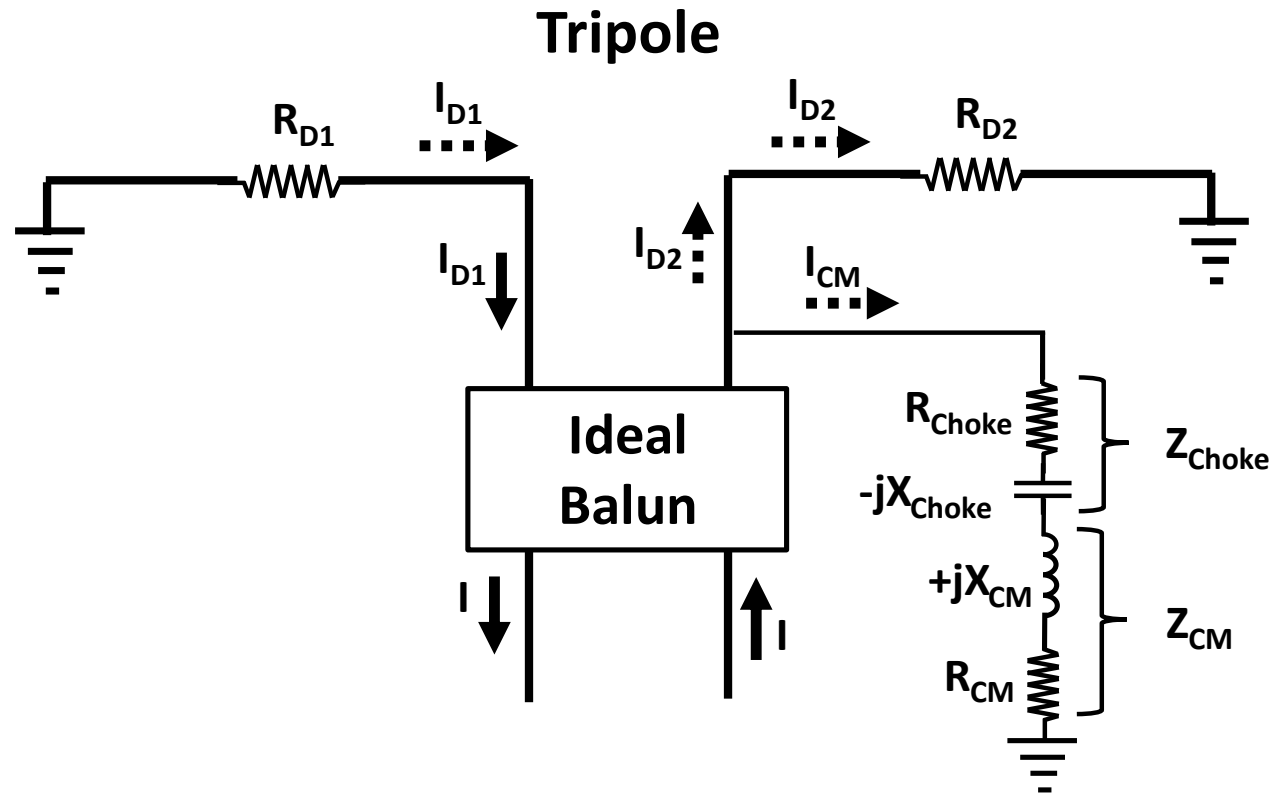
# Unwanted System Resonance

- Resonance occurs when  $X_{CM}$  cancels  $X_{Choke}$ 
  - $I_{CM}$  is limited only by  $R_{CM} + R_{Choke}$




When:

$$X_{Choke} = -X_{CM} \text{ and} \\ (R_{Choke} + R_{CM}) \ll R_{D2}$$



$$I_{CM} = I \text{ and} \\ I_{D2} = 0$$

# Unwanted System Resonance – cont'd

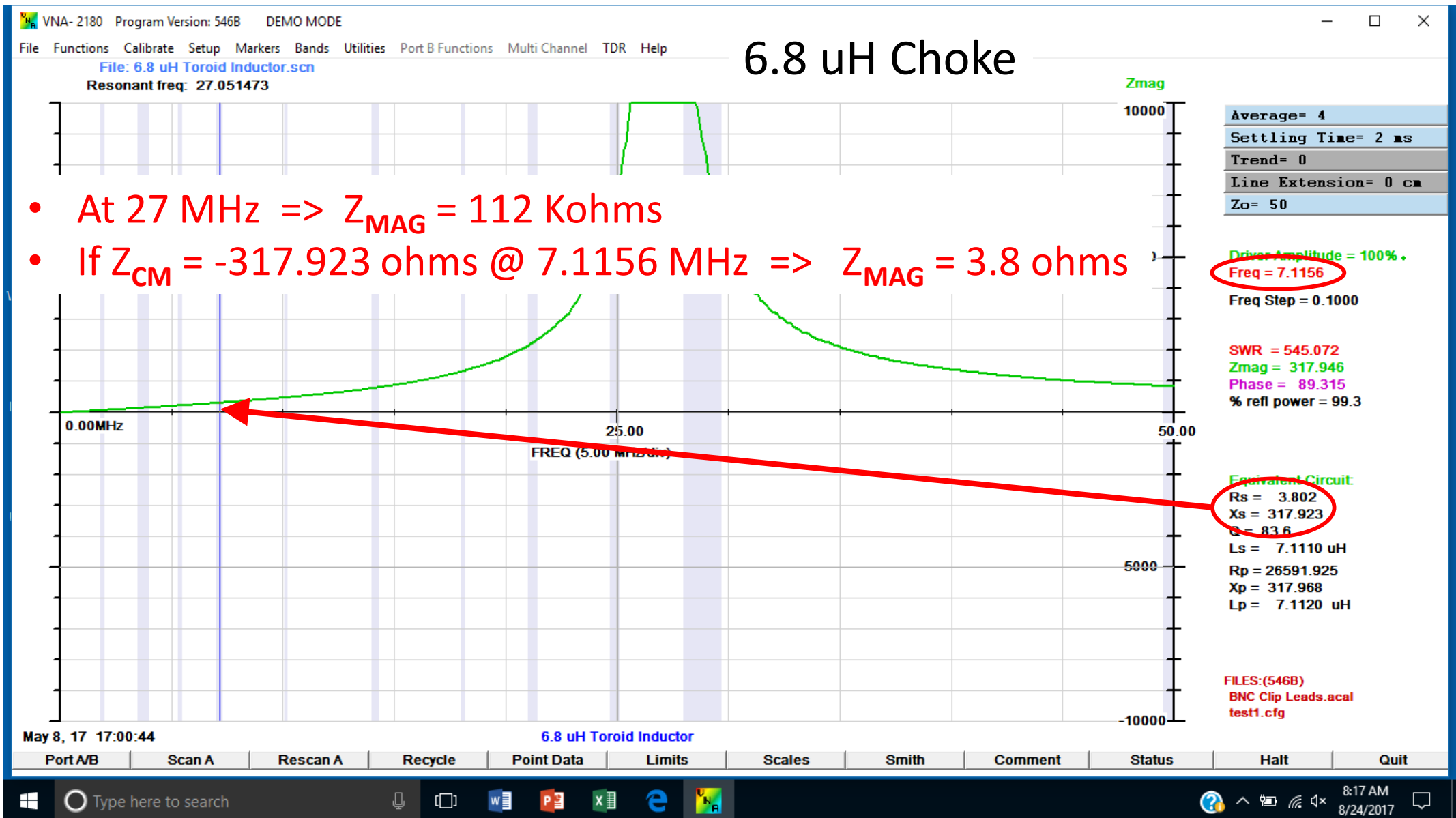


# Common Mode Impedance of a Coaxial Cable Shield

- $Z_{CM}$  is:
  - Very dependent upon:
    - Length and size of the cable
    - Location and impedance of the RF ground
  - Not easily measured
- ***EZNEC cannot model Common Mode Currents on a transmission line***
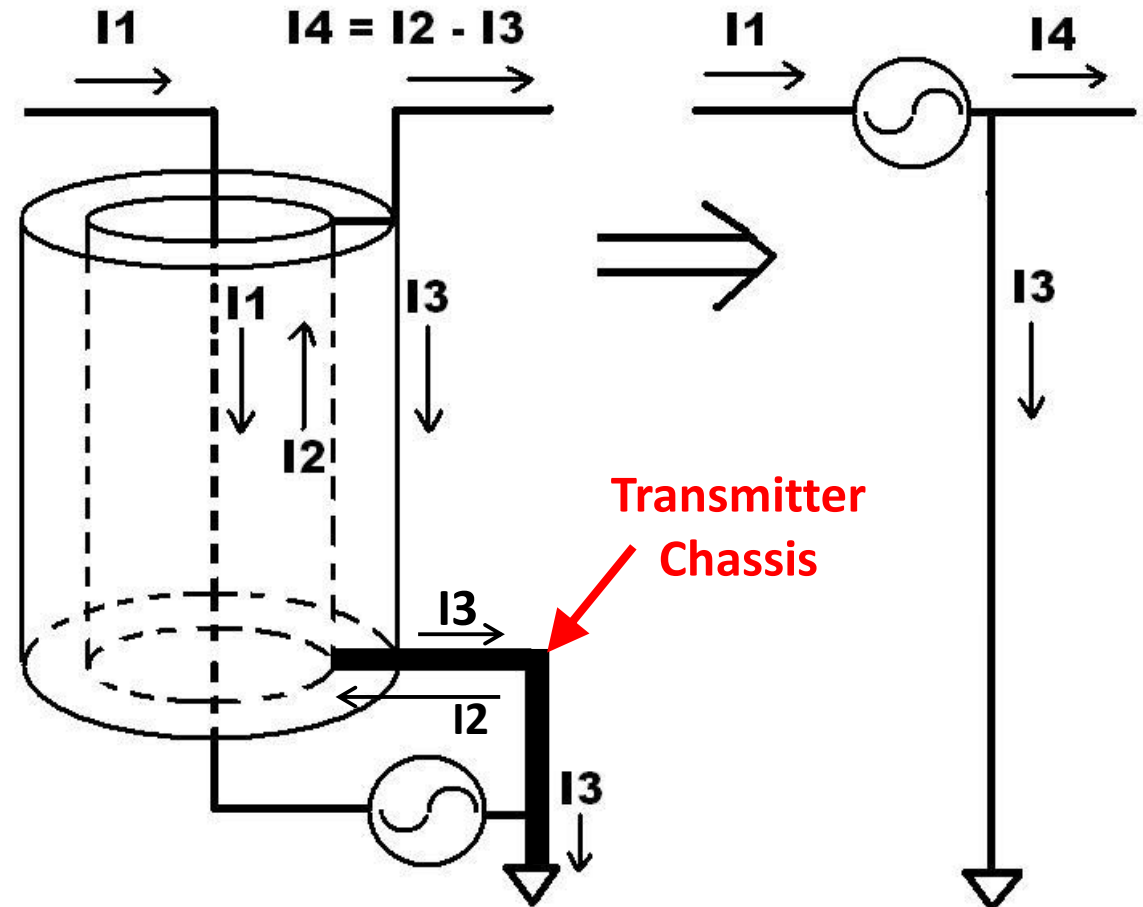
# To Use EZNEC To Roughly Estimate $I_{CM}$ : Tom Thompson (W0IVJ)

- Important assumptions:
  1. Perfect **RF** ground
  2. **RF** ground at known location
  3. No Balun
  4. Source moved up to antenna feed point
  5. Transmission line replaced with a wire






# Example of Tripole Common Mode Current: Tom Thompson (W0IVJ)


- 40 M halfwave Dipole with **halfwave wire for feed line**
- No Balun
- Tx power = 1500 W
- Feedline **NOT** grounded

**This is a dipole!**

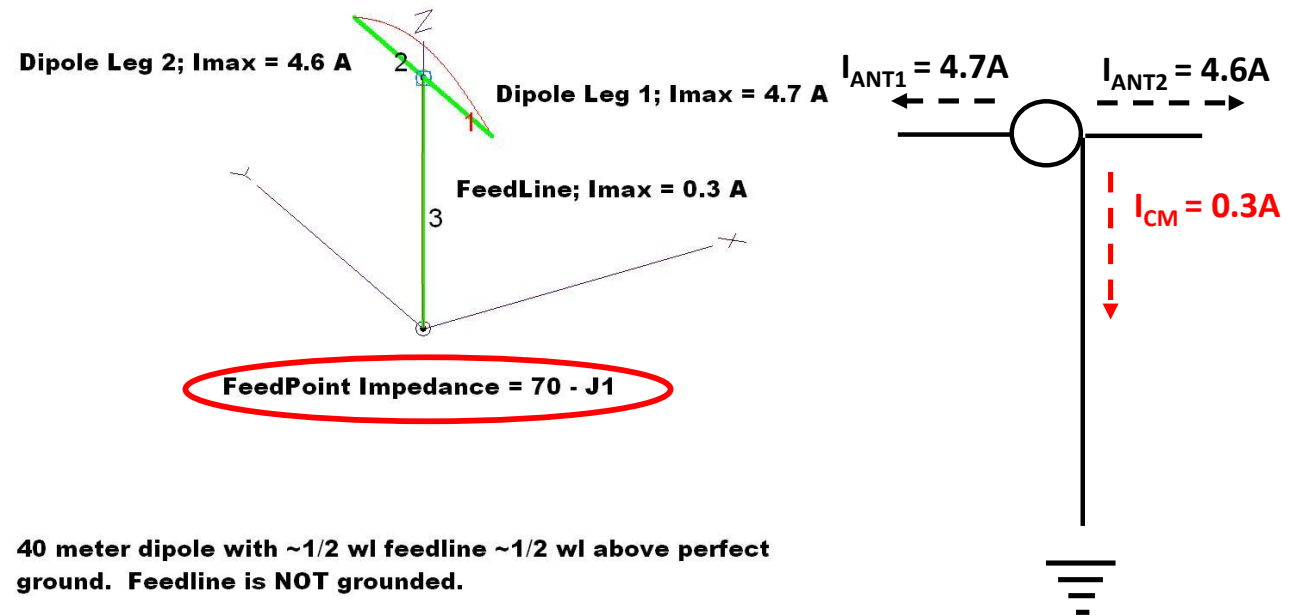
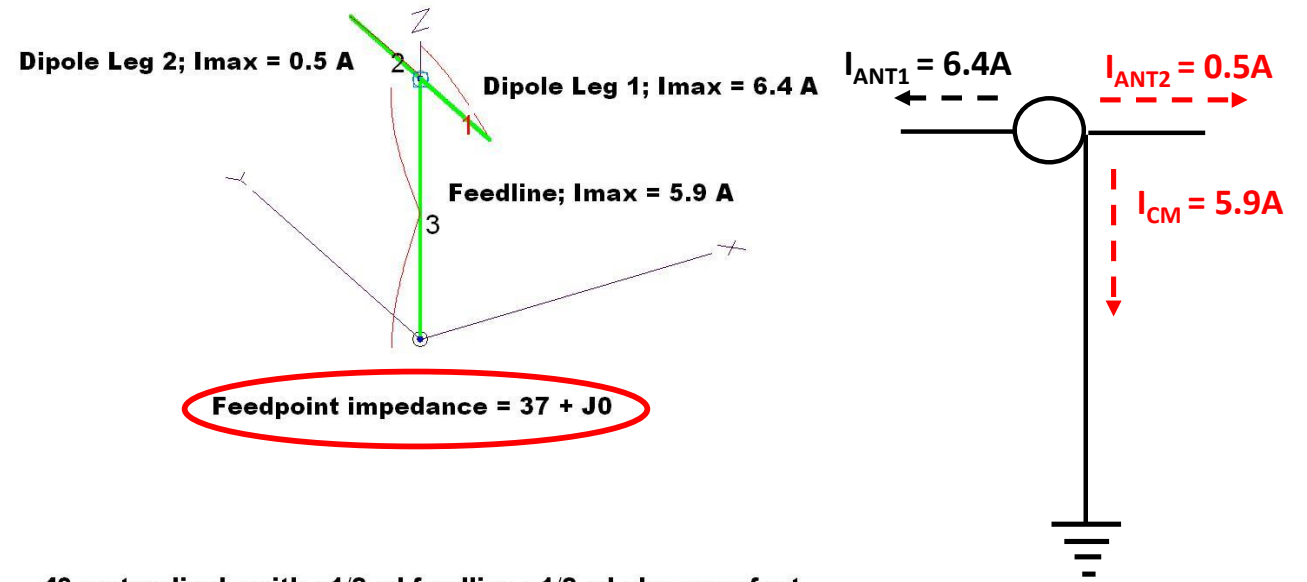
# Example of Tripole Common Mode Current - cont'd


- 40 M halfwave Dipole with **halfwave wire for feed line**
- No Balun
- Tx power = 1500 W
- Feedline **grounded**



# Example of Tripole Common Mode Current - cont'd


- 40 M halfwave Dipole with **halfwave wire for feed line**
- No Balun
- Tx power = 1500 W
- Feedline **grounded**

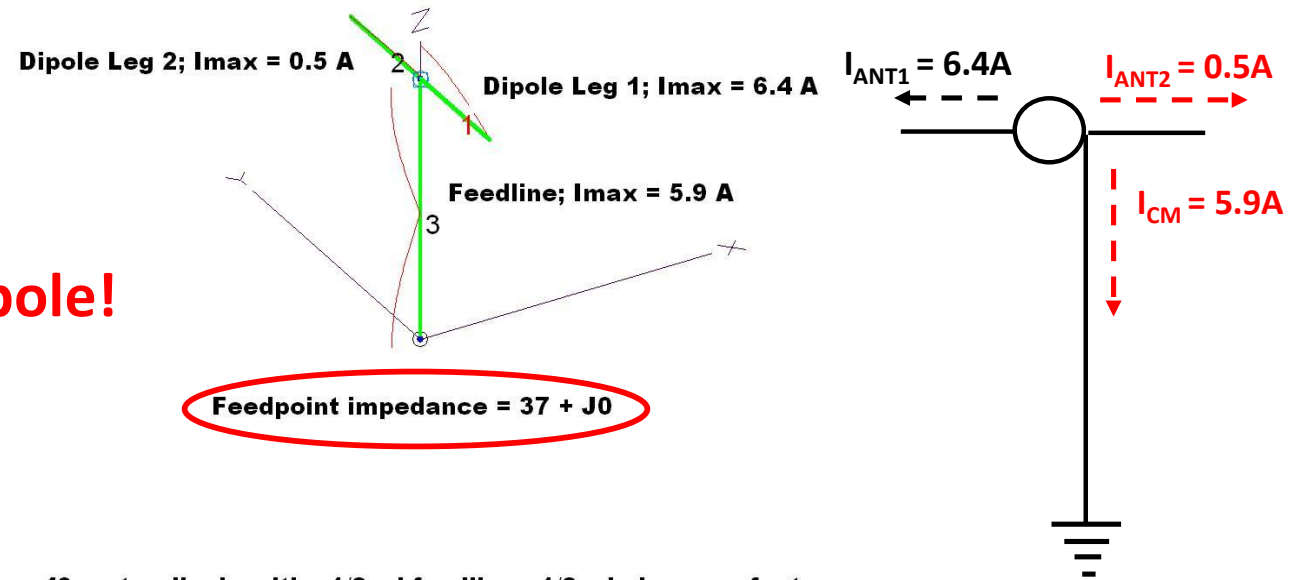**This is an inverted L antenna, not a dipole!**



40 meter dipole with  $\sim 1/2$  wl feedline  $\sim 1/2$  wl above perfect ground. Feedline IS grounded at transmitter end.
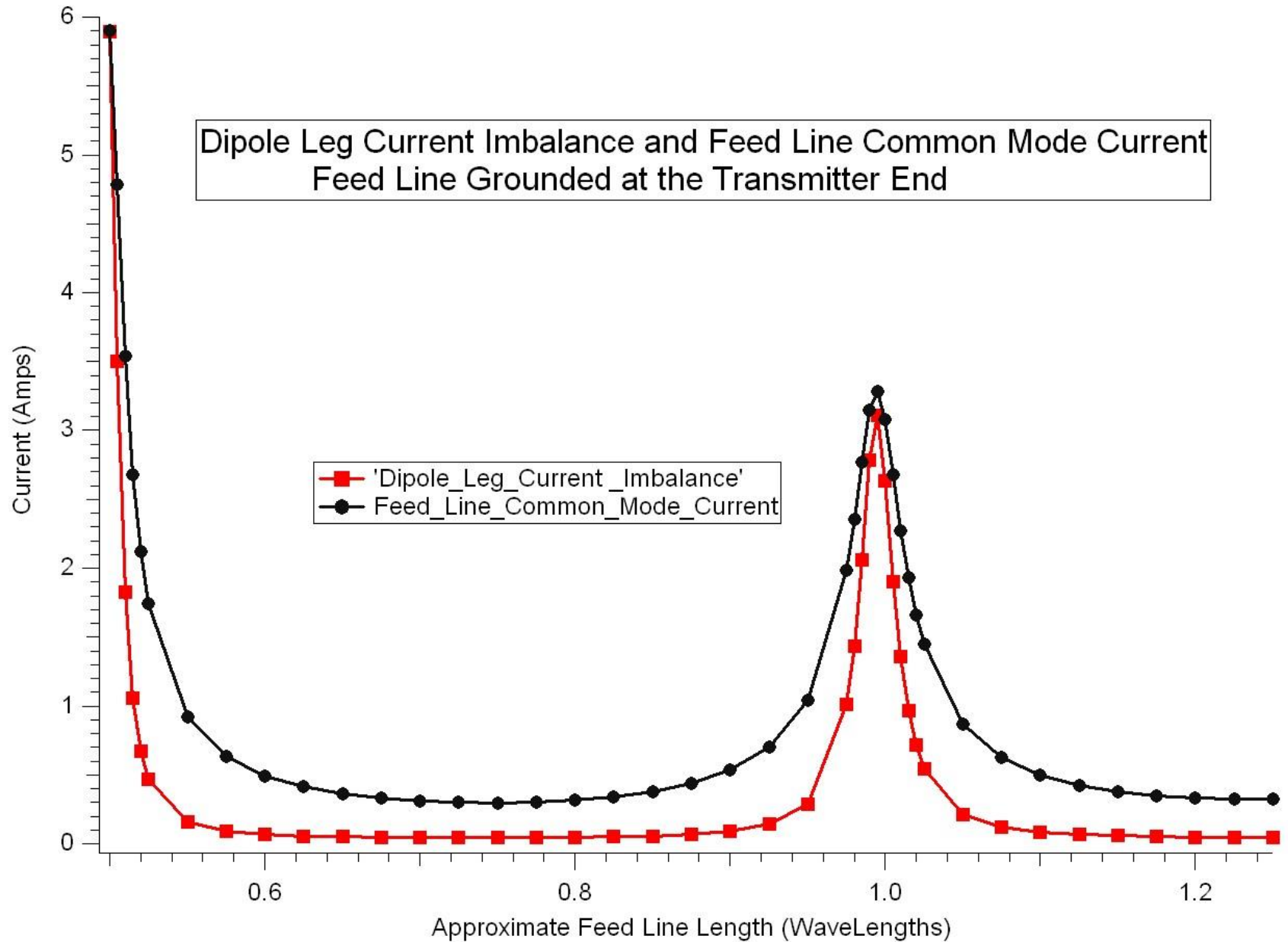
# Importance of Transmission Line Length : Tom Thompson (W0IVJ)



# Importance of Transmission Line Length – cont'd

- How long should a transmission line be to minimize  $I_{CM}$  ?
  - Note: length is physical length (x 0.98) to **RF ground**
  - **No Balun:**
    - Monoband antennas:
      - Use odd multiple of  $\frac{1}{4}$  wavelength
    - Multiband antennas: There may be no one length that is good for all bands
  - **With Balun: ???**
    - Chose a length that will avoid resonance
    - Some “Experts” recommend multiple of  $\frac{1}{2}$  wavelength
      - This seems like the worst choice to me => Use odd multiple of  $\frac{1}{4}$  wavelength

# Options When Installing a Balun

- Bottom line: it can be hard to predict what a Balun will do in any system
  - Option 1: Install a Balun/Choke and hope it is helping and not overheating
  - Option 2: Measure Common Mode Current with and without a Balun
    - Must measure current on outside of coax shield (not the Differential Current)

Roy Lewallen  
W7EL  
“Baluns: ...”

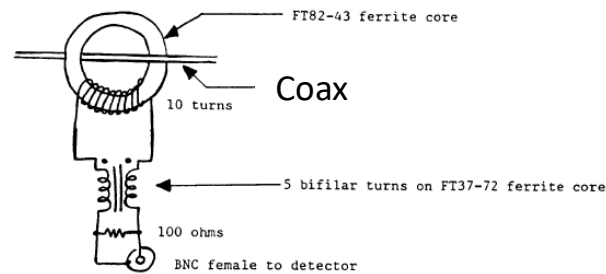


Fig. 12 — Current probe.



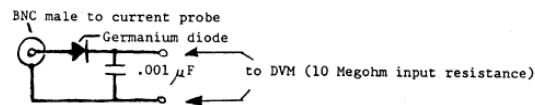


Fig. 13 — Detector.

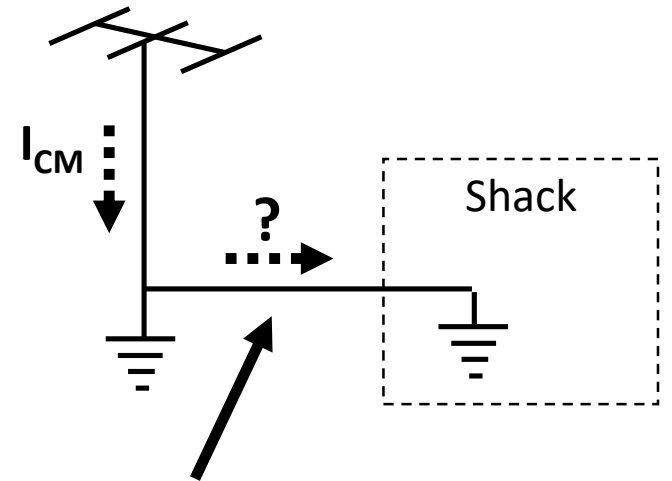

- Making the measurement inside the shack may give erroneous reading
- Option 3: Monitor temperature rise of Balun/Choke during transmit
  - A choke may be cool because it isn't doing anything
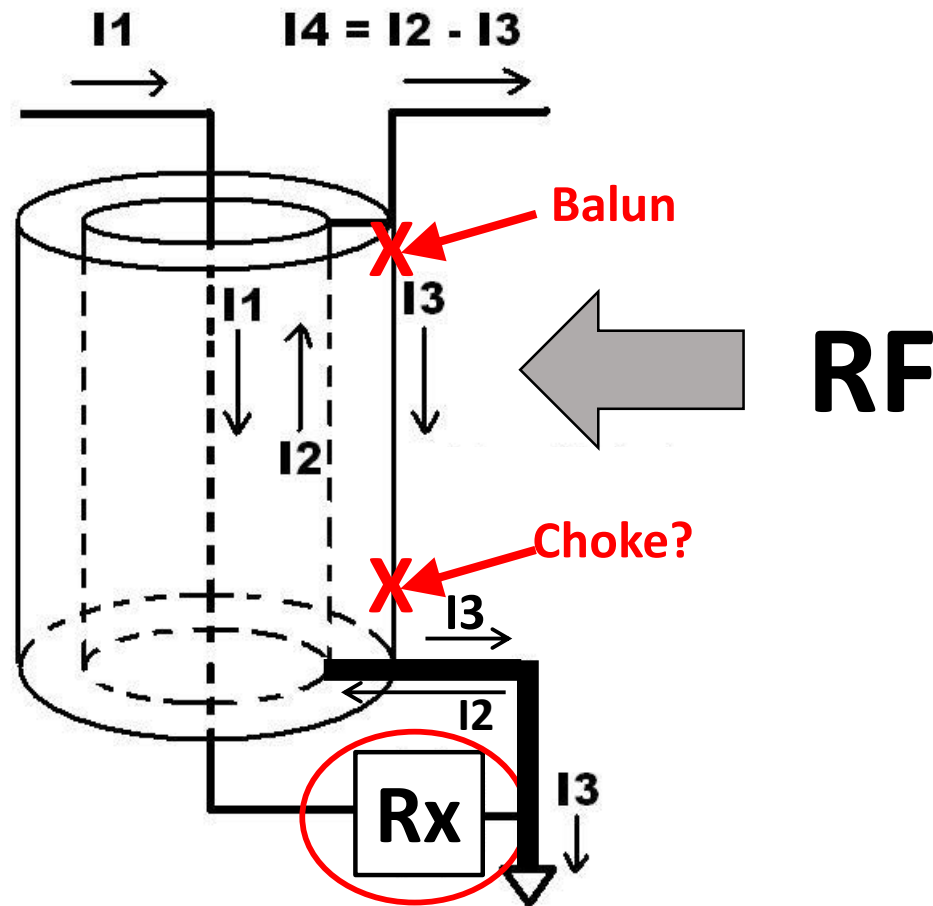
# Common Mode Currents Can Be Generated By External RF



- A Balun also reduces Common Mode current due to external RF fields
  - Some claim 1 to 5 S unit noise reduction
- Some claim that an additional Current Choke is required at the station to:
  - Reduce interference in the receiver => ??
    - **No documentation found showing when this is a problem**
  - Reduce Common Mode Currents caused by asymmetrical coupling to the line
    - **No documentation found showing when this is a problem**

# Where Should Baluns/Chokes Be Placed

- Start with a Balun at the antenna
- A Common Mode Choke at the transmitter?
  - No analytical or empirical justification found
- Common Mode Chokes as “Egg Insulators” every  $\frac{1}{4}$  wavelength?
  - No analytical or empirical justification found
- Use many chokes in series to increase net impedance (ie, CMMR)?
  - ***Point of diminishing returns***
    - Example:  $Z_{\text{choke}} = 10,000 \text{ Kohm}$  &  $Z_{\text{CM}} = 100 \text{ ohm}$   
**CMMR**
      - 1<sup>st</sup> choke => 40 dB
      - 2<sup>nd</sup> choke => 46 dB
      - 3<sup>rd</sup> choke => 50 dB



# Overheating

- Two Sources with Transmission Line Transformers (TLTs):
  1. Coaxial Transmission Line loss
    - Power spec based upon open-air applications (not enclosed in a box)
    - Deformation (coiled & hot) => degraded performance => failure (high SWR or short)
      - Minimum bend radius
      - This is what balun mfg's power specs are based on
  2. Core loss
    - Voltage Balun: both Common Mode and Differential Mode currents heat the core
    - Current Balun: only the Common Mode current heats the core
    - Heating increases with increasing permeability (ie, core loss)
    - ***This power limit is never spec'd by mfgs and is usually the important limitation***
    - Two sources of overheating:
      - From resonance with a reactive choke
      - With a resistive choke with insufficient resistance

## Overheating –cont'd

- Difficult to remove heat from a small enclosed box & and from ferrites
  - No air flow
  - No heat sinking options
  - Low thermal conductivity of ferrites & powdered iron

# Power Dissipation – Jack Lau W1VT

## Worst Case Example: using an 80 M dipole on 20 M

A high-impedance antenna and a low-impedance path shield. The applied power is 1-kW at 14.0 MHz.

Balun $Z_{CM}$	Shield Current (A)	Balun Loss (W)	(dB)
1000 $\Omega$	0.5	253	1.3
2000 $\Omega$	0.3	211	1.0
4000 $\Omega$	0.2	144	0.7
10000 $\Omega$	0.08	72	0.3
20000 $\Omega$	0.04	39	0.2

W2DU bead balun

1300  $-j400$  0.44 258 1.3

6t RG-213  
4-1/4" dia  
6 +  $j514$

0.74 3 0.01

12t RG-213  
4-1/4" dia  
449 +  $j5833$

0.14 9 0.04

12t RG-213  
@ 7.00MHz  
5 +  $j561$


0.72 2.6 0.01

12t RG-213  
@ 28.00MHz  
30  $-j482$

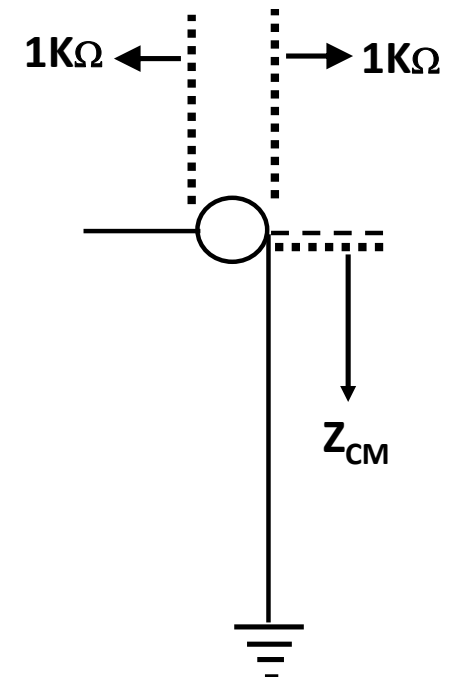1.34 54 0.2

Jan/Feb 2004 QEX:

Max Power Dissipation for 2" core ~ **4 Watts**




# Power Dissipation – Jack Lau W1VT

## Worst Case Example: using an 80 M dipole on 20 M


**Note: Even well balanced antennas can have high Common Mode currents!  
This fact is missed by many “Experts”.**

1000 $\Omega$	0.5	253	1.3
2000 $\Omega$	0.3	211	1.0
4000 $\Omega$	0.2	144	0.7
10000 $\Omega$	0.08	72	0.3
20000 $\Omega$	0.04	39	0.2
W2DU bead balun			
1300 $-j400$	0.44	258	1.3
6t RG-213 4-1/4" dia 6 + $j514$			
	0.74	3	0.01
12t RG-213 4-1/4" dia 449 + $j5833$			
	0.14	9	0.04
12t RG-213 @ 7.00MHz 5 + $j561$			
	0.72	2.6	0.01
12t RG-213 @ 28.00MHz 30 $-j482$			
	1.34	54	0.2

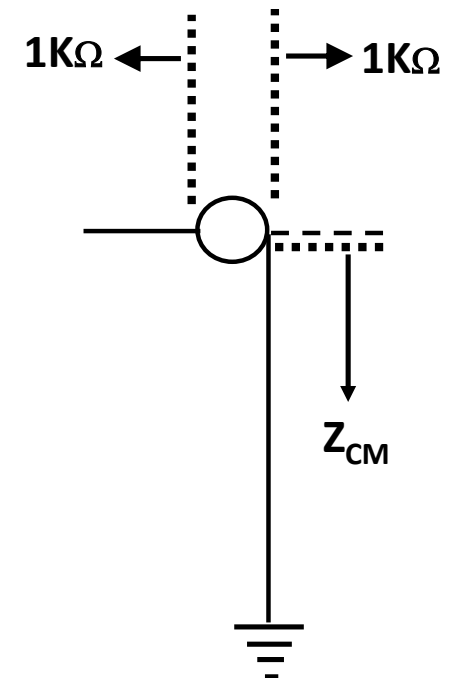
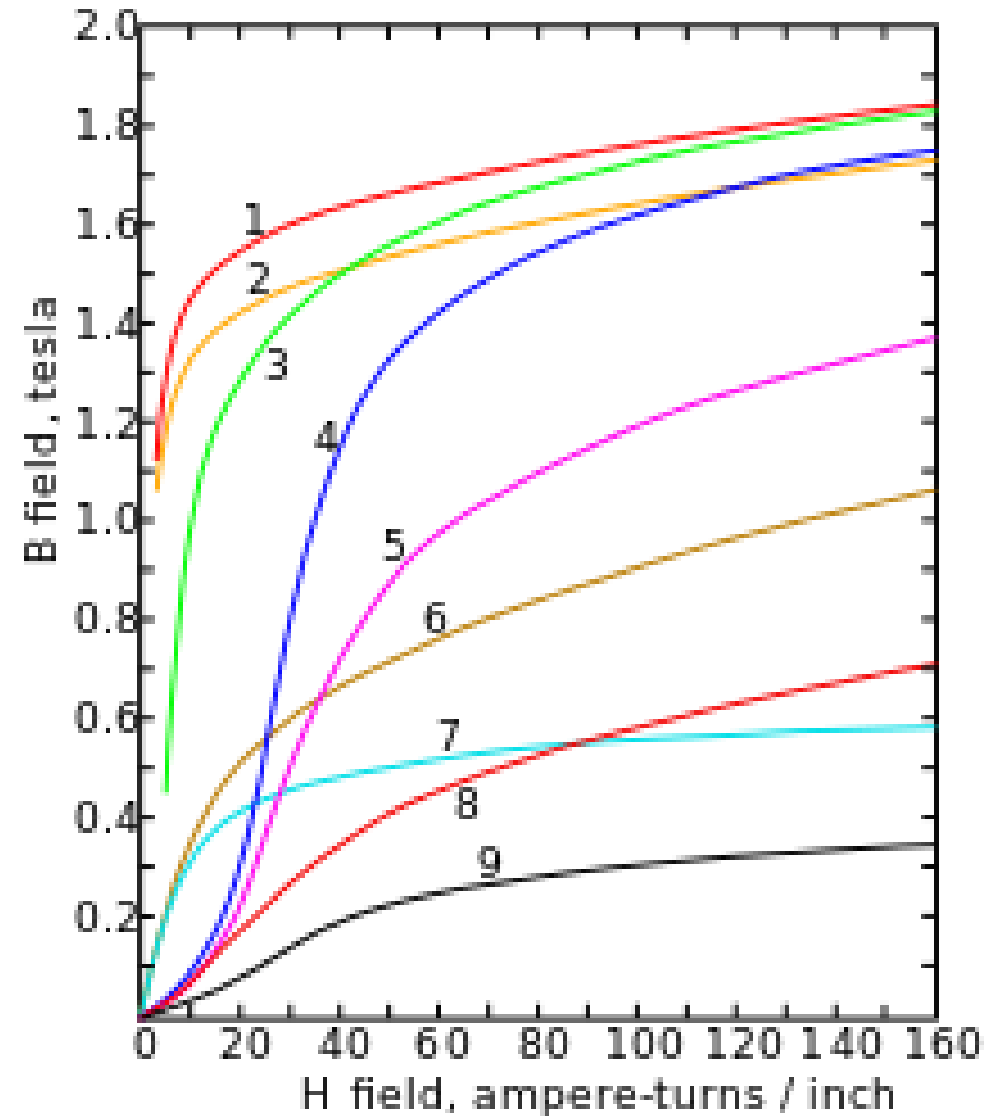
# Intermodulation Distortion

- Ferrites are non-linear components
  - They can generate IMD just like an overdriven amplifier
  - Hard to know when this is occurring
- **Avoid operating near saturation!**
  - **Thermal run-away**



# Building Current Baluns & Chokes

# Types of Common Mode Current Chokes


- Inductively Coupled Air Core Coils
  - Rarely used today
- Powdered iron
- Ferrite
- Ferrite Sleeved Coax Baluns
- Coiled Coax “Ugly” Baluns
- Transmission Line Transformer (TLT) Baluns

# Design Goals for Common Mode Current Chokes

- High Common Mode impedance
  - At least 500 ohms (>5 Kohms recommended)
  - Resistive vs Reactive?
    - Resistive is better if you can get the impedance high enough (ie, no overheating)
- Low Differential Mode SWR & loss
- Adequate power limits
  - Differential Mode (easy)
  - Common Mode (difficult design problem)
- Desired frequency range
- Optimized bandwidth
  - Wideband vs. narrowband
- Optimized SRF



# How Common Mode Current Chokes Work

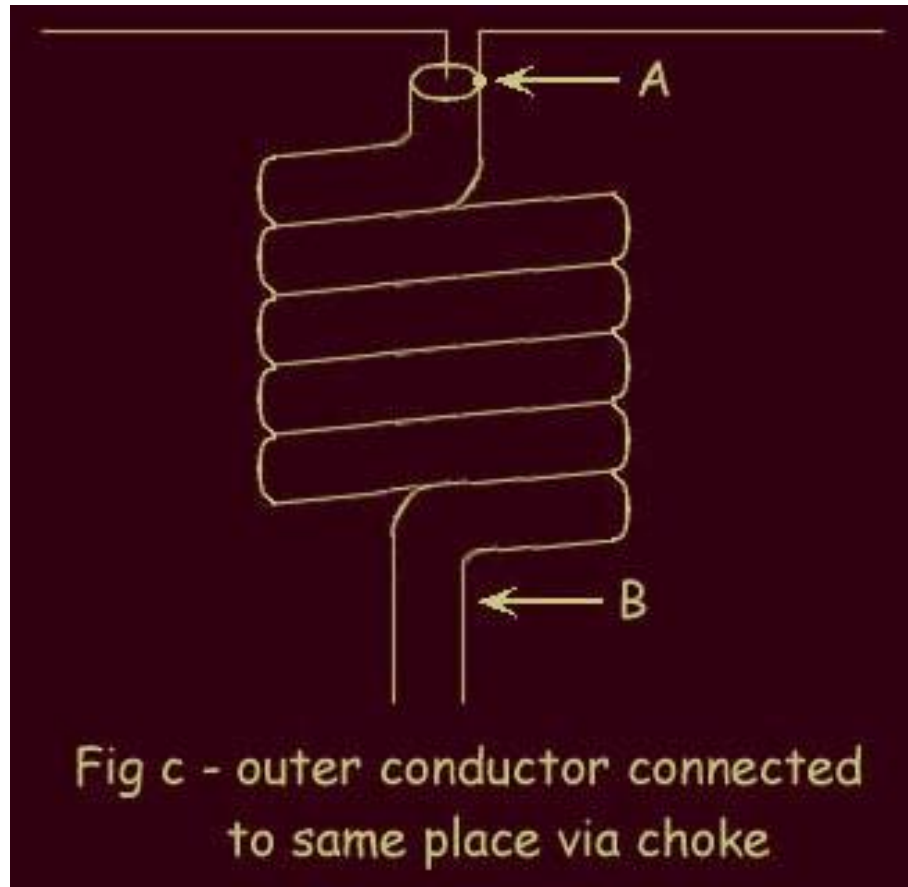


- Differential Mode signal only sees the coax
  - Coiling the coax has no effect
  - Typical:
    - SWR < 1.1:1
    - Loss < 0.1 dB
    - Bandwidth (depends on coax)
- Common Mode signal only sees the choke
- Common Mode impedance is a function of:
  - Number of turns
  - Coil dimensions
  - Frequency
  - Core media (ferrite, air, ...)


# Choke Impedance Performance Claims

- ***Be careful!***
- Some charts of performance can be misleading

## 6.8 uH Choke #1

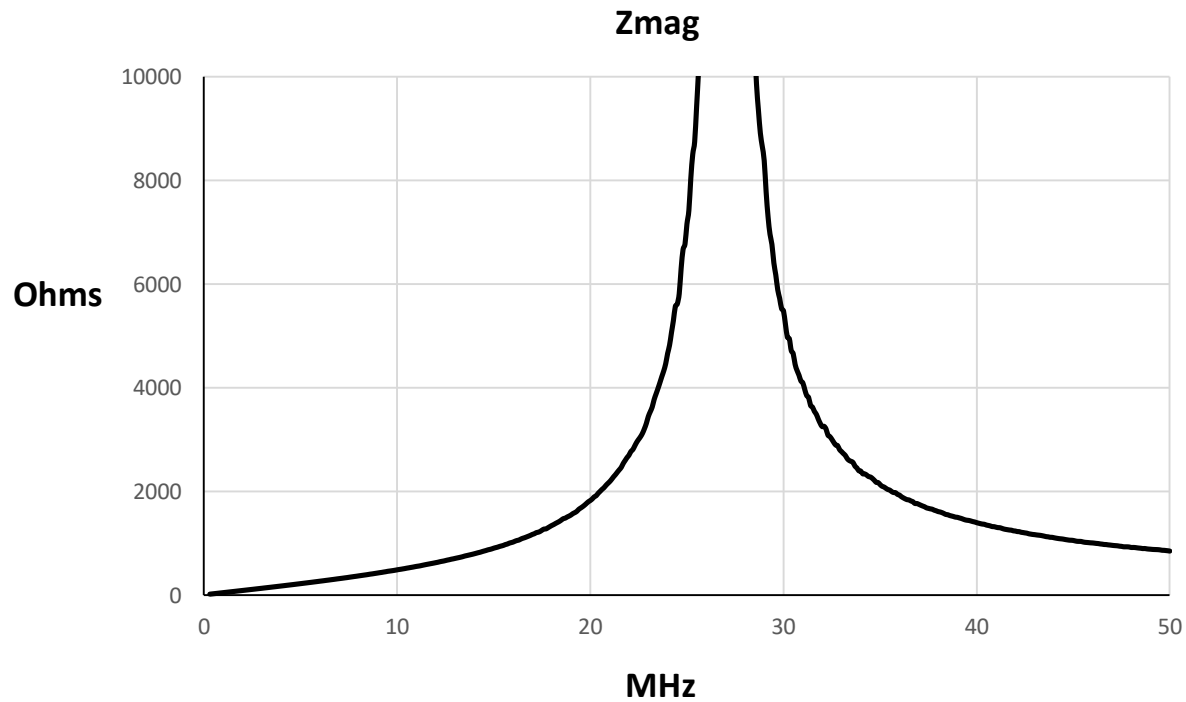

## 6.8 uH Choke #2

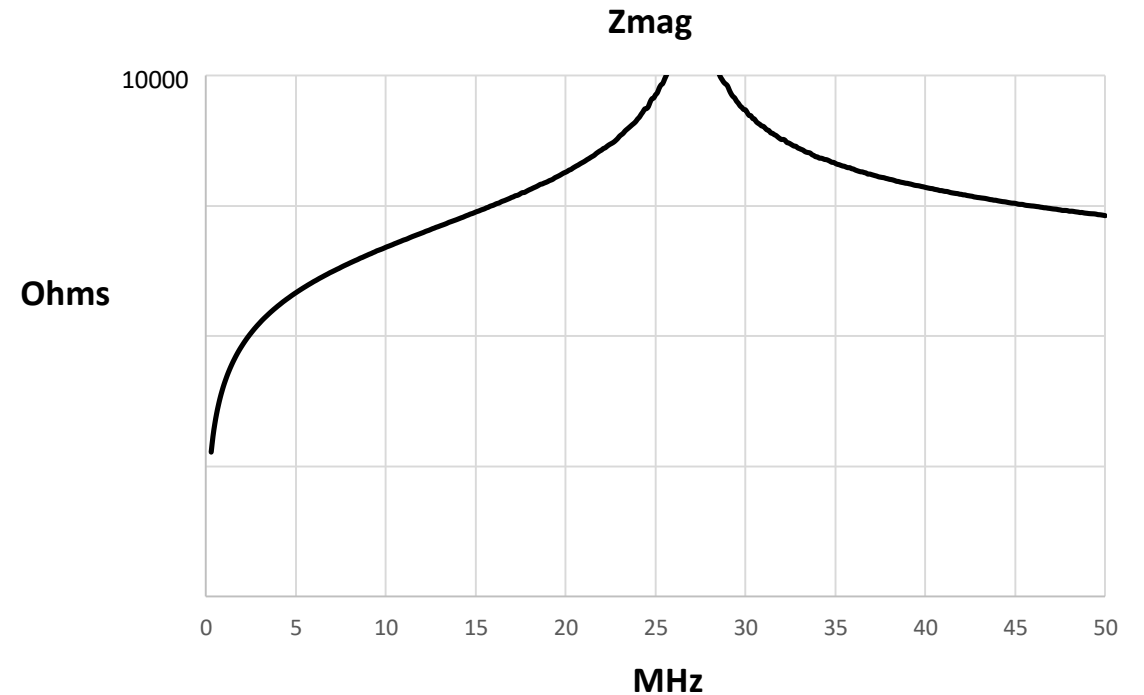


# Choke Impedance Performance Claims


- Be careful
- Some Charts of performance can be misleading

Same 6.8  $\mu\text{H}$  Choke

**Linear**

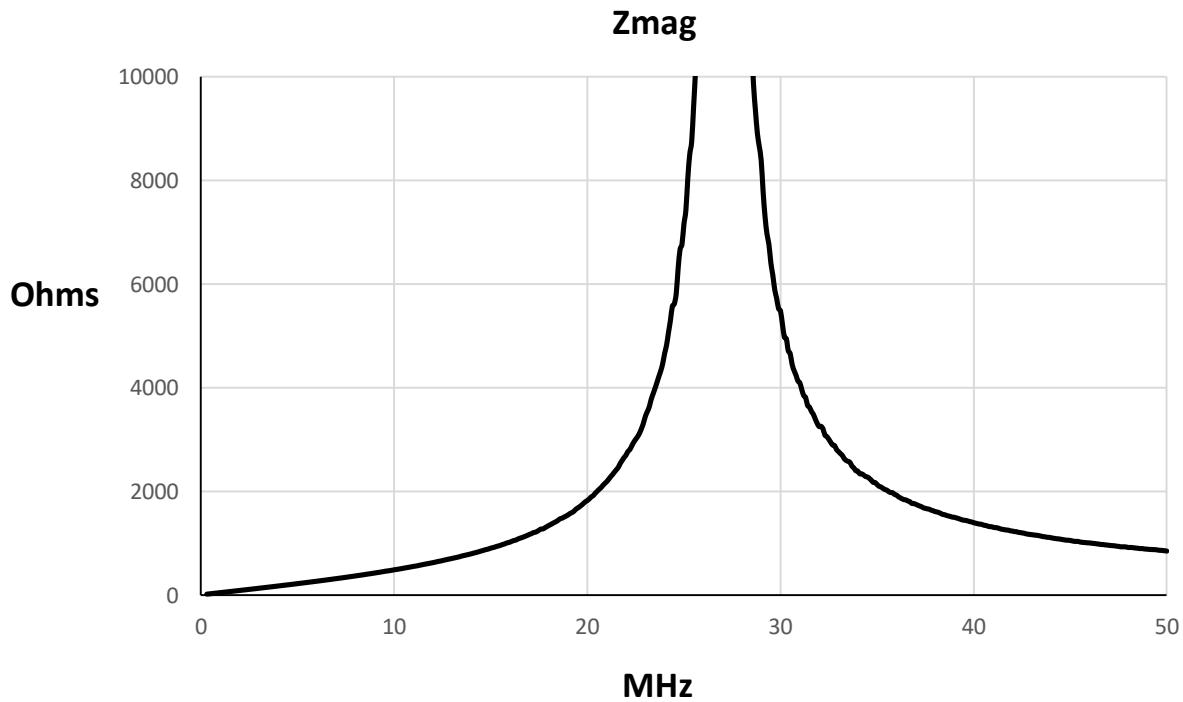

**Log**

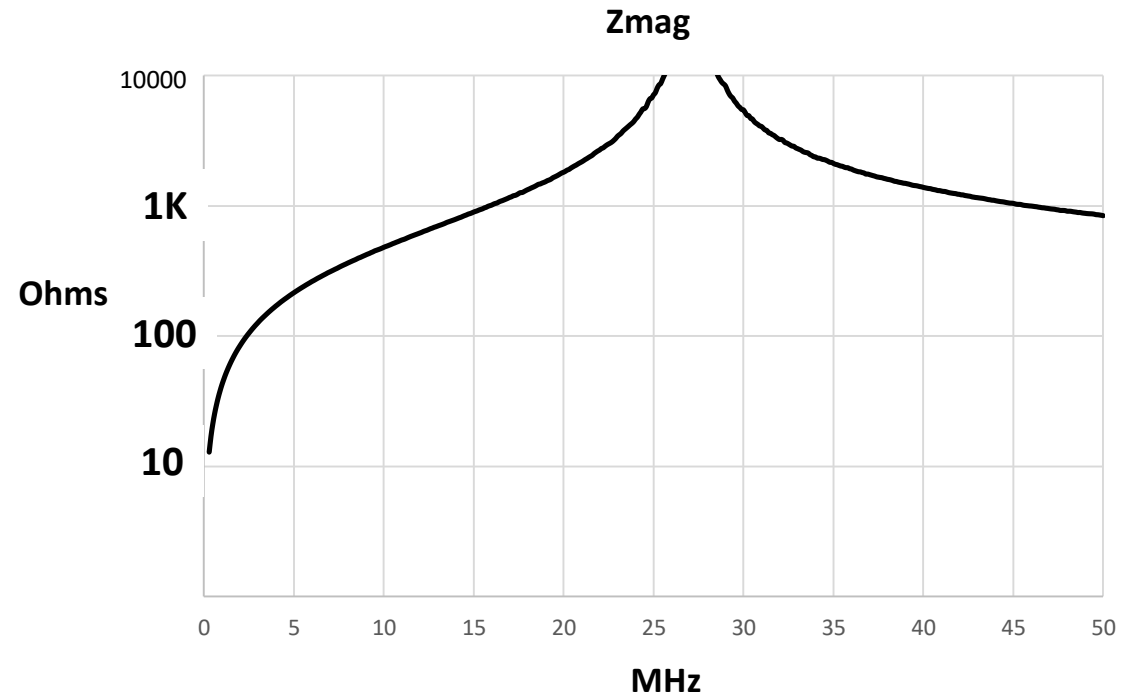


# Powdered Iron

- Low permeability =  $\mu$  = how much inductance per turn)
  - Very low loss (ie, hi Q = narrowband)
    - Less heating of the core
    - Impedance is mostly inductive reactance
  - Very low Z/turn
- Rarely used for Baluns/Chokes
  - Commonly used for high Q inductors
- Example:
  - To get  $\sim 20$   $\mu\text{H}$  on T50-6 ( $\mu=8$ ) requires  $\sim 50$  turns
    - No way to get this many turns of coax around even the largest core available
    - Ferrite cores would only require 4-6 turns
  - Impedance at 10 MHz:
    - Resistance: only 45 ohms
    - Inductive reactance: 1300 ohms

# Ferrites

- Wide range of permeability ( $\mu$ )
  - Mix:
    - “31”:  $\mu=1500$  “33”:  $\mu=600$  “43”:  $\mu=800$  “61”:  $\mu=125$  “77”:  $\mu=2000$
- Impedance examples ( 10 turns around a 2.4 inch core):

## Type 43

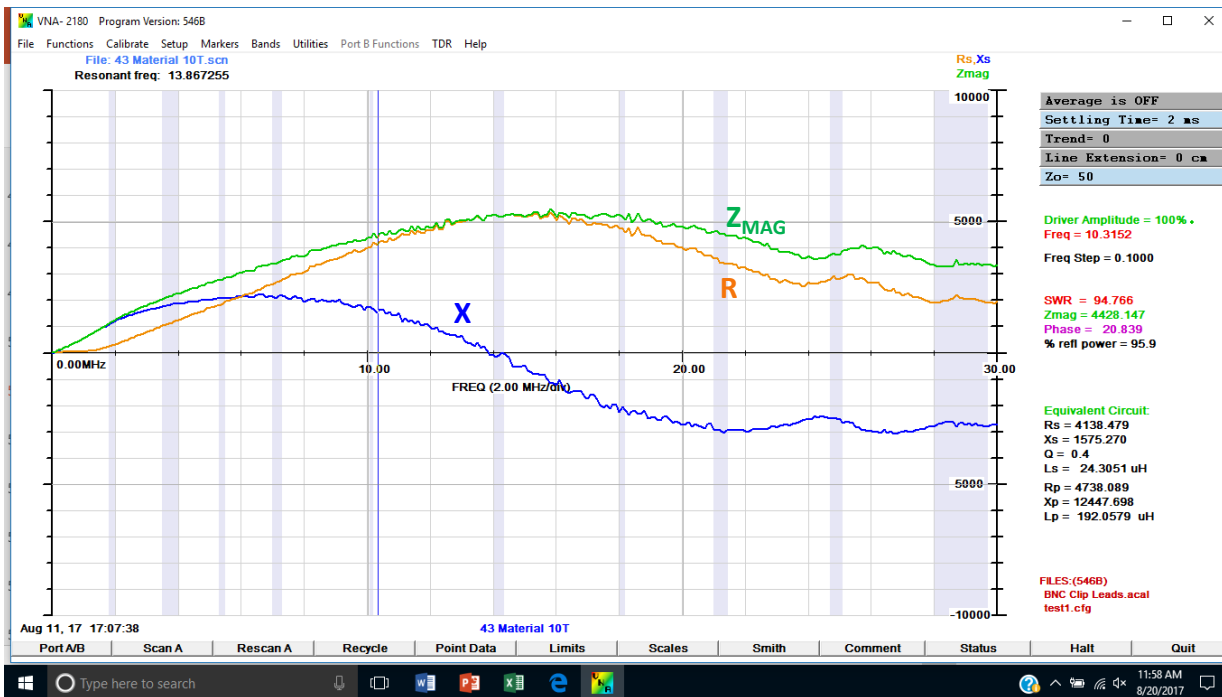

## Type 61



# Ferrite Sleeved Current Chokes


- Ferrite beads over coax
  - These chokes are 1:1 UNUNs
- Mostly resistive impedance
  - No system resonance risk
  - Low Q (wideband)
  - Difficult to achieve sufficient choking impedance
    - No  $n^2$  multiplier as with coils
    - May need to use more than 100 beads
  - **History of failures from overheating**
    - “W2DU design overheats at 500W”
- Simple to build but not necessarily cheap
  - Comtek uses 100 beads (\$130 )



# Ferrite Sleeved Current Chokes – cont'd

- Homebrew Sleeved choke performance
  - Max Impedance < 800 ohms
  - Mostly resistive

SWR < 1.08:1

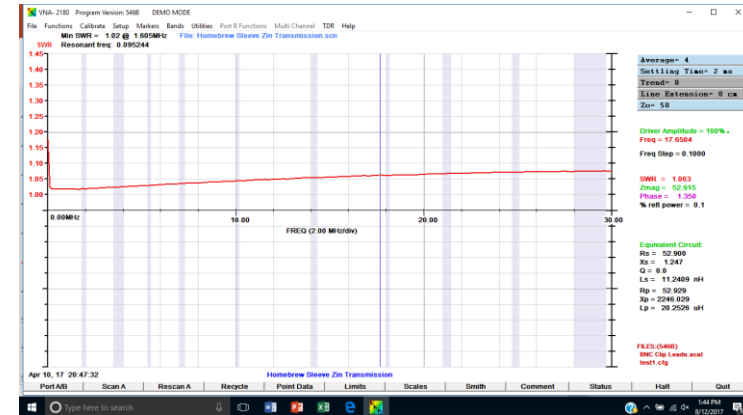

Loss < 0.05 dB




# Coiled Coax “Ugly” Baluns

- Two basic types
  - Single layer
  - Bunched
    - Performance not as good as single layer
- Both types can achieve high impedance
  - Very high Q
    - Very small R and large X
    - Very narrow band
    - **SRF very sensitive to build parameters**
    - **System resonance can be a serious problem**
- Large and heavy
- Best “Bang for the Buck”




Coax Air Core Single Layer Chokes

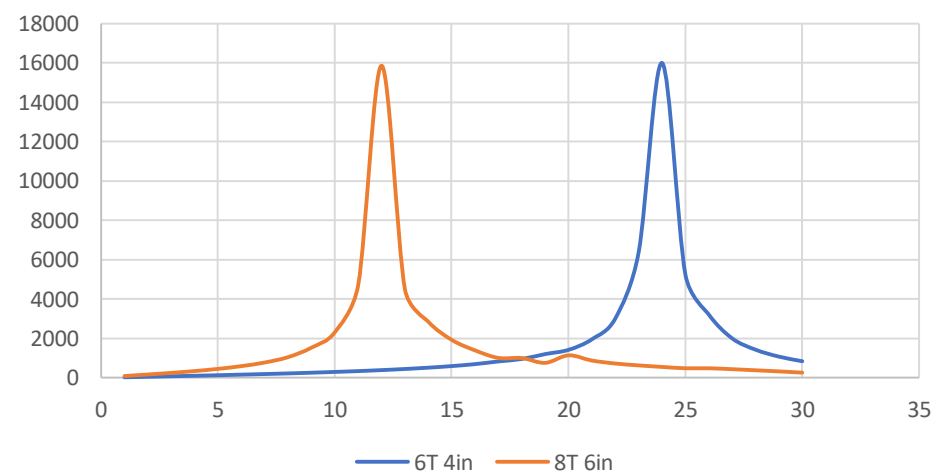


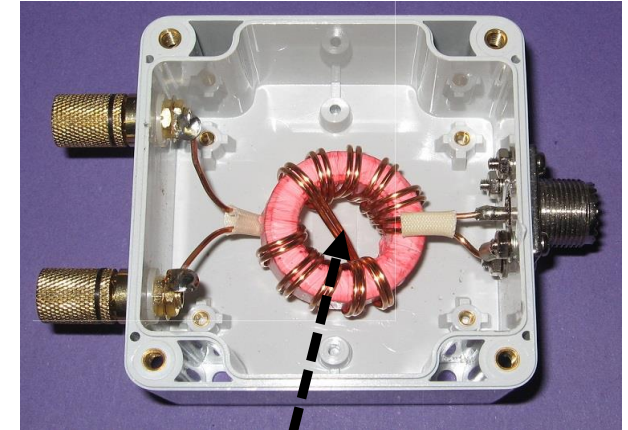
# Transmission Line Transformer (TLT) Baluns

- Most common method of building Current Baluns & Chokes
- The transmission line can be coax or bifilar (parallel) wires
  - Line impedance is important for best performance
  - Line length  $\ll \frac{1}{4}$  wavelength
  - Chose the line based upon impedance & power reqm'ts
- Use of coax yields very low SWR & insertion loss
- Only the Common Mode Current magnetizes the ferrite core
  - Minimizes Differential signa loss & core heating
- Choking Bandwidth:
  - Lowest useable freq: set by the inductance of the coil
    - More inductance lowers bottom cutoff frequency
    - More inductance requires more turns and/or higher permeability ferrite
  - Highest useable freq: set by **Self Resonant Frequency (SRF)** of the coil
    - More turns lowers upper frequency cutoff



Crossover done for layout,  
not performance reasons

# High Power Coax Chokes


- For high power applications



**"MOAB"**
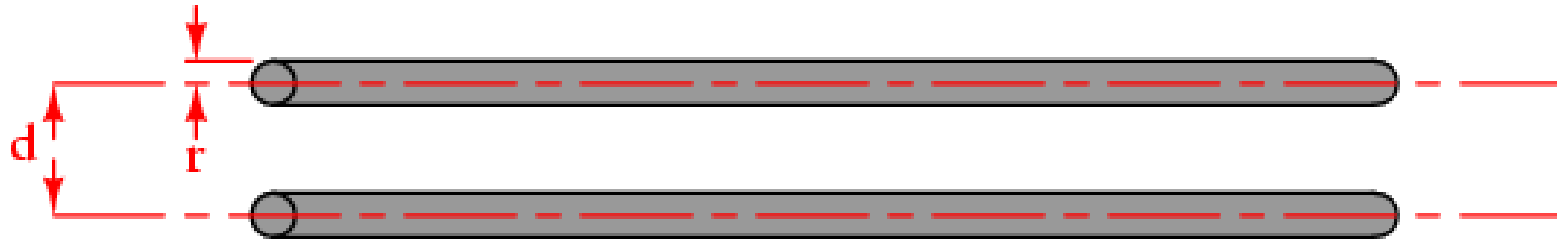
# Parallel Wire Transmission Line Impedance

- Optimal line impedance is determined by input & output impedances
  - Ex: a 50 to 200 ohm Balun requires a 100 ohm line



$$Z_0 = \frac{276}{\sqrt{k}} \log \frac{d}{r}$$

Where,

$Z_0$  = Characteristic impedance of line

$d$  = Distance between conductor centers

$r$  = Conductor radius


$k$  = Relative permittivity of insulation  
between conductors

# Design Tradeoffs


- Most Balun/Choke designs don't provide both high Z and wide bandwidth
- Ferrite material
  - High Mu (61 & 77)
    - High loss
    - Narrow BW
    - High Z/turn
  - Low Mu (33 & 43)
    - Low loss
    - Wider BW
    - Low Z/turn
    - Frequent choice for HF Baluns/Chokes
- Power dissipation
  - For Current Baluns, Common Mode power is the critical spec
  - Single 2.4 in ferrite core may only be good for 5-10 watts of dissipation
  - Use stacked cores for more power dissipation

# Examples: Common Mode Chokes


## DX Engineering DXE-FCC050-H05-B

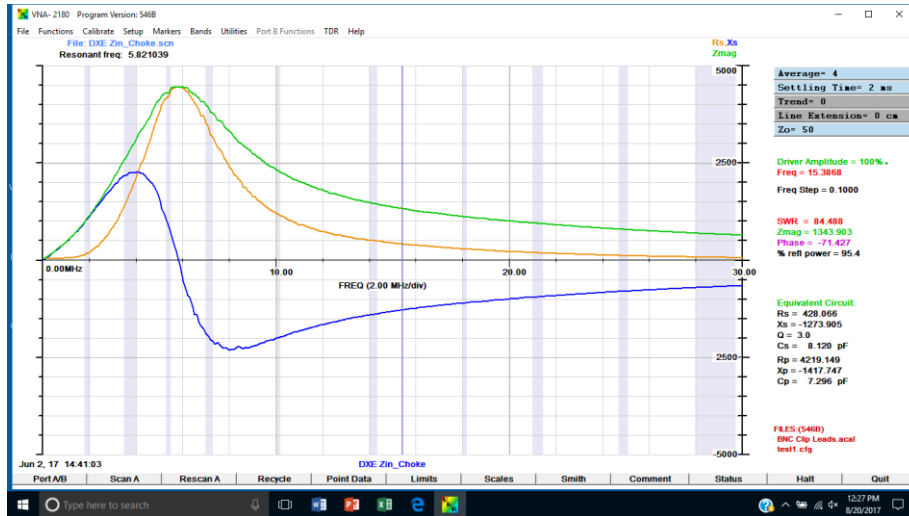

## Homebrew Toroidal Choke

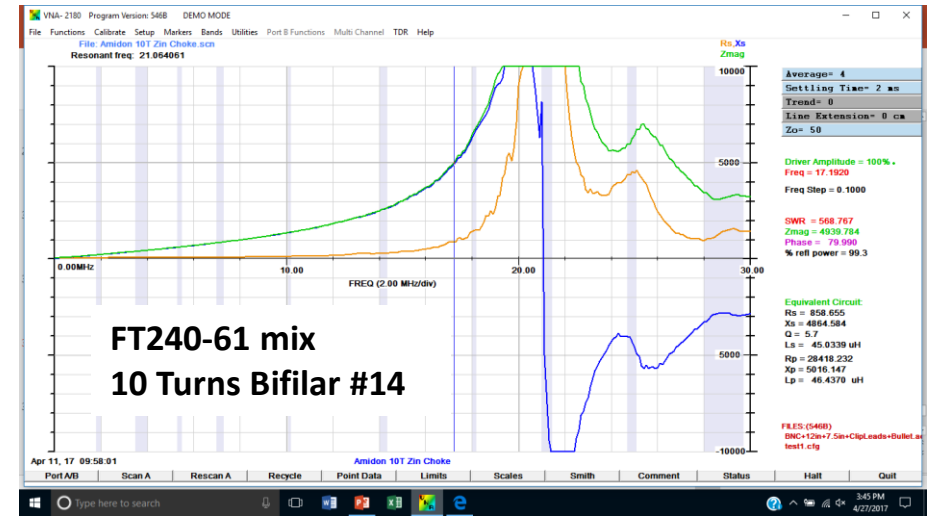


## Homebrew Toroidal Choke

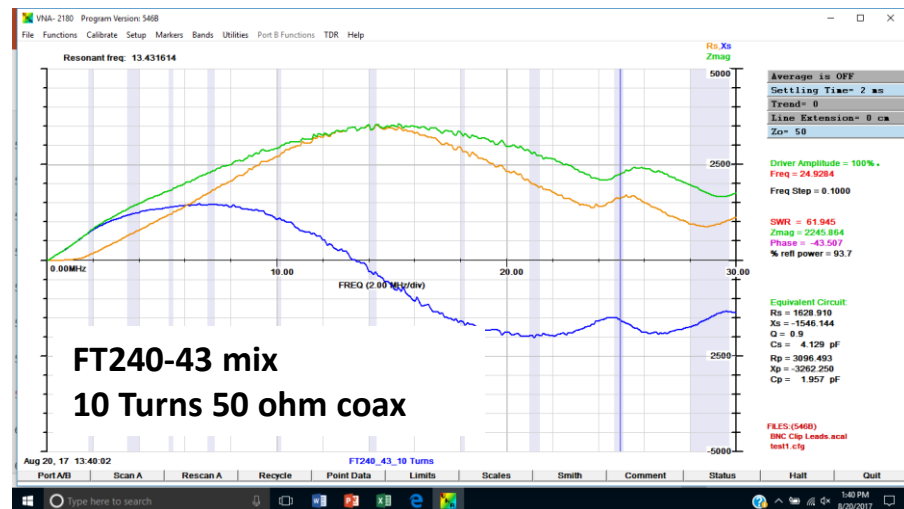

## FT240-43 mix vs 61 mix



# Examples: Common Mode Chokes

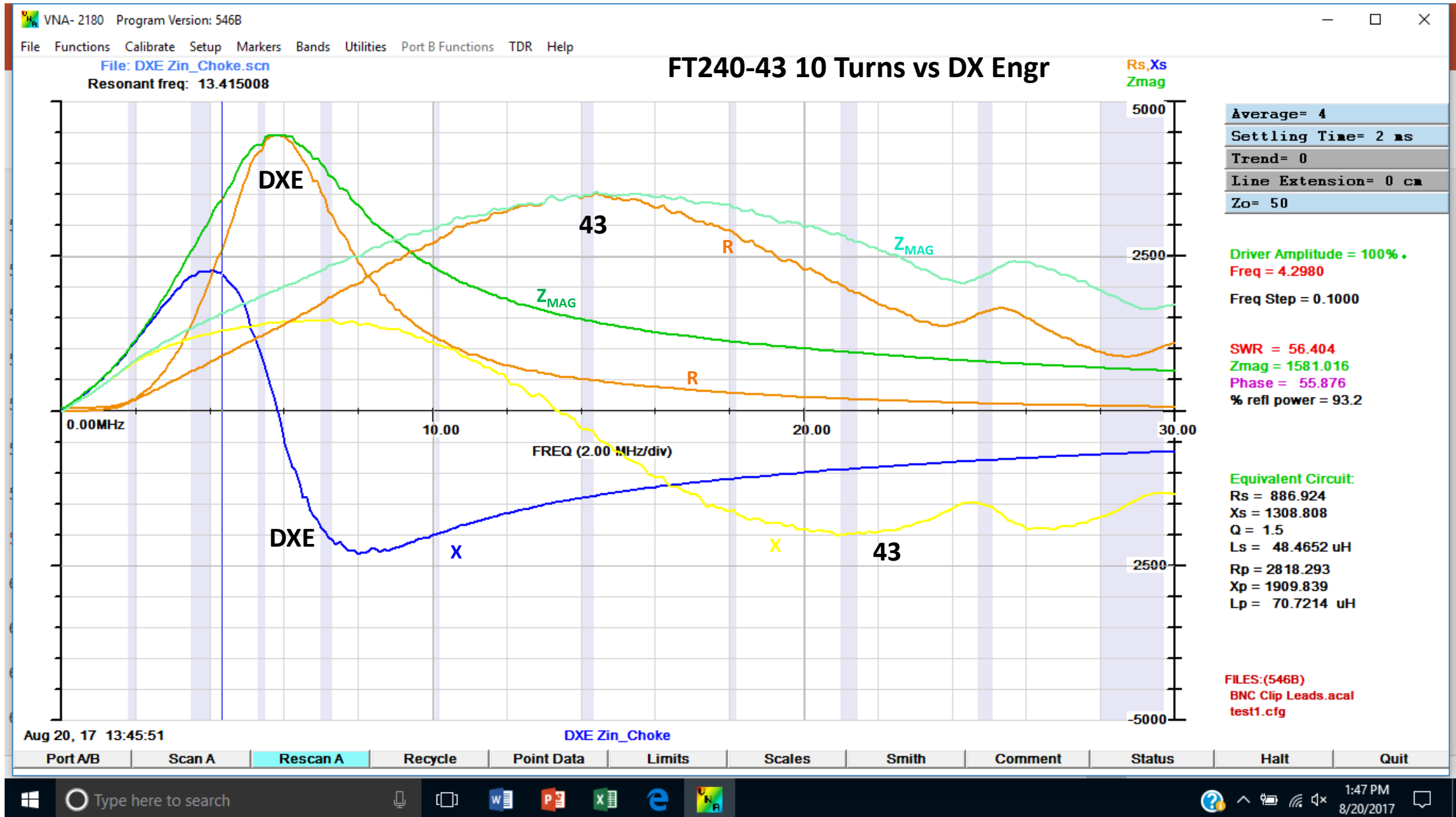

# Ferrite & Powdered Iron (Iron Powder) Suppliers

- Amidon
  - Wide variety of products
  - Recently changed ownership
    - Used to have a good info sheet (=>?)
    - Used to have a minimum order requirement
  - Balun kits
    - Kit with handbook for extra \$ => handbook is available free on the Internet
- Fair-Rite
  - Producer of ferrite & powdered iron products
    - Not a good source for “how to build ....” info (ie, don’t call for help)
  - Evaluation (not balun or transformer) kits
  - Distributors (Mouser, ...)
- Other Distributors: Palomar-Engineers, Radioworks, KF7P, ...
  - May not be cost effective for some orders


# Example: Using the Amidon Spec Sheet

What type core do I have?

- 1) Wrap 10 turns around core
- 2) Measure inductance at a frequency well below resonance (4.3 MHz):

$$L = 16.4 \mu\text{H} = 0.0164 \text{ mH}$$

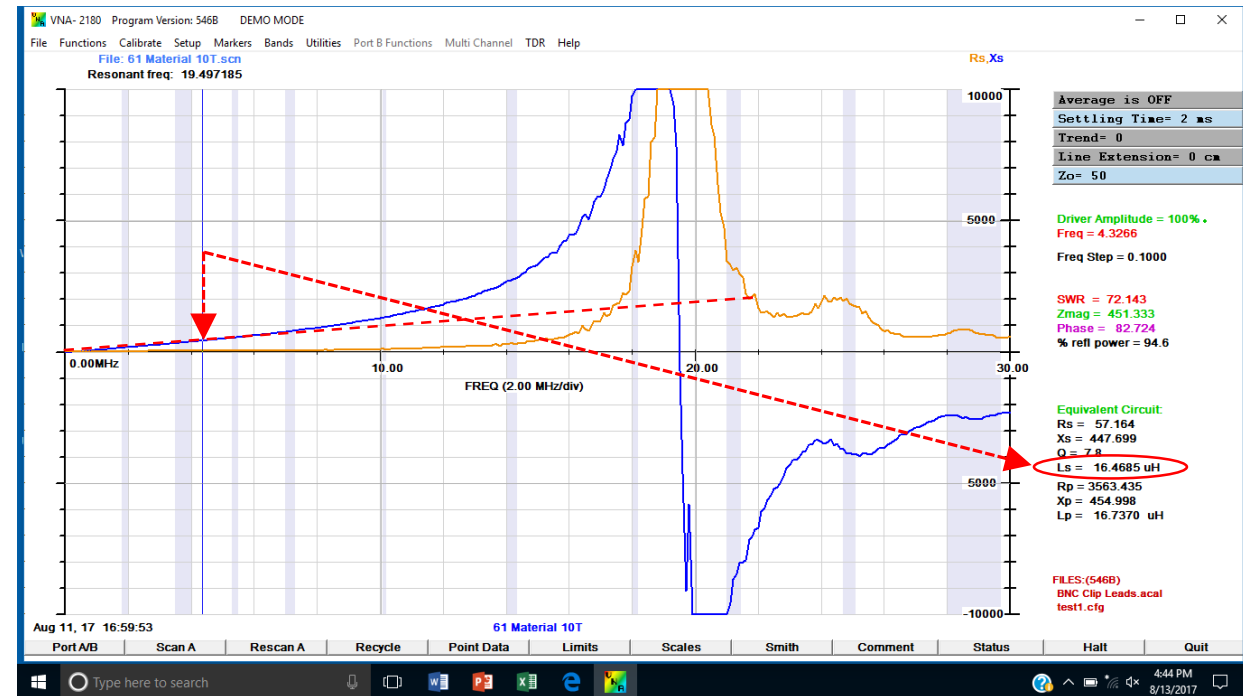- 3) Calculate  $A_L = \text{mH}/1000 \text{ turns}$   
 $= \text{mH}/10 \text{ turns} \times (n_{\text{RATIO}})^2$   
 $= \text{mH}/10 \text{ turns} \times 10,000$   
 $= 0.0164 \times 10,000$   
 $= 164 \text{ mH}/1000 \text{ turns}$





# Example: Using the Amidon Spec Sheet – cont'd

## FERRITE TOROIDAL CORES

MATERIAL 43								Permeability 800
Core number	O.D. (inches)	I.D. (inches)	Hgt. (inches)	$\epsilon_r$ (cm)	$A_e$ (cm) <sup>2</sup>	$V_e$ (cm) <sup>3</sup>	$A_L$ Value mh/1000 turns	
FT-23 -43	.230	.120	.060	1.30	.020	.027	158	
FT-37 -43	.375	.187	.125	2.07	.072	.150	350	
FT-50 -43	.500	.281	.188	2.95	.129	.380	440	
FT-50A -43	.500	.312	.250	3.12	.150	.470	480	
FT-50B -43	.500	.312	.500	3.12	.299	.930	965	
FT-82 -43	.825	.520	.250	5.20	.243	1.260	470	
FT-114 -43	1.142	.748	.295	7.30	.370	2.700	510	
FT-140 -43	1.400	.900	.500	8.90	.790	7.000	885	
FT-240 -43	2.400	1.400	.500	14.50	1.580	22.800	1075	

- On a mfg spec sheet, find the  $A_L$  that is closest to your measured value
- Core is 2.4 in diameter => Material = 61 (Actual  $A_L$  values can vary +/- 25%)

MATERIAL 61								Permeability 125
Core number	O.D. (inches)	I.D. (inches)	Hgt. (inches)	$\epsilon_r$ (cm)	$A_e$ (cm) <sup>2</sup>	$V_e$ (cm) <sup>3</sup>	$A_L$ Value mh/1000 turns	
FT-23 -61	.230	.120	.060	1.34	.020	.029	24.8	
FT-37 -61	.375	.187	.125	2.15	.076	.163	55.3	
FT-50 -61	.500	.281	.188	3.02	.133	.401	69.0	
FT-50A -61	.500	.312	.250	3.68	.152	.559	75.0	
FT-50B -61	.500	.312	.500	3.18	.303	.963	150.0	
FT-82 -61	.825	.516	.250	5.26	.246	1.290	75.0	
FT-114 -61	1.142	.750	.295	7.42	.375	2.790	80.0	
FT-114A -61	1.142	.750	.545	7.42	.690	5.130	145.0	
FT-140 -61	1.400	.900	.500	9.02	.806	7.280	145.0	
FT-240 -61	2.400	1.400	.500	14.80	1.610	23.900	171.0	

MATERIAL 67								Permeability 40
Core number	O.D. (inches)	I.D. (inches)	Hgt. (inches)	$\epsilon_r$ (cm)	$A_e$ (cm) <sup>2</sup>	$V_e$ (cm) <sup>3</sup>	$A_L$ Value mh/1000 turns	
FT-23 -67	.230	.120	.060	1.34	.021	.029	6.0 Min	
FT-37 -67	.375	.187	.125	2.15	.076	.163	18.0	
FT-50 -67	.500	.281	.188	3.02	.133	.401	22.0	
FT-50A -67	.500	.312	.250	3.68	.152	.559	24.0	
FT-50B -67	.500	.312	.500	3.18	.303	.963	48.0	
FT-82 -67	.825	.516	.250	5.26	.246	1.290	24.0	
FT-114 -67	1.142	.750	.295	7.42	.375	2.790	25.4	
FT-140 -67	1.400	.900	.500	9.02	.806	7.280	45.0	
FT-240 -67	2.400	1.400	.500	14.80	1.610	23.900	55.0	

MATERIAL 68								Permeability 20
Core number	O.D. (inches)	I.D. (inches)	Hgt. (inches)	$\epsilon_r$ (cm)	$A_e$ (cm) <sup>2</sup>	$V_e$ (cm) <sup>3</sup>	$A_L$ Value mh/1000 turns	
FT-23 -68	.230	.120	.060	1.34	.021	.029	4.0	
FT-37 -68	.375	.187	.125	2.15	.076	.163	8.8	
FT-50 -68	.500	.281	.188	3.02	.133	.401	11.0	
FT-50A -68	.500	.312	.250	3.68	.152	.559	12.0	
FT-82 -68	.825	.520	.250	5.26	.246	1.290	11.7	
FT-114 -68	1.142	.750	.295	7.42	.375	2.790	12.7	

# Conclusions

- When should a Balun/Choke be used
  - Answer1: When you suspect Common Mode Current is causing a problem
    - Not just because someone told you to use one
  - Answer2: With monoband antennas, try a different length of transmission line first
- What type of Balun/Choke should be used
  - Answers:
    - Usually a Current Balun/Choke
    - Voltage Baluns for high impedance antennas like end fed halfwaves
- Where should they be installed
  - Answer: Start with one at the antenna
- What should I observe after I install one
  - Answer: Problem gets better, gets worse, or doesn't change at all
- It is best to know the impedance vs frequency of a Balun/Choke before you use it
  - Some antenna analyzers don't have enough range (MFJ-259 limited to  $Z < 600$  ohms)