

# Transmission Lines As Impedance Transformers

Bill Leonard N0CU

285 TechConnect Radio Club

2017 TechFest

# Topics

- Review impedance basics
- Review Smith chart basics
- Demonstrate how antenna analyzers display impedance data
- Demonstrate some important transmission line characteristics

# Impedance

- Impedance (Z) is a measure of the opposition to current flow
  - Unit of measure = Ohm =  $\Omega$
- Impedance describes a series circuit
- Impedance has two components:
  - The DC component = Resistance = R (ohms)
  - The AC component = Reactance = X (ohms)

## Inductive Reactance

$$X_L \text{ (ohms)} = + j2\pi fL$$

$$\text{Phase} = + 90^\circ$$

(Voltage leads current)

## Capacitive Reactance


$$X_C \text{ (ohms)} = - j[1/(2\pi fC)]$$

$$\text{Phase} = - 90^\circ$$


(Voltage lags current)

## Impedance – cont'd

- Impedance can be expressed in two ways:
  1. **Resistance** and **reactance**  $\Rightarrow \mathbf{Z} = \mathbf{R} + \mathbf{jX}$  (Complex Number)
  2. **Magnitude** and **phase**  $\Rightarrow \mathbf{Z} = |\mathbf{Z}| \angle \theta$ 
    - Magnitude of Z (ohms)  $= |\mathbf{Z}| = \sqrt{R^2 + X^2}$
    - Phase of impedance (degrees)  $= \theta = \arctan(X/R)$

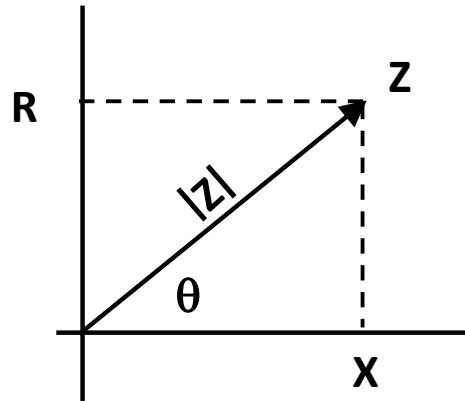

# Impedance of a Series Circuit



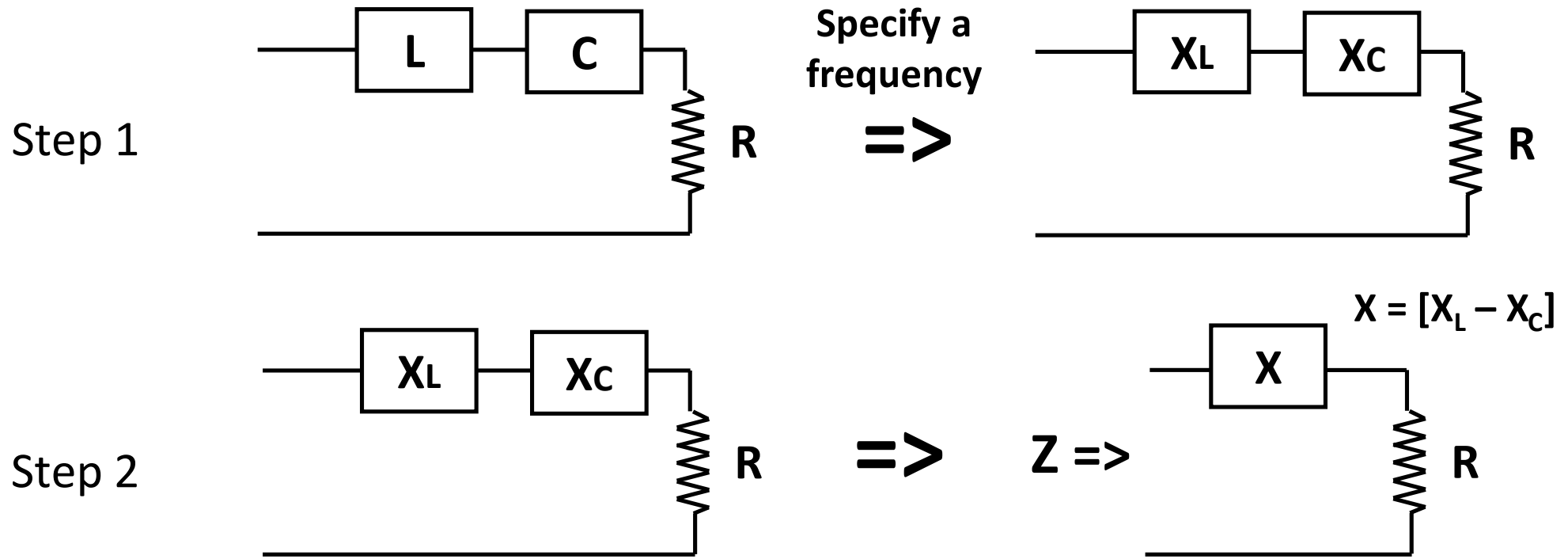


1.  $Z = R + j X = R + j(X_L - X_C) = R + j[(2\pi fL - 1/(2\pi fC))]$
2.  $Z = |Z|$  and  $\angle\theta$

# Impedance of a Parallel Circuit

- Z is defined only for a series circuit
  - Must convert a parallel circuit to a series circuit
    - Frequency must be known to do the conversion
    - Both component values change when converted

$$Z \neq R_p + jX_p$$
$$= ?$$

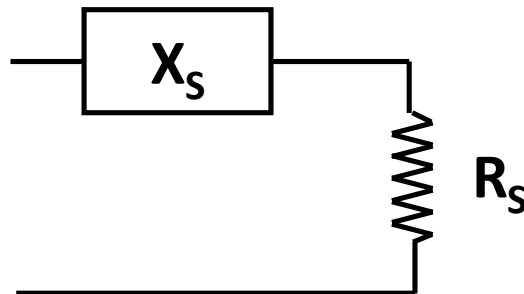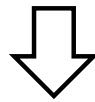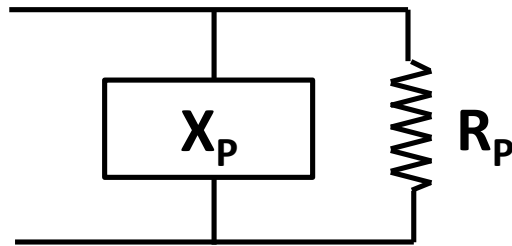


$$Z = R_s + j X_s$$

$$R_s = \frac{R_p \times X_p^2}{R_p^2 + X_p^2}$$

$$X_s = \frac{R_p^2 \times X_p}{R_p^2 + X_p^2}$$

# Example 1: Impedance at 2 MHz

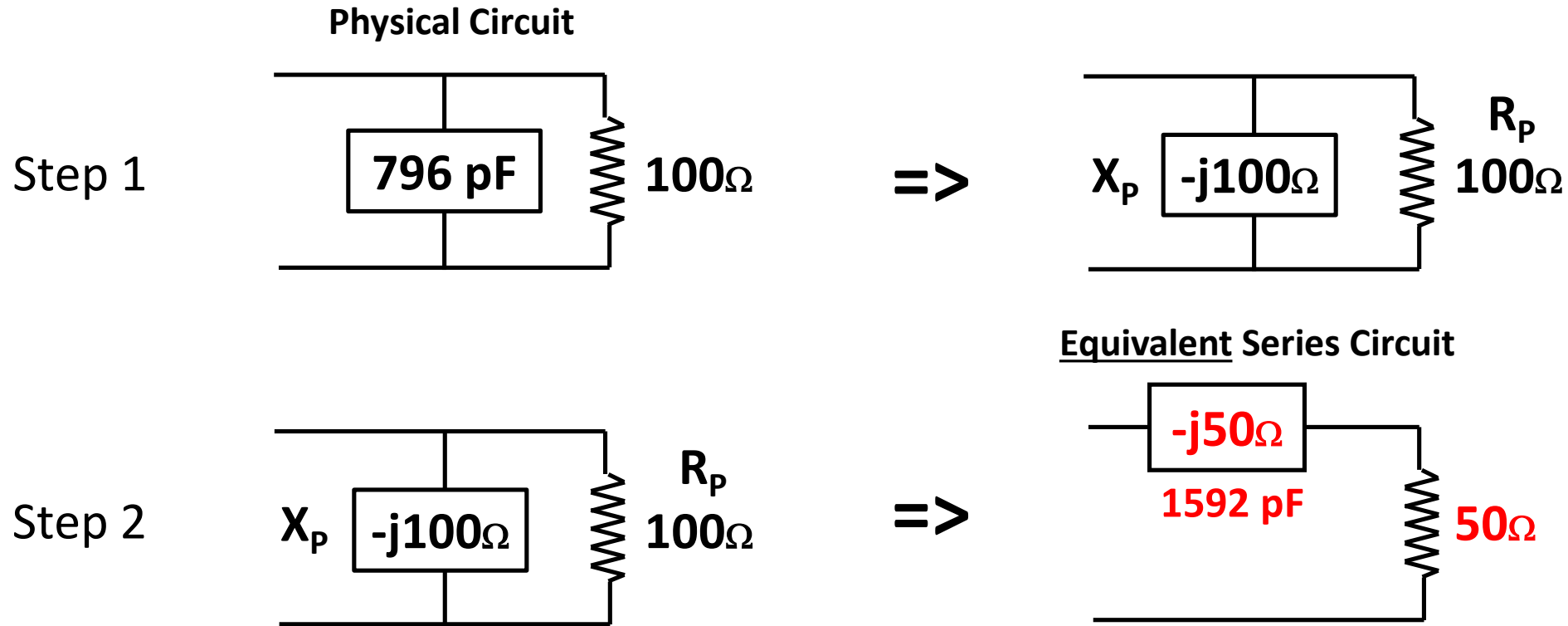


Note: Two different circuits have the same impedance at 2 MHz:

$$Z = 50\Omega - j50\Omega = 70.7\Omega @ -45^\circ$$

# Example 1: Impedance at 2 MHz - cont'd

- What an MFJ-259B measured at 2 MHz:

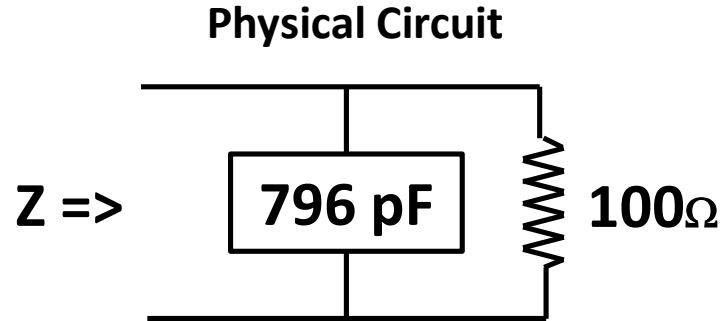


	<u>Calculated</u>	<u>Measured</u>
$R_s =$	50 Ω	56 Ω
$X_s =$	-50 Ω	48 Ω
$ Z  =$	70 Ω	74 Ω
Phase =	-45°	40°
SWR =	2.6	2.4
"Impedance" Meter =	70	70 => $ Z $

**Note: The MFJ-259B does not display  $R_p$ ,  $X_p$ , or the sign of a reactance**


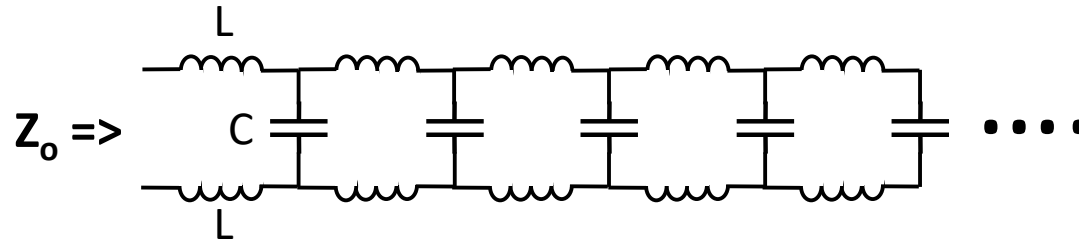
# Transmission Lines Are Lowpass Filters

- “Lumped element” circuit approximation for lossless transmission line:



- $Z_o$  is called the “Surge Impedance” or “Characteristic Impedance” of the line
  - When  $Z_{LOAD} = Z_o$ 
    - The line is “Matched”
    - The input impedance of a transmission line equals  $Z_o$  and is independent of length
  - $Z_o \approx \sqrt{L/C}$
  - Example: Belden RG-58/U (9201)

$$Z_o = 52\Omega$$

$$C = 27 \text{ pF/ft}$$


$$L = 94 \text{ nH/ft}$$

$$VP = 0.66$$


# When $Z_{LOAD} \neq Z_0$

Input impedance of a 50 ohm line when the SWR = 2.0:

$R_{LOAD} = 100 \text{ ohm}$

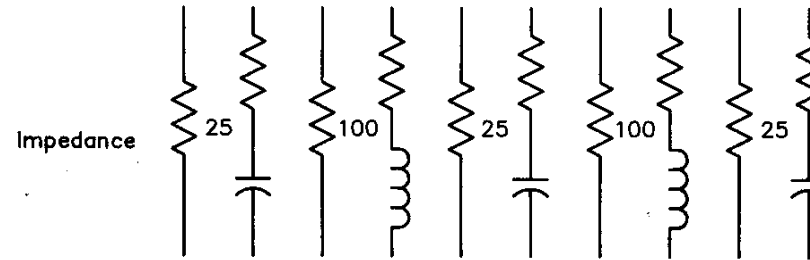


$Z_{IN} \Rightarrow$

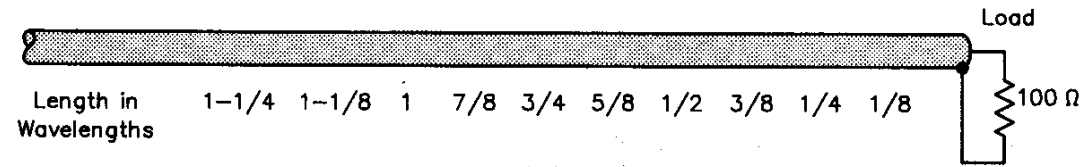


(A)

$R_{LOAD} = 25 \text{ ohm}$

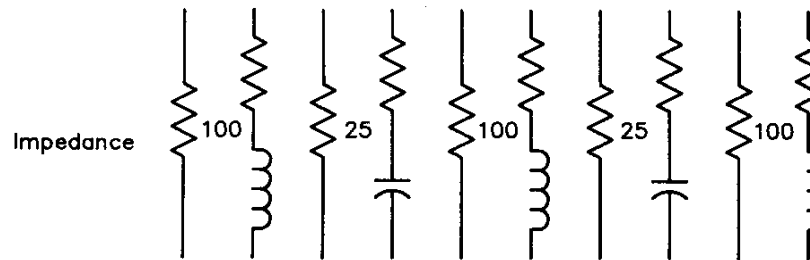



$Z_{IN} \Rightarrow$

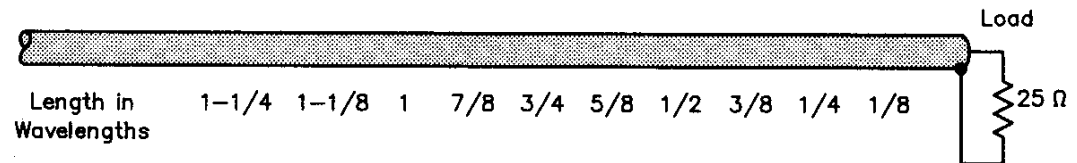

(B)



## Example 2

- What is  $Z_{IN}$  at **32 MHz** ?

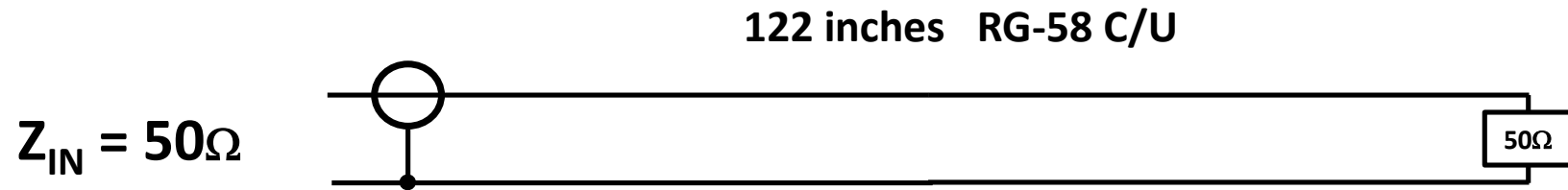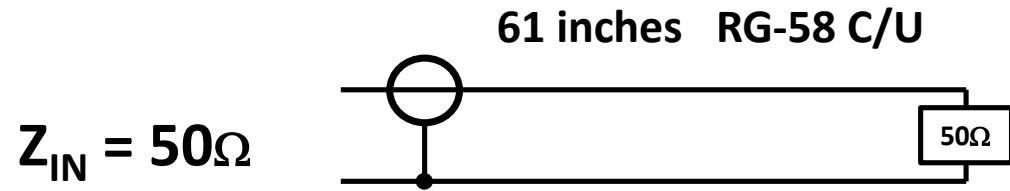


## Example 2 (cont'd)

- What is  $Z_{IN}$  at **32 MHz** ?

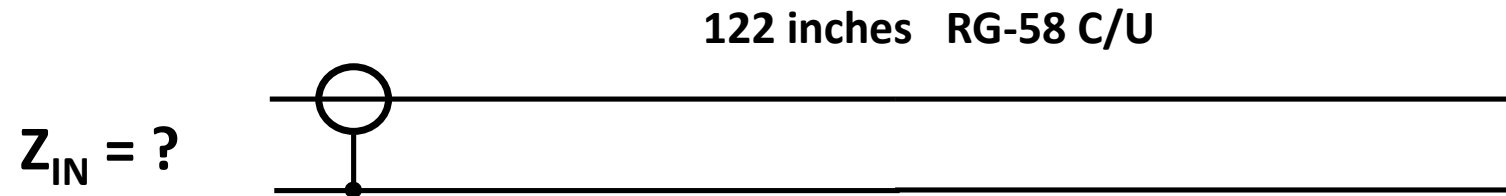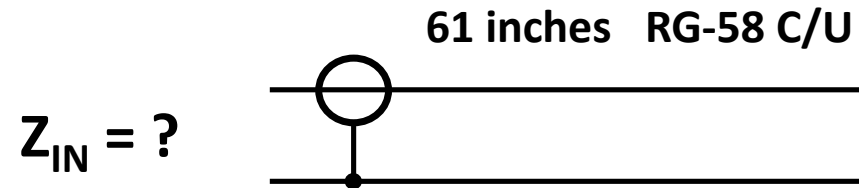



# Example 2 (cont'd)

- What is  $Z_{IN}$  at **32 MHz** ?

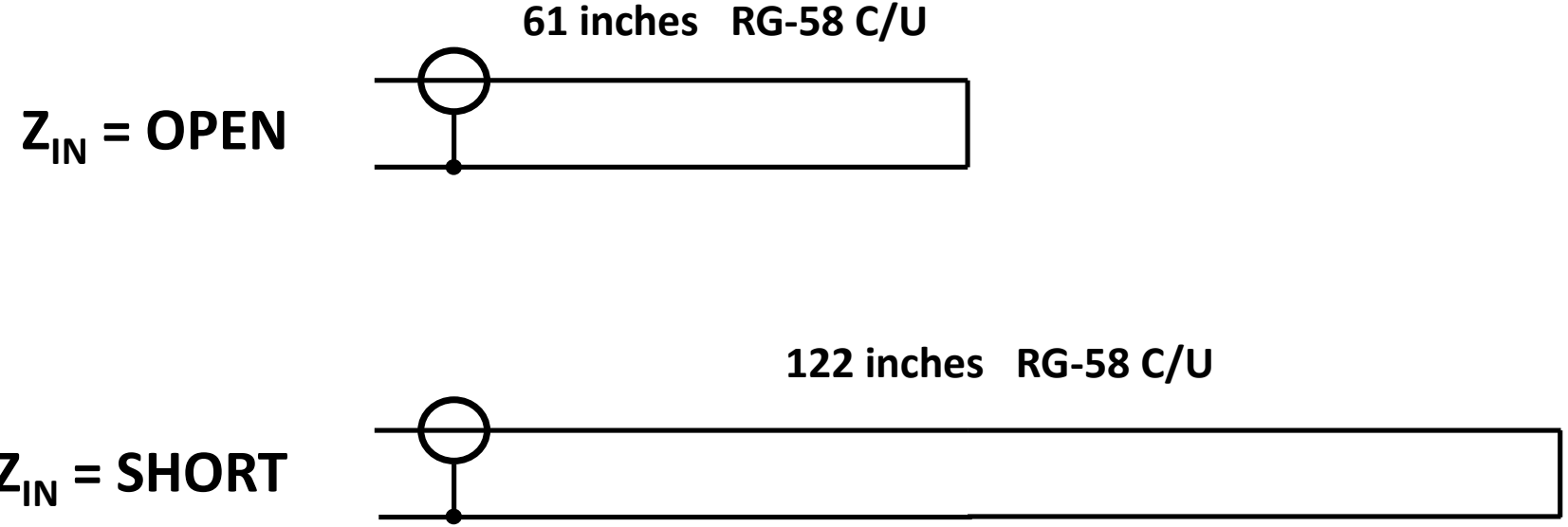

# Example 2 (cont'd)


- What is  $Z_{IN}$  at **32 MHz** ?

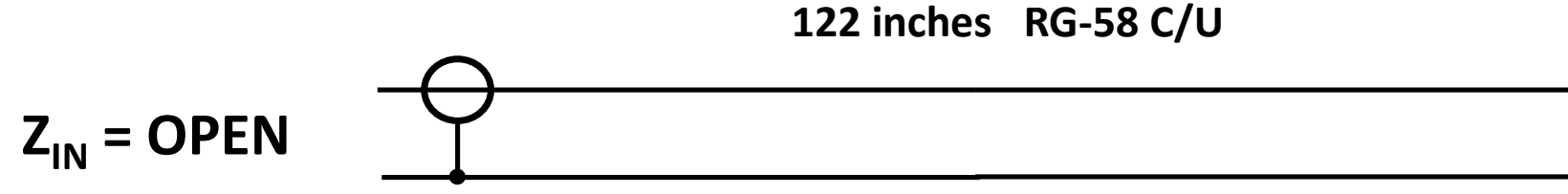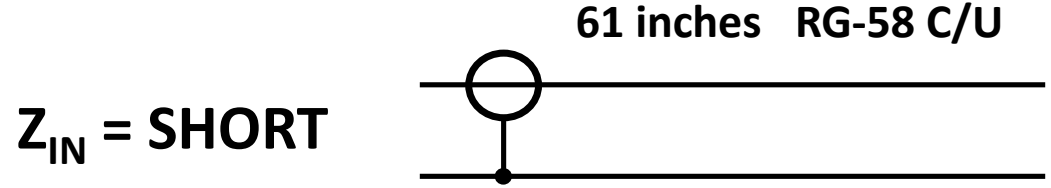

## Example 2 (cont'd)

- The electrical lengths at **32 MHz** are:
  - **61 inches =  $\frac{1}{4}$  wavelength**
  - **122 inches =  $\frac{1}{2}$  wavelength** } Electrical length  $\neq$  physical length
- Electrical length = VP x physical length
  - “VP” = velocity of propagation
- When  $Z_{\text{Load}} = Z_0$ :
  - $Z_{\text{IN}} = Z_0 = Z_{\text{Load}}$  (for any length of line)
- When  $Z_{\text{Load}} \neq Z_0$ :
  - **Transmission lines become impedance transformers**
  - When length =  $n_{\text{odd}} \times \frac{1}{4}$  wavelength, transmission lines **invert** the load impedance
    - “Invert” => high goes to low and low goes to high
    - Quarter wave transformer:  $Z_{\text{IN}} = (Z_0)^2 / Z_{\text{LOAD}}$
  - When length =  $n \times \frac{1}{2}$  wavelength, transmission lines **replicate** the load impedance

## Quiz: High SWR

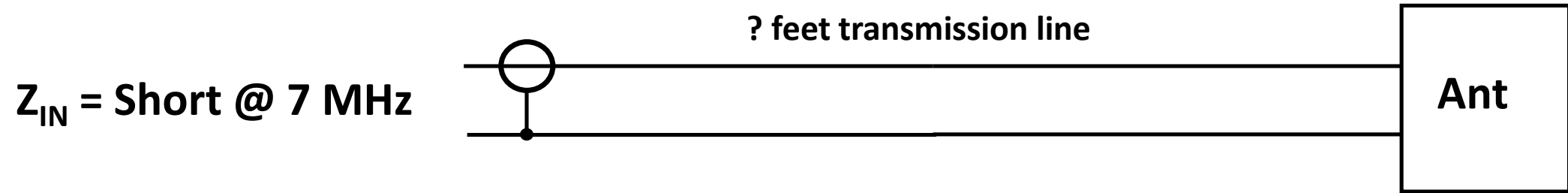

Is the antenna shorted?



## Quiz: High SWR – cont'd




Is the antenna shorted?

Don't know:

- Need to know the electrical length of the transmission line at 7MHz
- The antenna could be an open circuit


# Vector Network Analyzer: VNA 2180

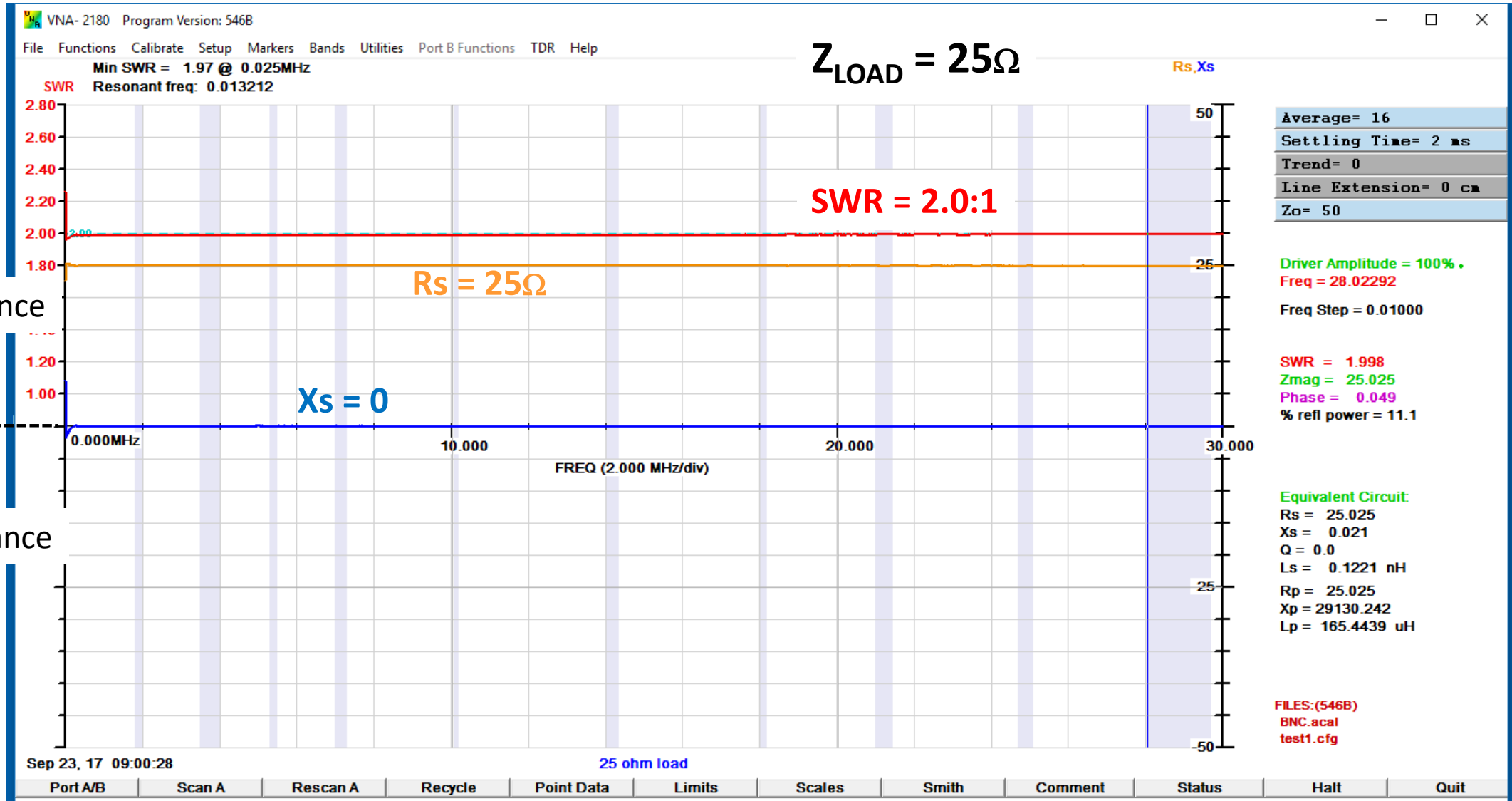


Inductance  
↑  
-----  
↓  
Capacitance
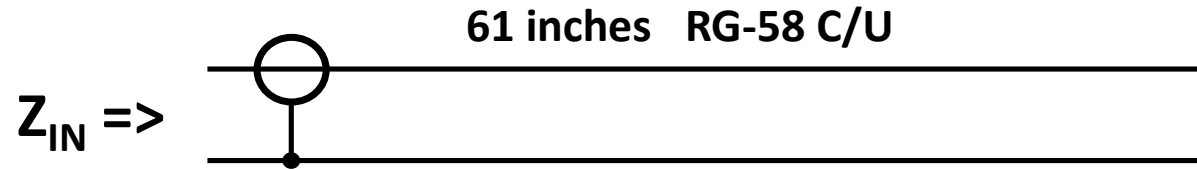
## Example 3: $Z_{IN}$ vs Frequency


- Use a VNA2180 to plot  $Z_{IN}$  vs frequency



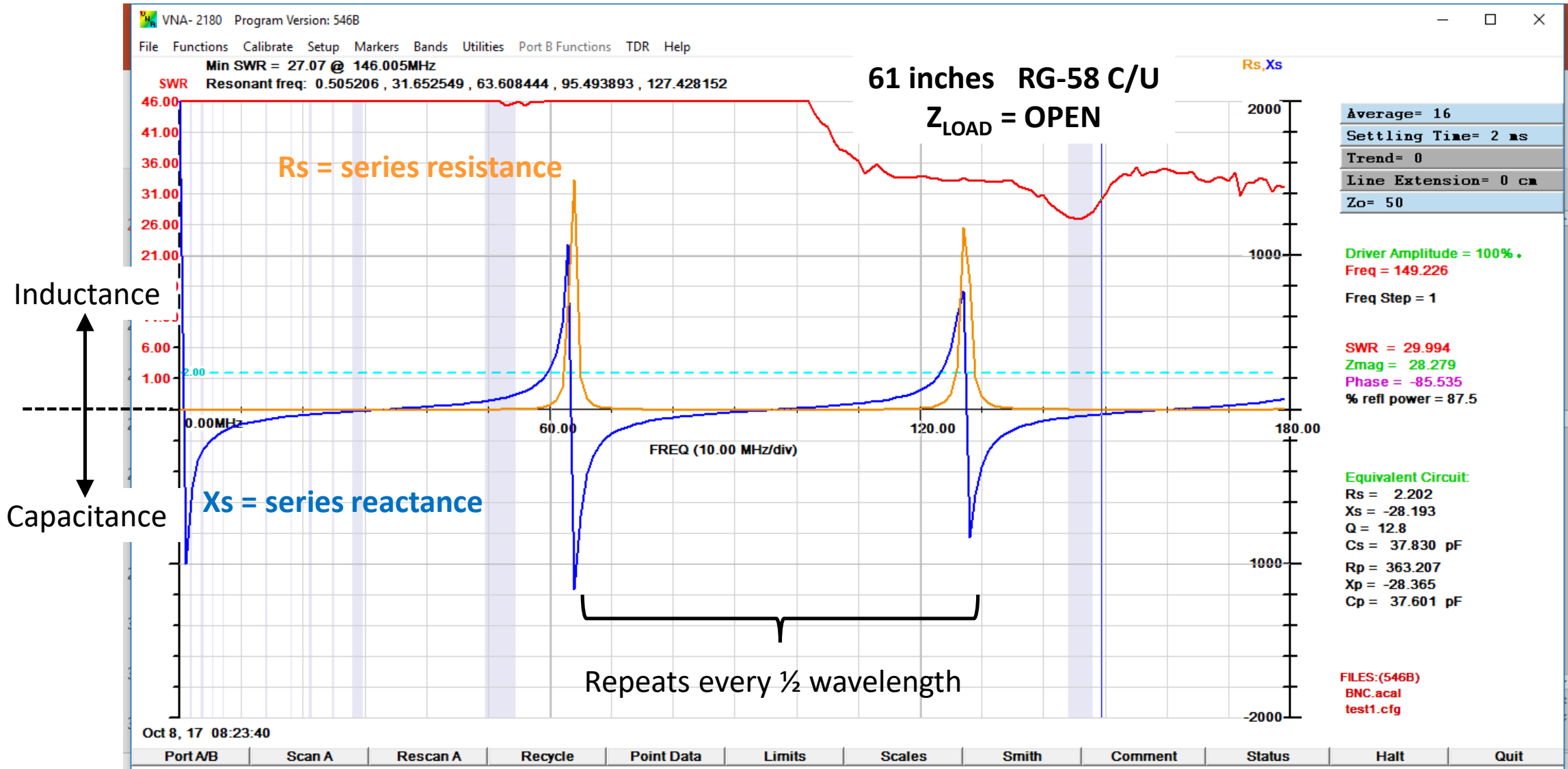
# Example 3: $Z_{IN}$ vs Frequency (cont'd)




# VNA 2180 With 25Ω Load

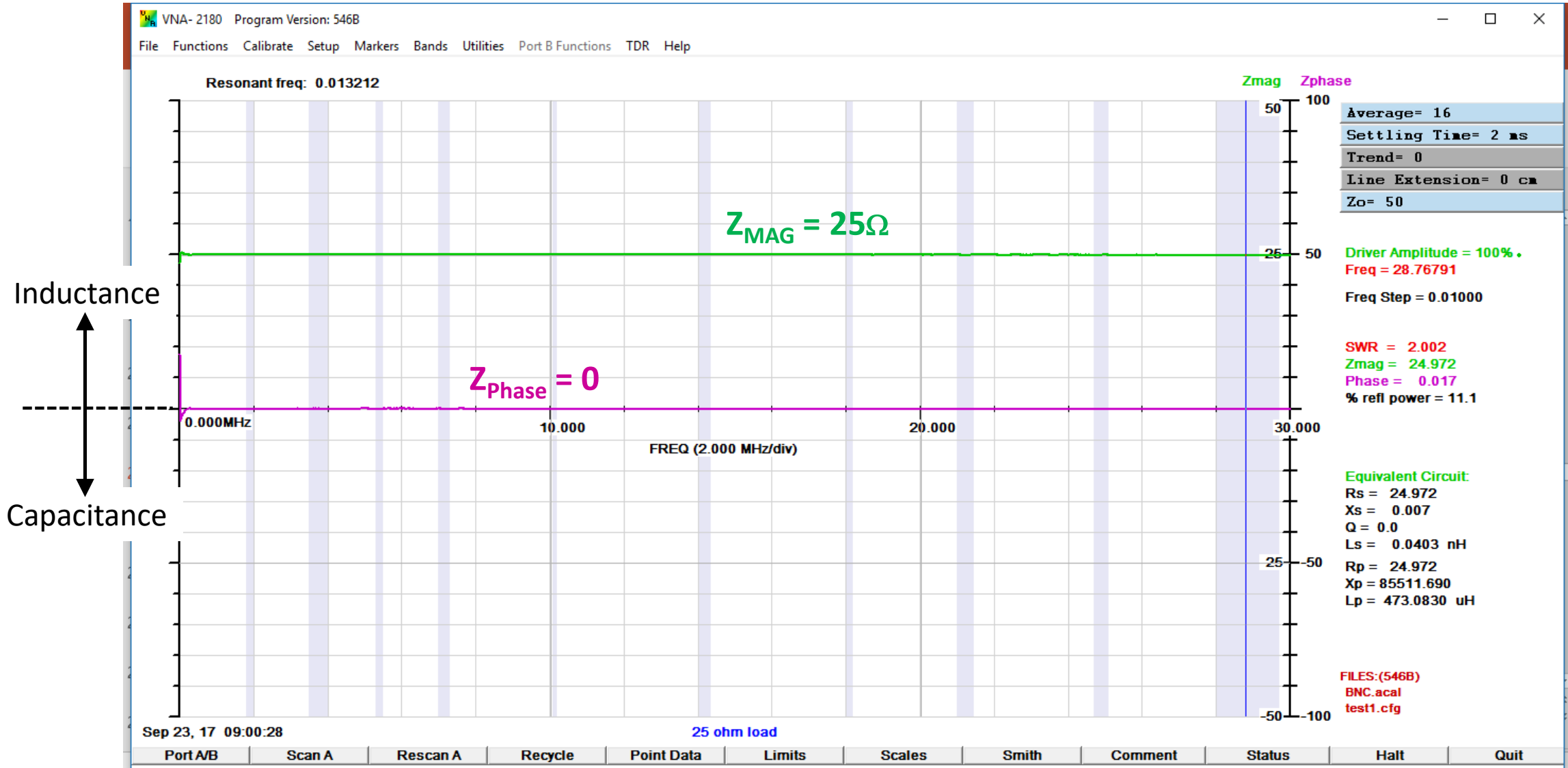

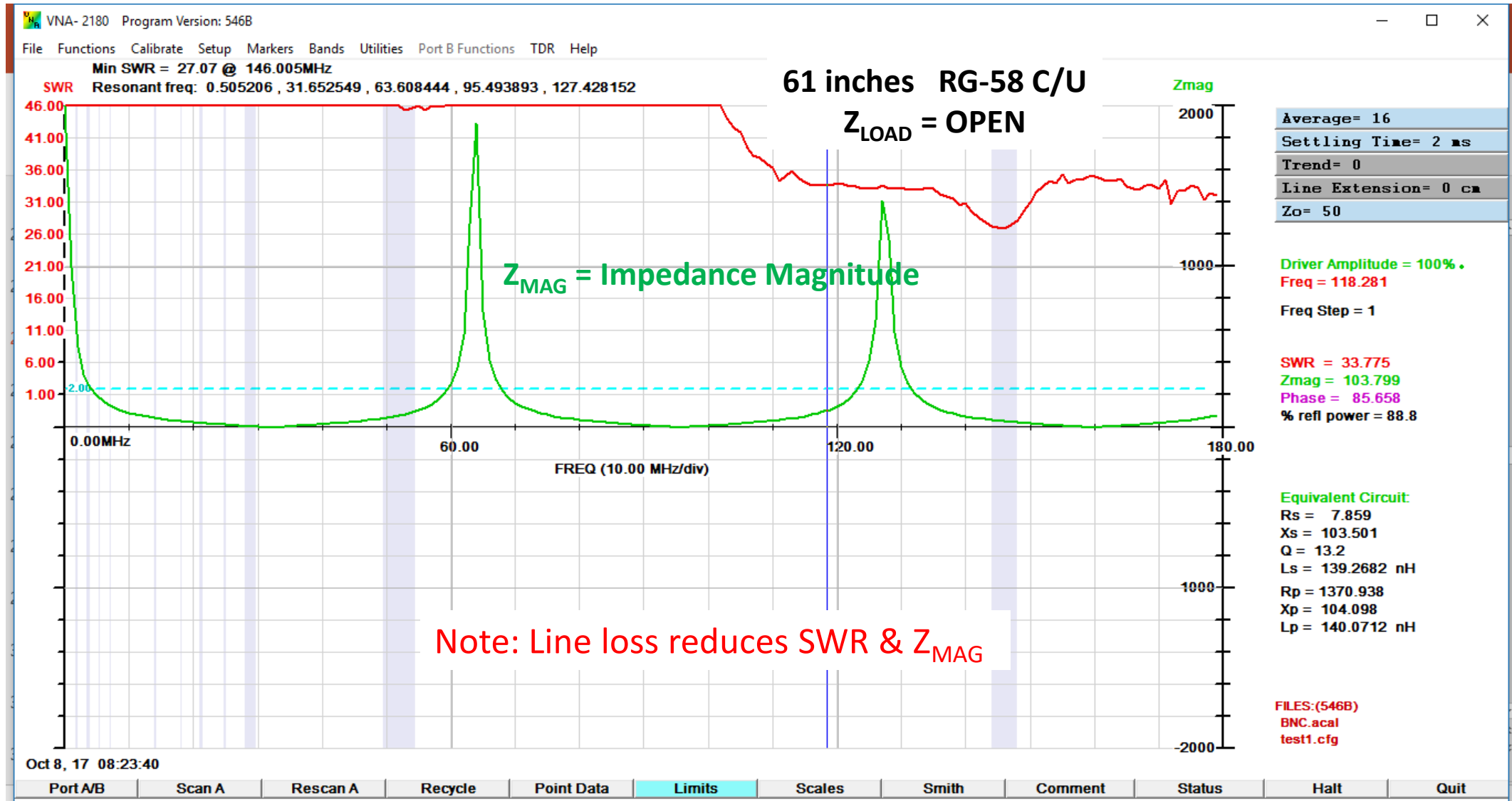
# Example 3: Plot $Z_{IN}$ vs Frequency (cont'd)


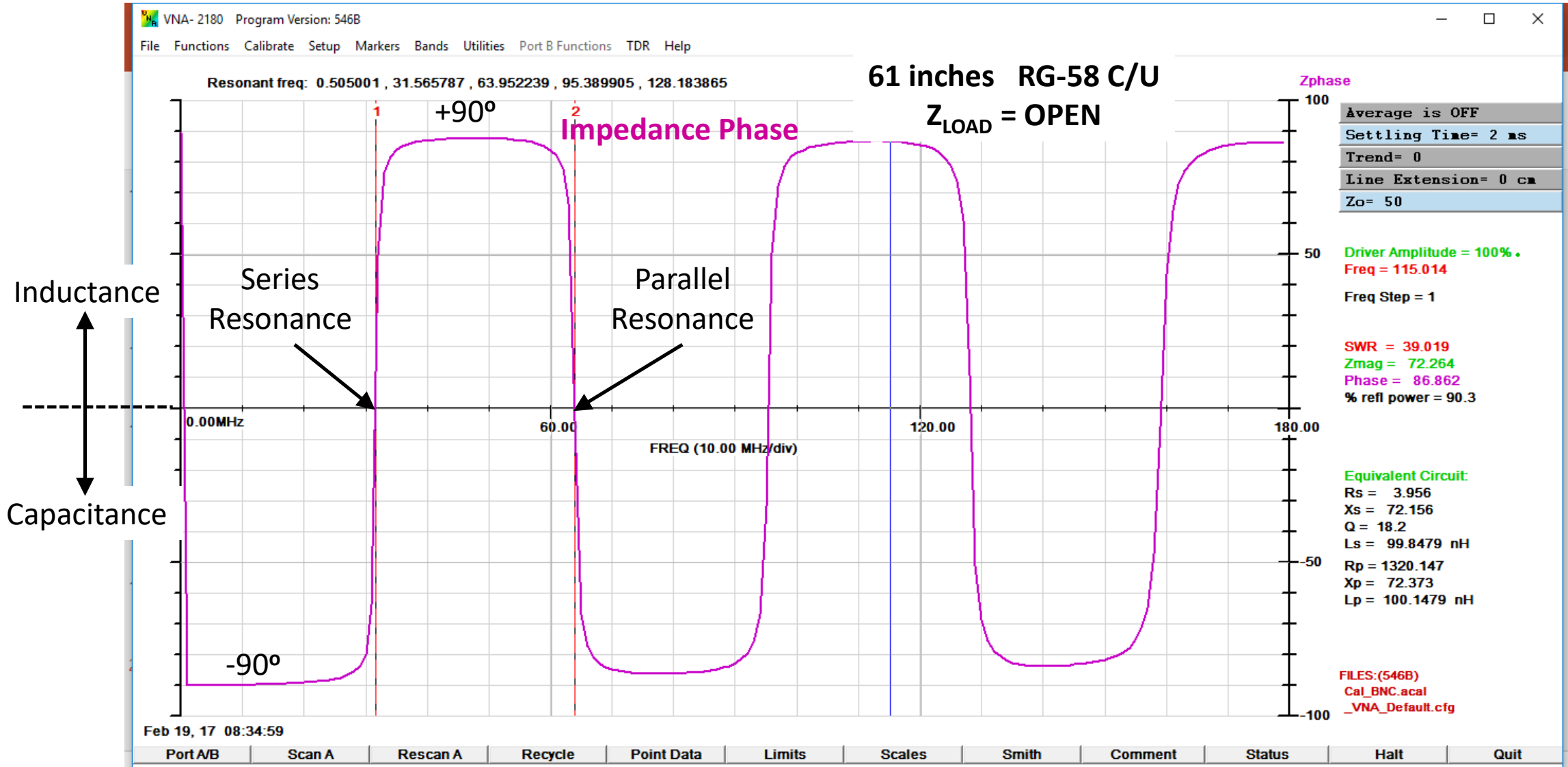
# Example 3: Plot $Z_{IN}$ vs Frequency (cont'd)



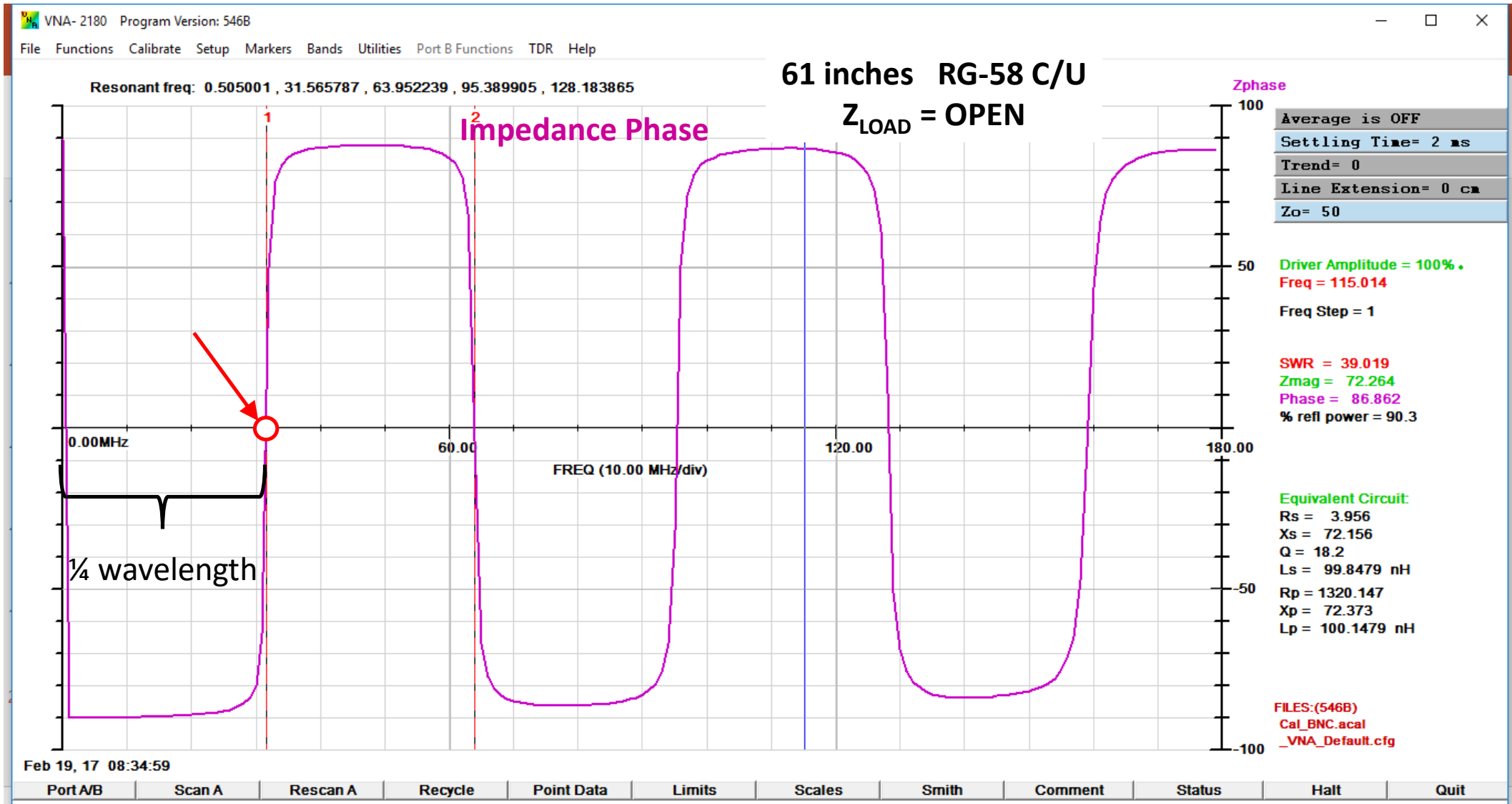
# Example 3: Plot $Z_{IN}$ vs Frequency (cont'd)





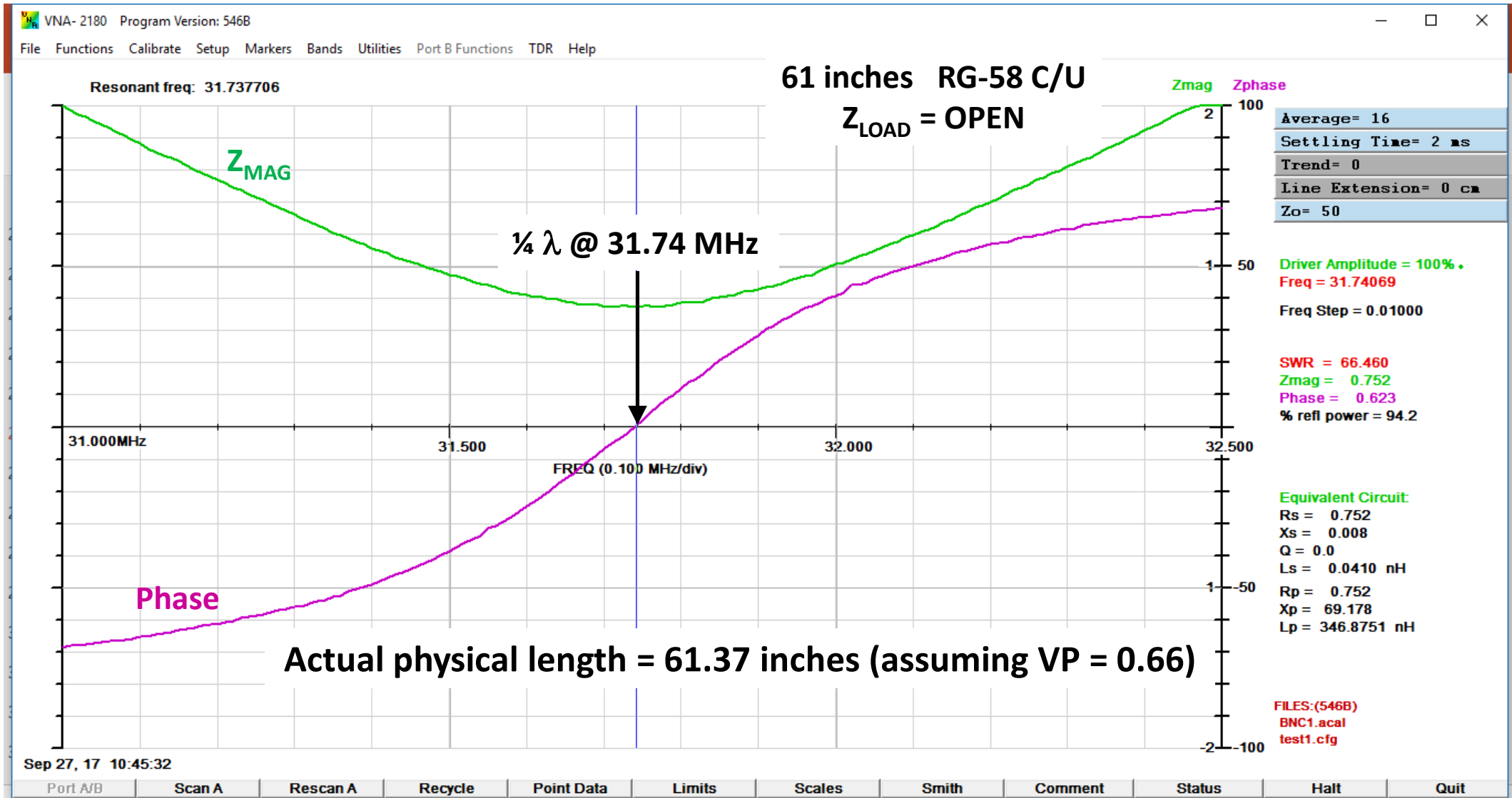
# Finding the Electrical Length of a Transmission Line


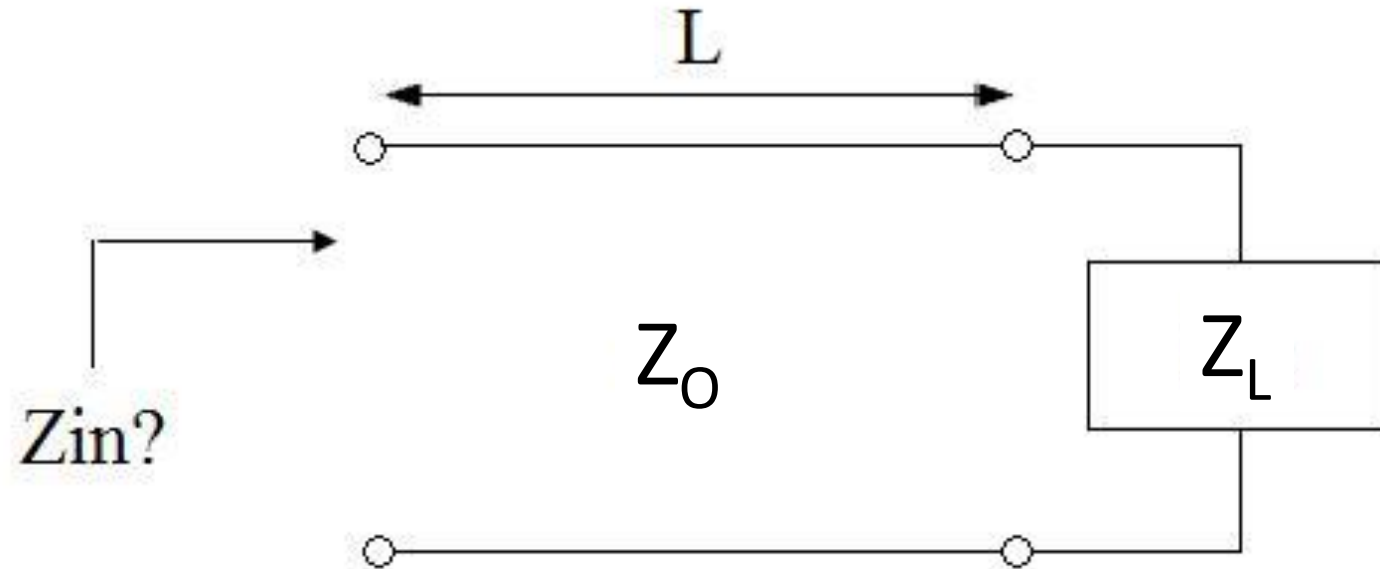
# Finding the Input Impedance of a Transmission Line



# Why Was The Smith Chart Developed?

Frank Lynch, W4FAL

## The Formula!

Impedance Looking  
Into A Transmission

Line

$$Z_x = Z_0 \frac{Z_L + Z_0 \tanh \gamma x}{Z_0 + Z_L \tanh \gamma x}$$


Hyperbolic Tangent

$$\gamma = \alpha + j\beta$$


Complex  
Numbers

This is why the chart was developed.. Before calculators and computers the above formula's were impossible! They're still not easy today.


# Smith Chart

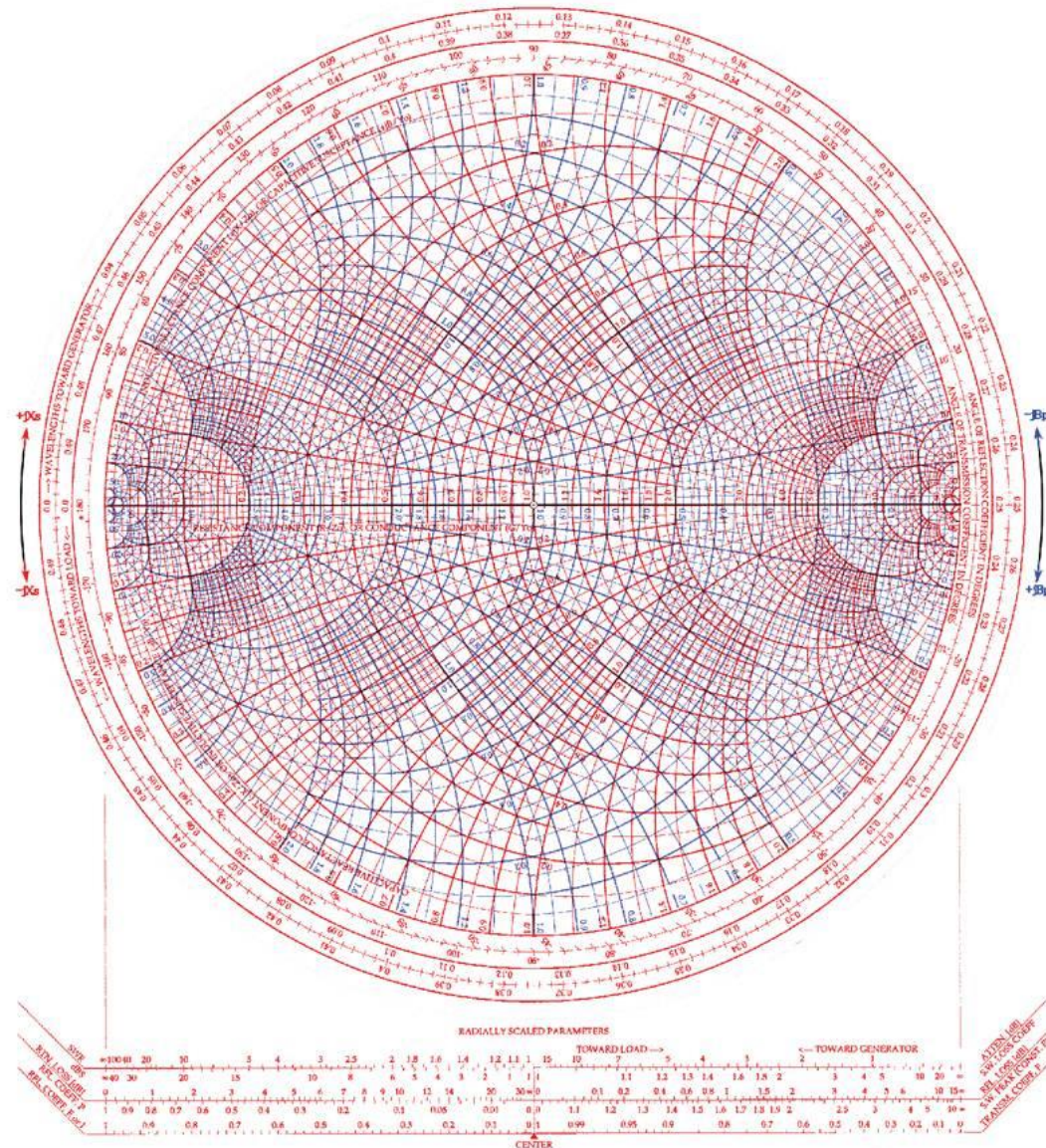

# Simplified Smith Chart

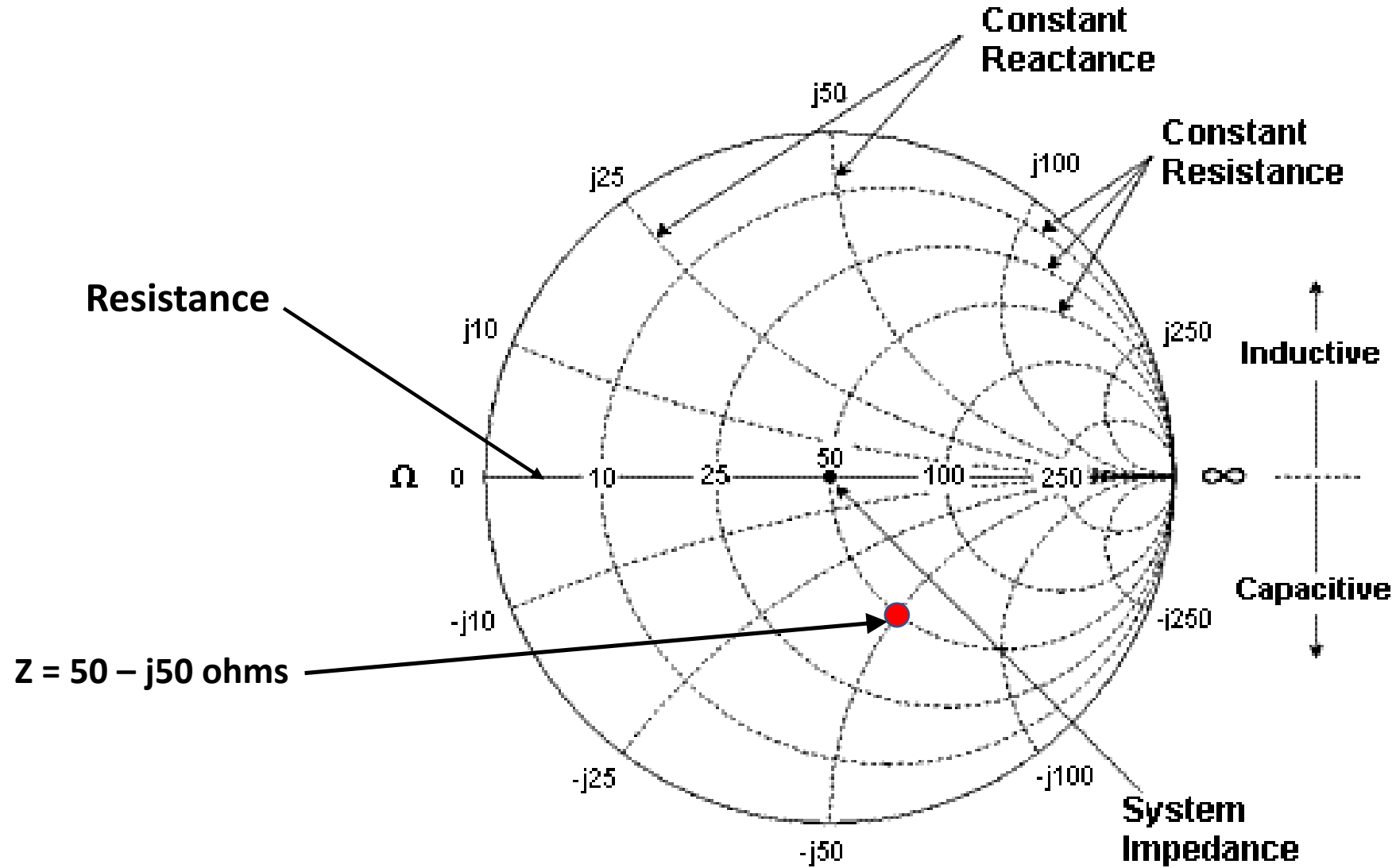


# Normalized Smith Chart

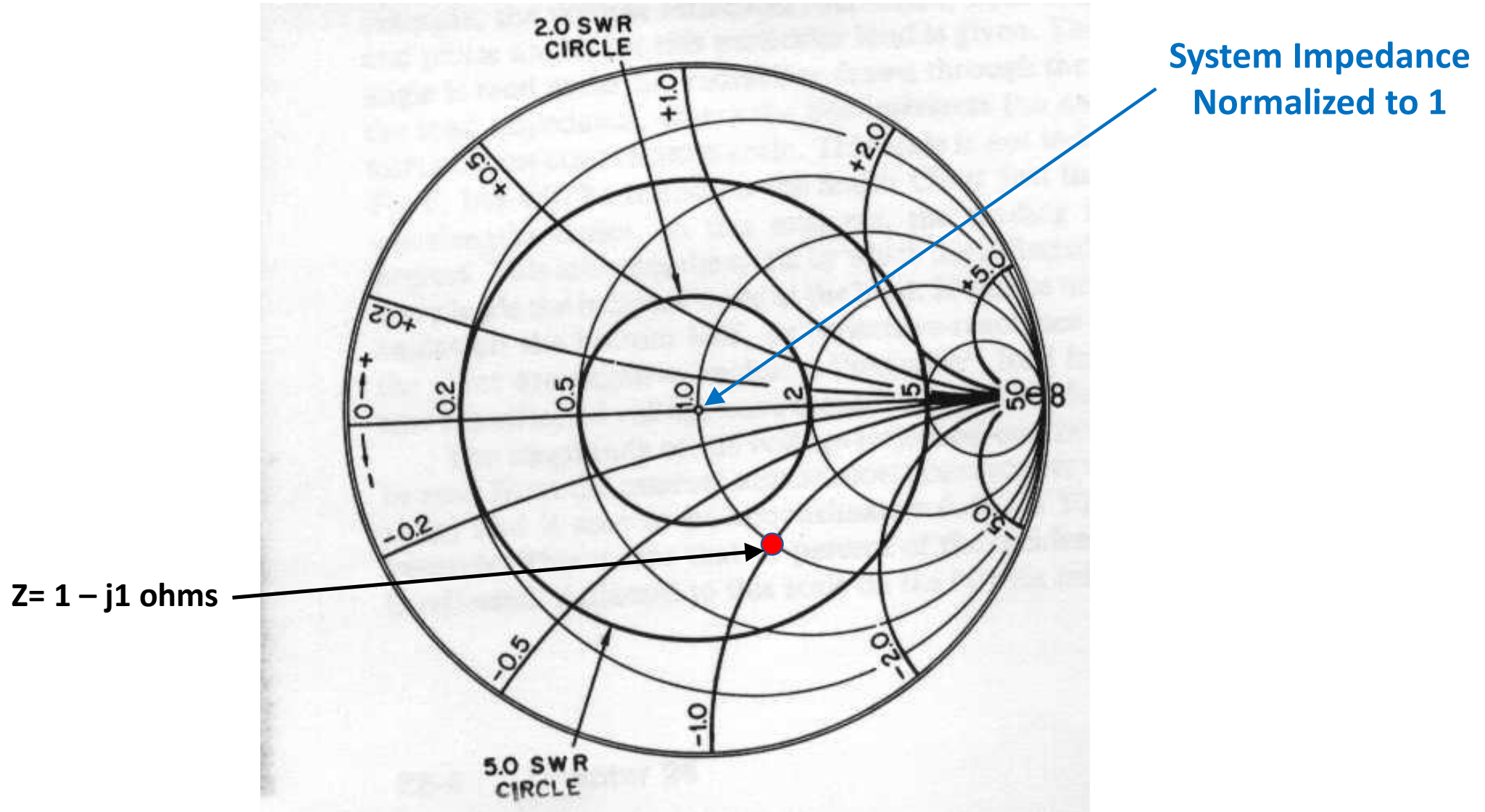

# SWR vs Transmission Line Length


For Lossless Transmission Line:

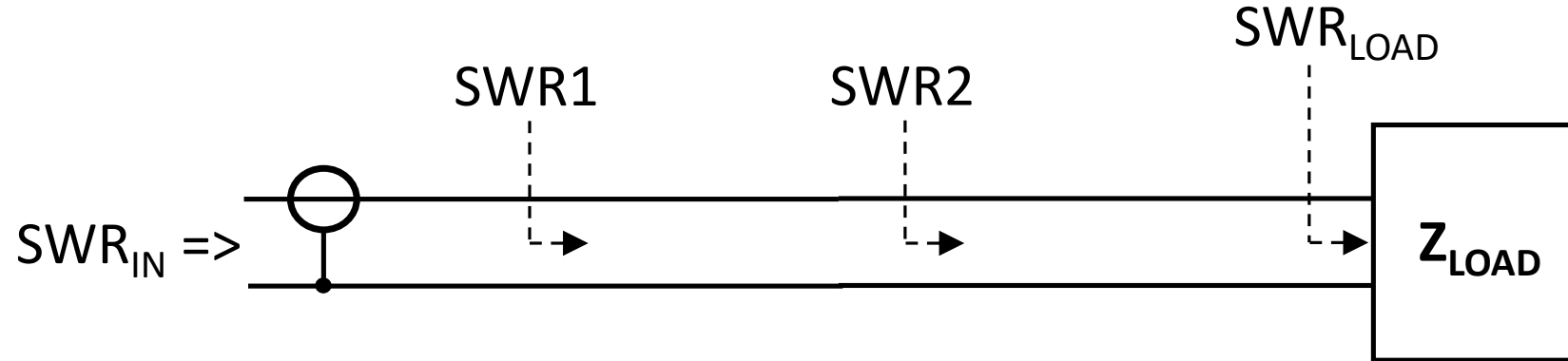

- SWR is determined solely by  $Z_0$  &  $Z_{LOAD}$
- SWR is constant along a lossless transmission line
  - $SWR_{IN} = SWR1 = SWR2 = SWR_{LOAD}$


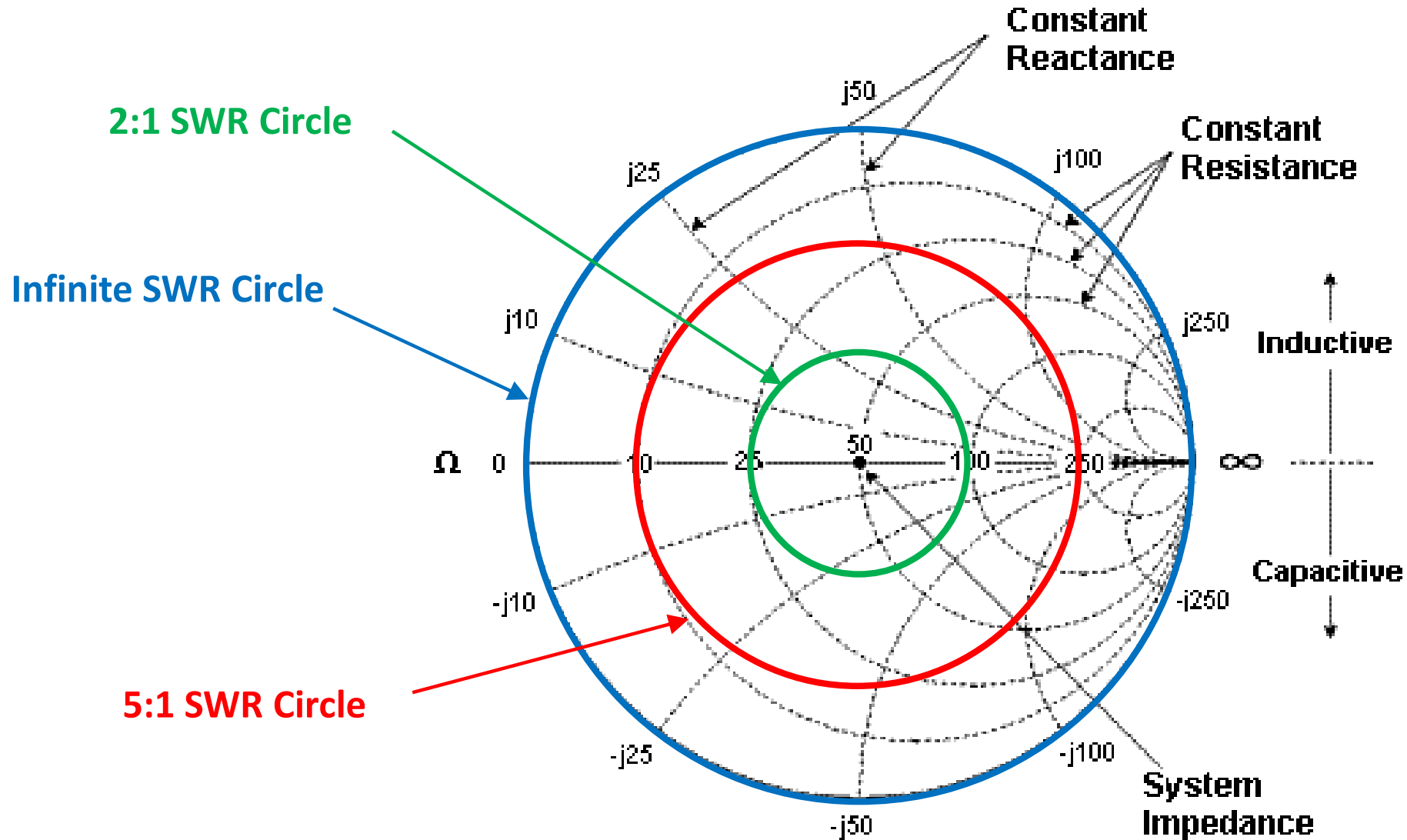
# Simplified Smith Chart – Constant SWR Circles



1. Adding Length to a Lossless Transmission Line Causes Clockwise Rotation Around a Constant SWR Circle
2. Z changes but SWR is constant
3. One Full Rotation Equals  $\frac{1}{2}$  Wavelength



# Problem: Antenna Tuner Can't Find A Match

- Many built-in antenna tuners can only match up to a 3:1 SWR
  - External tuners have much better range than built-in tuners
- It is easier for most antenna tuners to match a high impedance
  - Ex: MFJ-993B spec'd matching range is 6 – 1600 $\Omega$ 
    - SWR:
      - 1600 $\Omega$  => 32:1
      - 6 $\Omega$  => 8:1
  - Many antenna tuners become very lossy at very low impedances
    - Obtaining a match is only part of the solution
    - Example: Palstar AT-Auto
      - Loss matching 6.25 ohms on 160M is **42%**! (QST Aug 2006)

# Problem: Antenna Tuner Can't Find A Match

- Many built-in antenna tuners can only match up to a 3:1 SWR
  - External tuners have much better range than built-in tuners
- It is easier for most antenna tuners to match a high impedance
  - Ex: MFJ-993B spec'd matching range is 6 – 1600 $\Omega$


Common recommendation: add a short length of coax to reduce the SWR

6 $\Omega$  => 8:1


- Many antenna tuners become very lossy at very low impedances
  - Obtaining a match is only part of the solution
  - Example: Palstar AT-Auto
    - Loss matching 6.25 ohms on 160M is **42%**! (QST Aug 2006)

## Example 4: Antenna Matching Problem

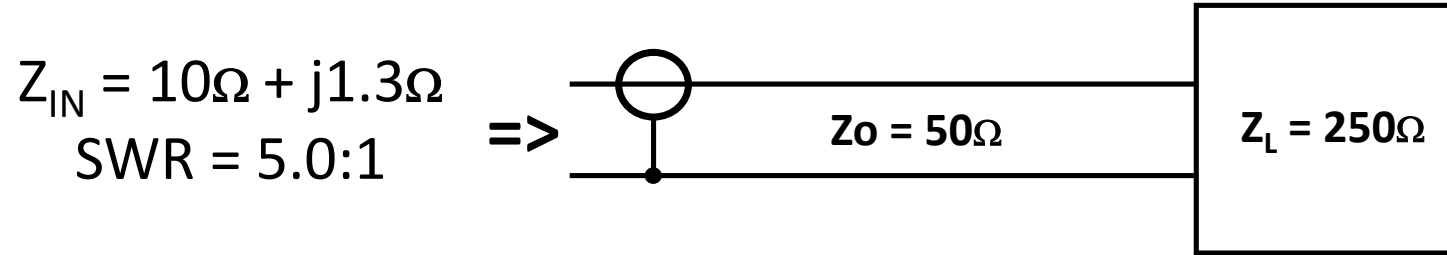
- Problem: Antenna Tuner Can't Find A Match At **14.0 MHz**:




$\Downarrow$

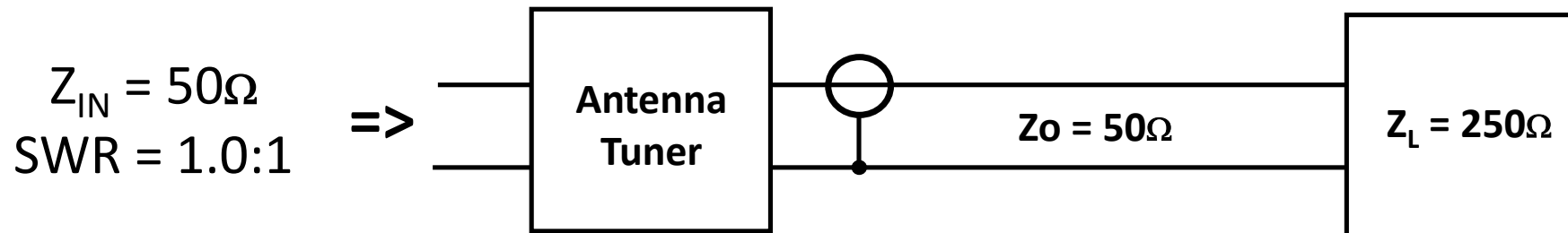
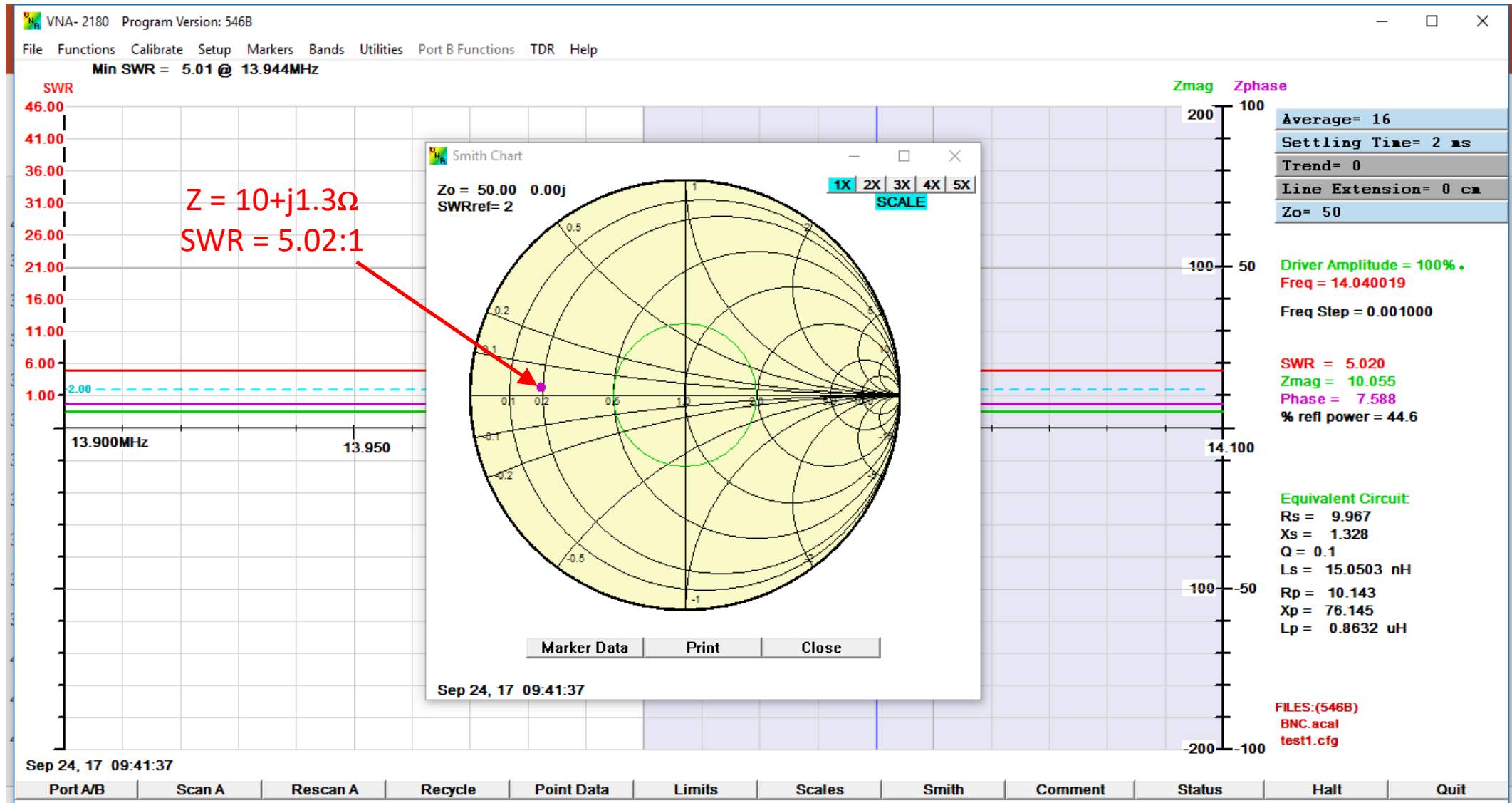
# Example 4: Antenna Matching Problem (cont'd)



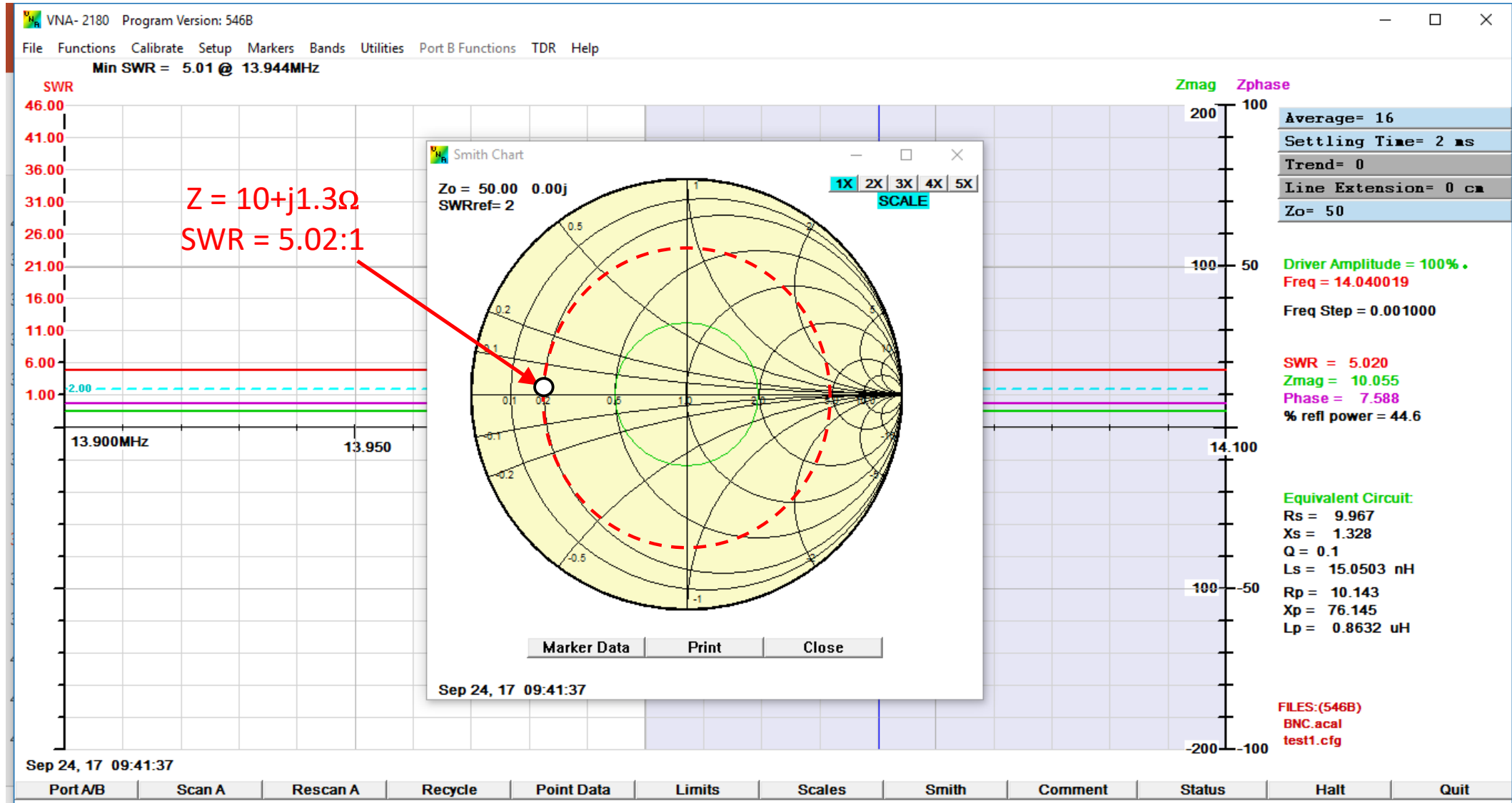
# Example 4: Antenna Matching Problem (cont'd)




$Z = 10 + j1.3 \Omega$   
SWR = 5.02:1
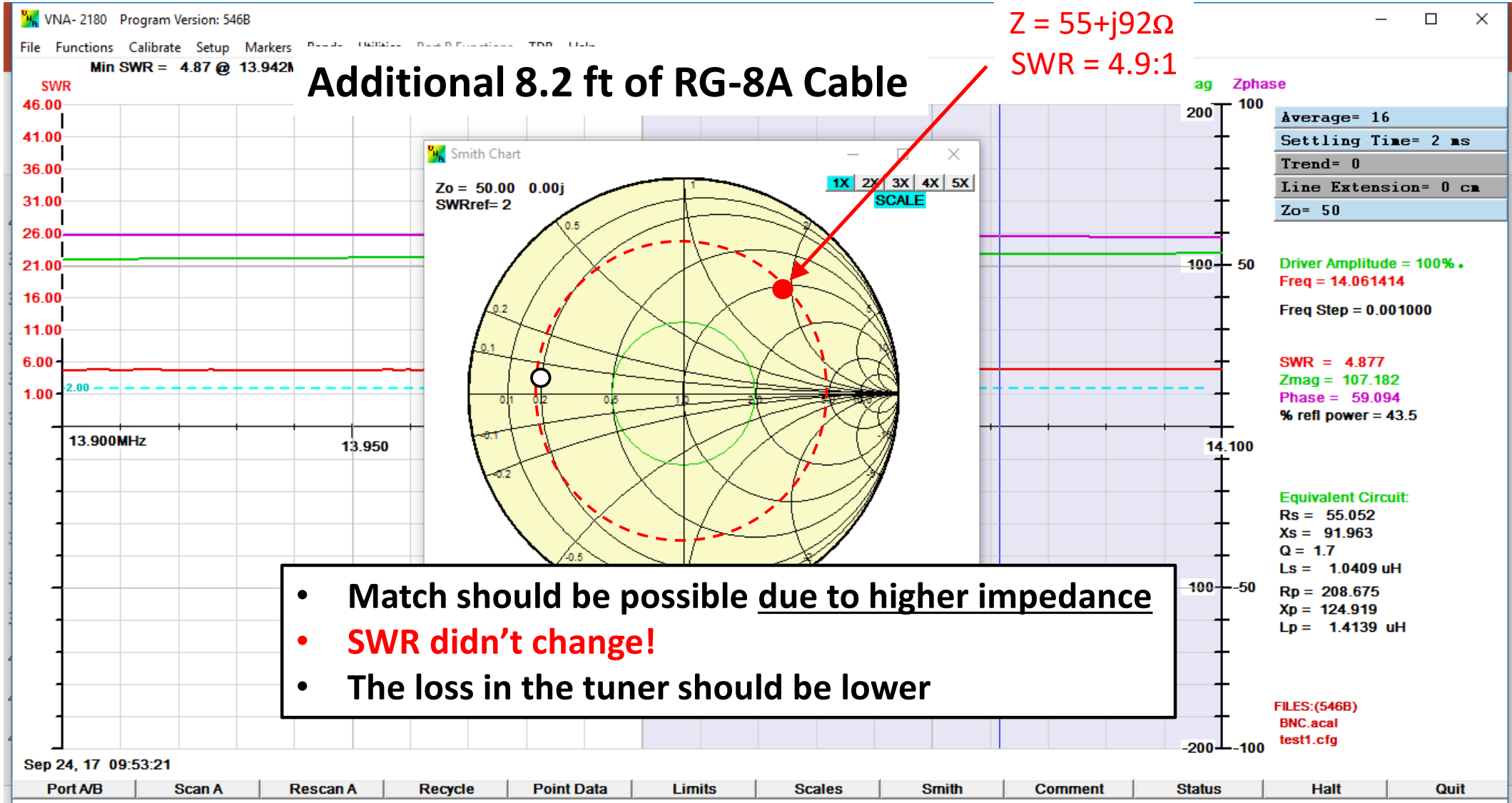
# Example 4: Antenna Matching Problem (cont'd)



# Example 4: Antenna Matching Problem (cont'd)

- Simple (Single Band) Solution:

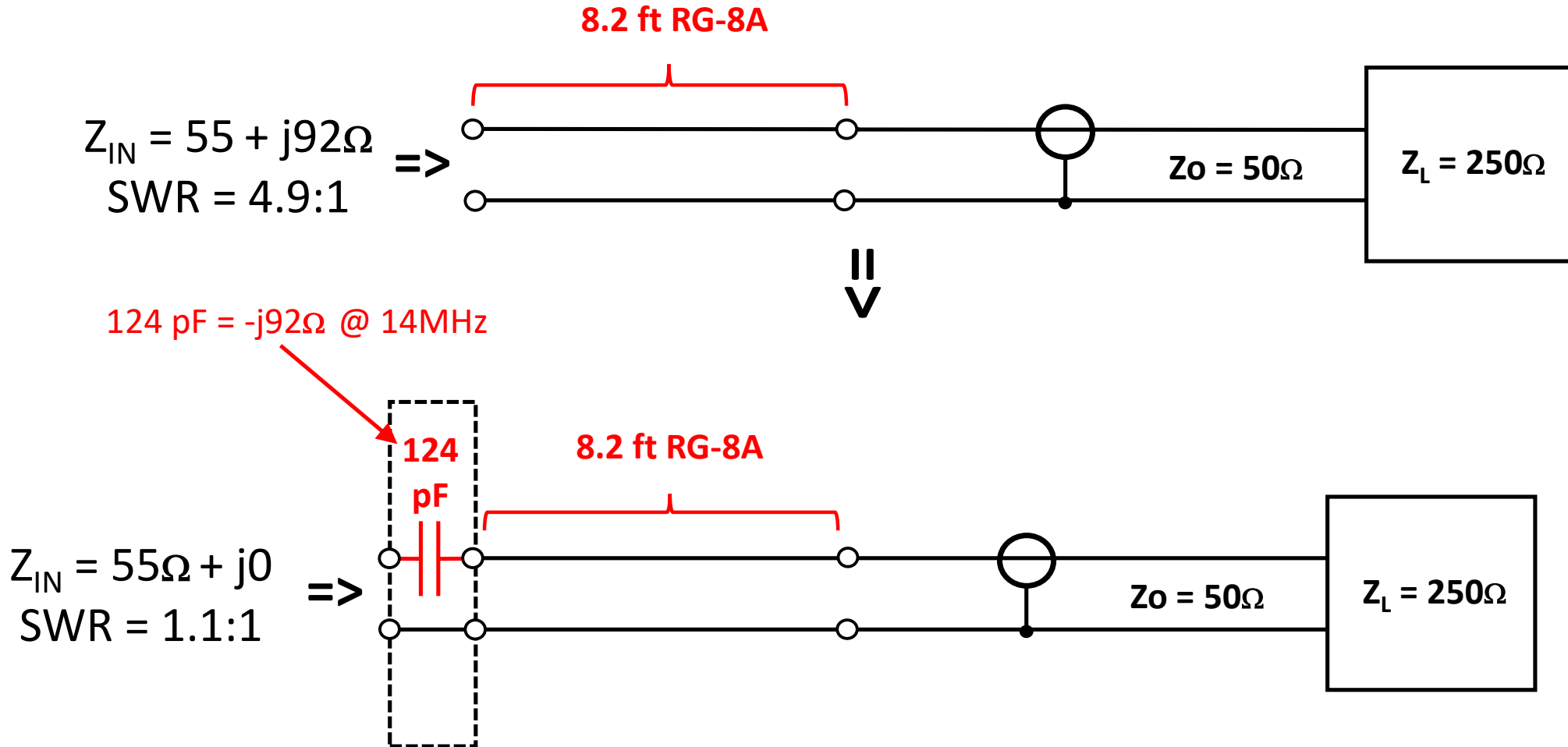



# ARRL Transmission Line for Windows (TLW)

- Free software with ARRL Antenna Book

**TLW, Transmission Line Program for Windows** Help

Version 2.0, Copyright 2000-2003, ARRL, by N6BV, July 22, 2003

Cable Type: **RG-8A (Belden 8237)**

Feet Length: **8.2** Feet **0.177** Lambda Frequency: **14.0** MHz  
 Meters Use "w" suffix for wavelength (for example, 0.25w)

Characteristic Z<sub>0</sub>: 52.2 - j 0.31 Ohms Matched-Line Loss: 0.706 dB/100 Feet  
Velocity Factor: 0.66 Max Voltage 3700 V Total Matched-Line Loss: 0.058 dB

Source  
 Normal  
 Autek  
 Noise Bridge

Load Resistance: **10** Ohms  
 Input Reactance: **1.3**

Volt./Current **Graph**  
 Resist./Reac.

**Tuner** **Print** **Exit**

SWR at Line Input: **5.06** SWR at Load: **5.23** Rho at Load: **0.67895**  
Additional Loss Due to SWR: **0.141** dB Total Line Loss: **0.199** dB  
Impedance at Input: **50.17 + j 91.54** Ohms ⇒ **104.39** Ohms at **61.27** Degrees




## Example 5: Antenna Tuning

- Should an antenna be tuned to resonance, or for lowest SWR?
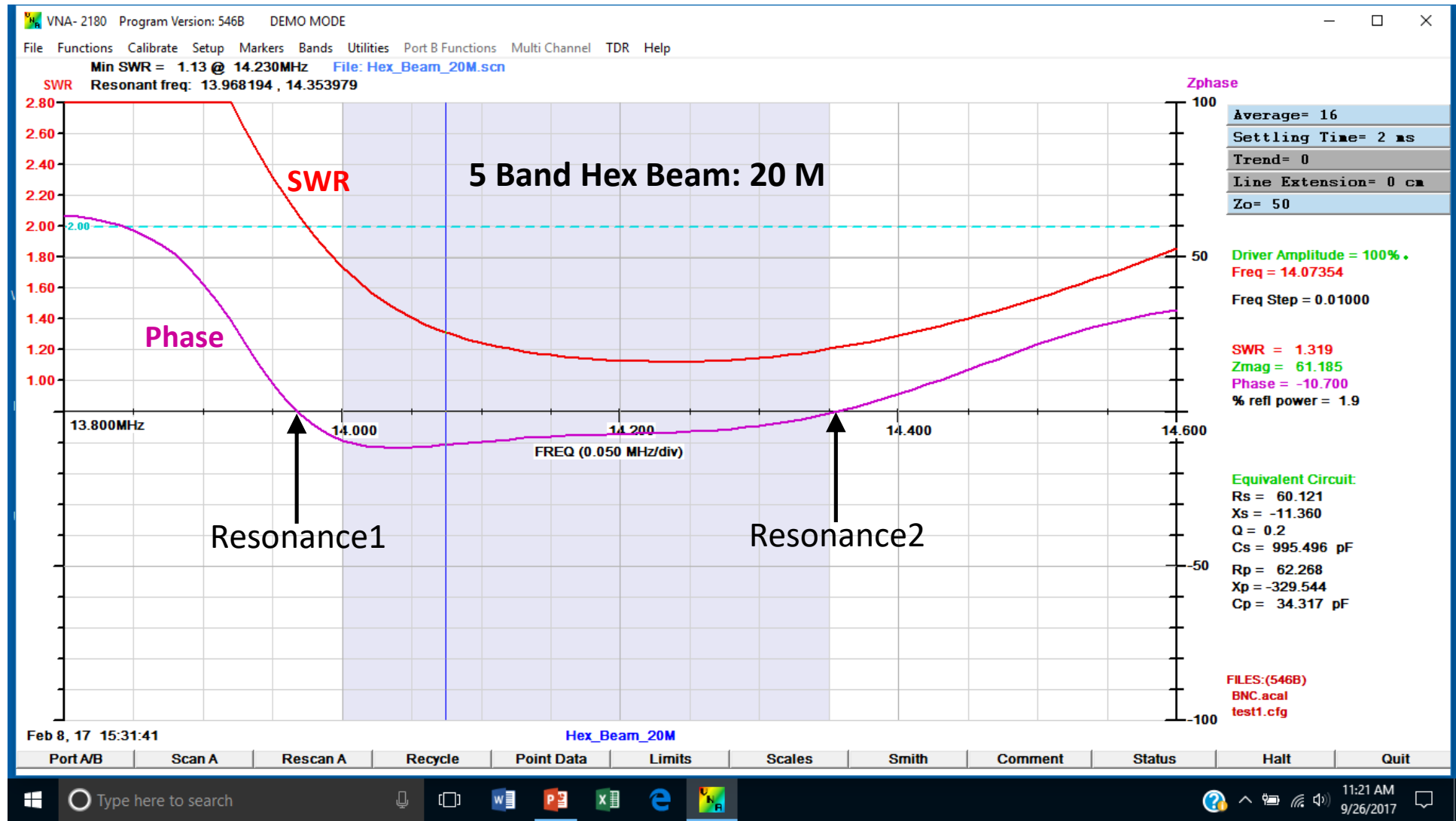
# Example 5: Antenna Tuning – cont'd

- Should an antenna be tuned to resonance, or for lowest SWR?




# Example 5: Antenna Tuning – cont'd

## 40 M Dipole




# Example 5: Antenna Tuning – cont'd

## 40 M Dipole


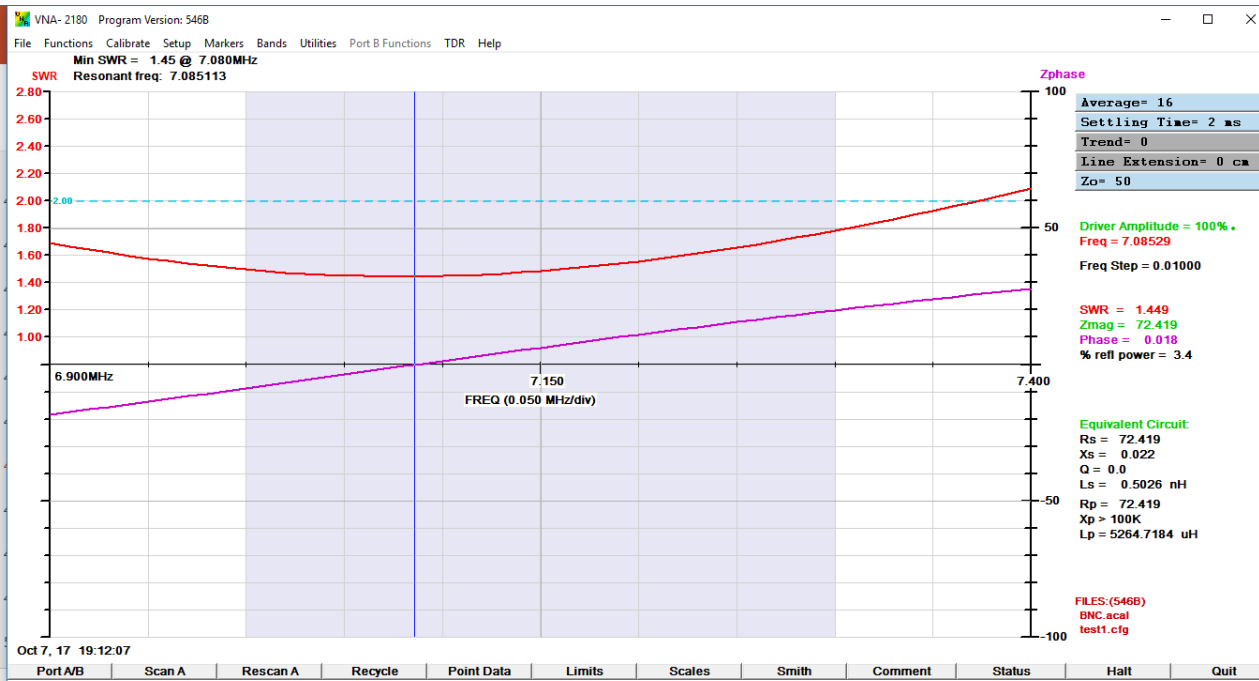

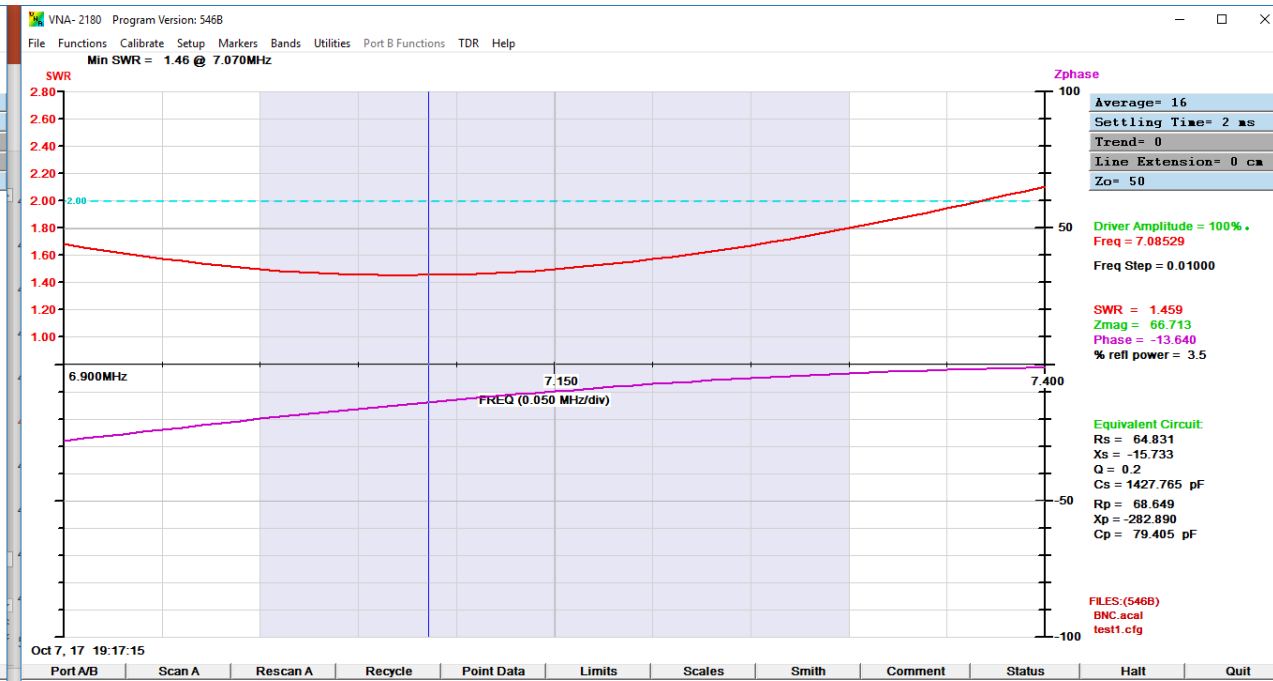
## 40 M Dipole at input to transmission line





Is the antenna no longer resonant?

## Example 5: Antenna Tuning – cont'd

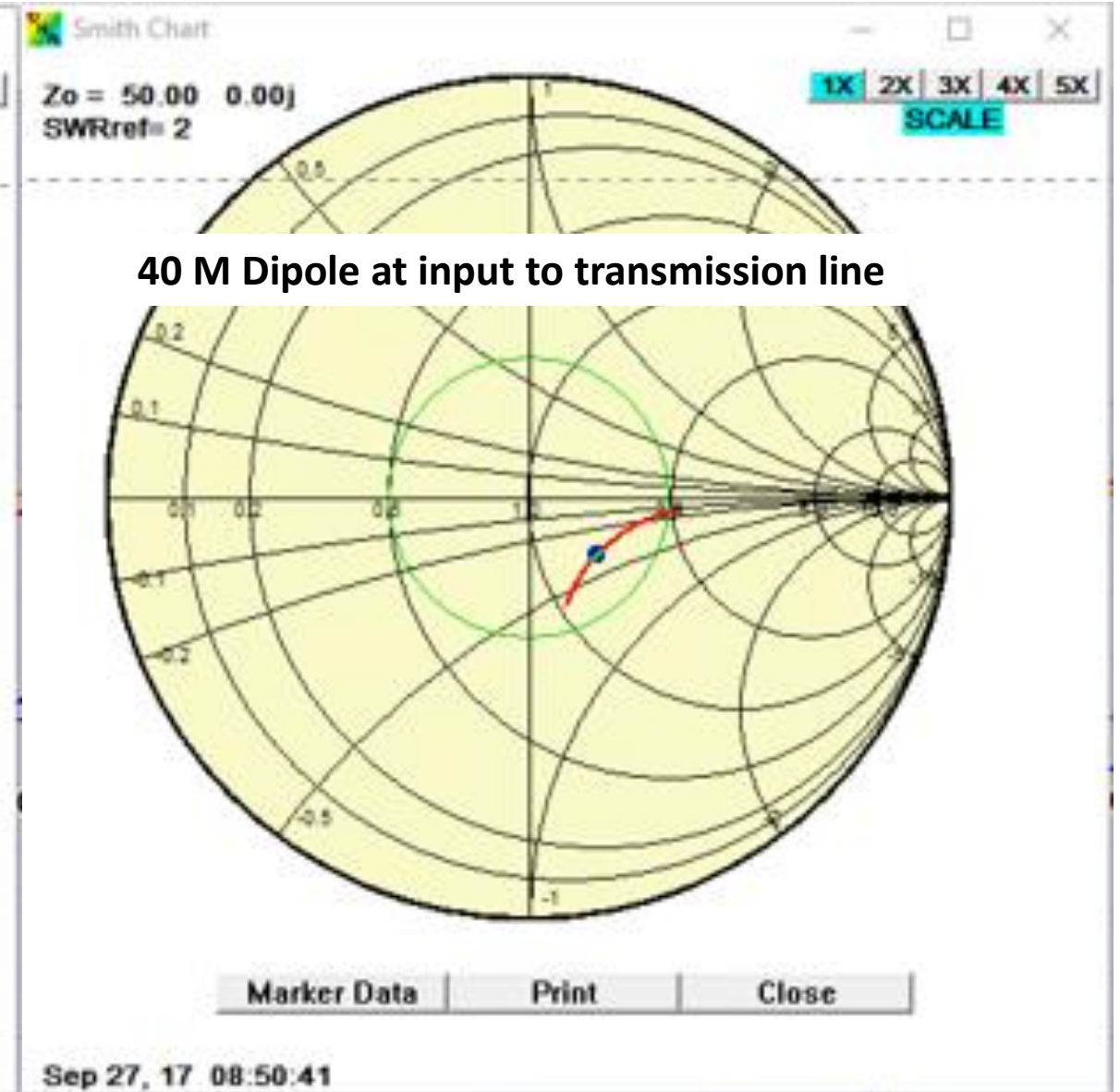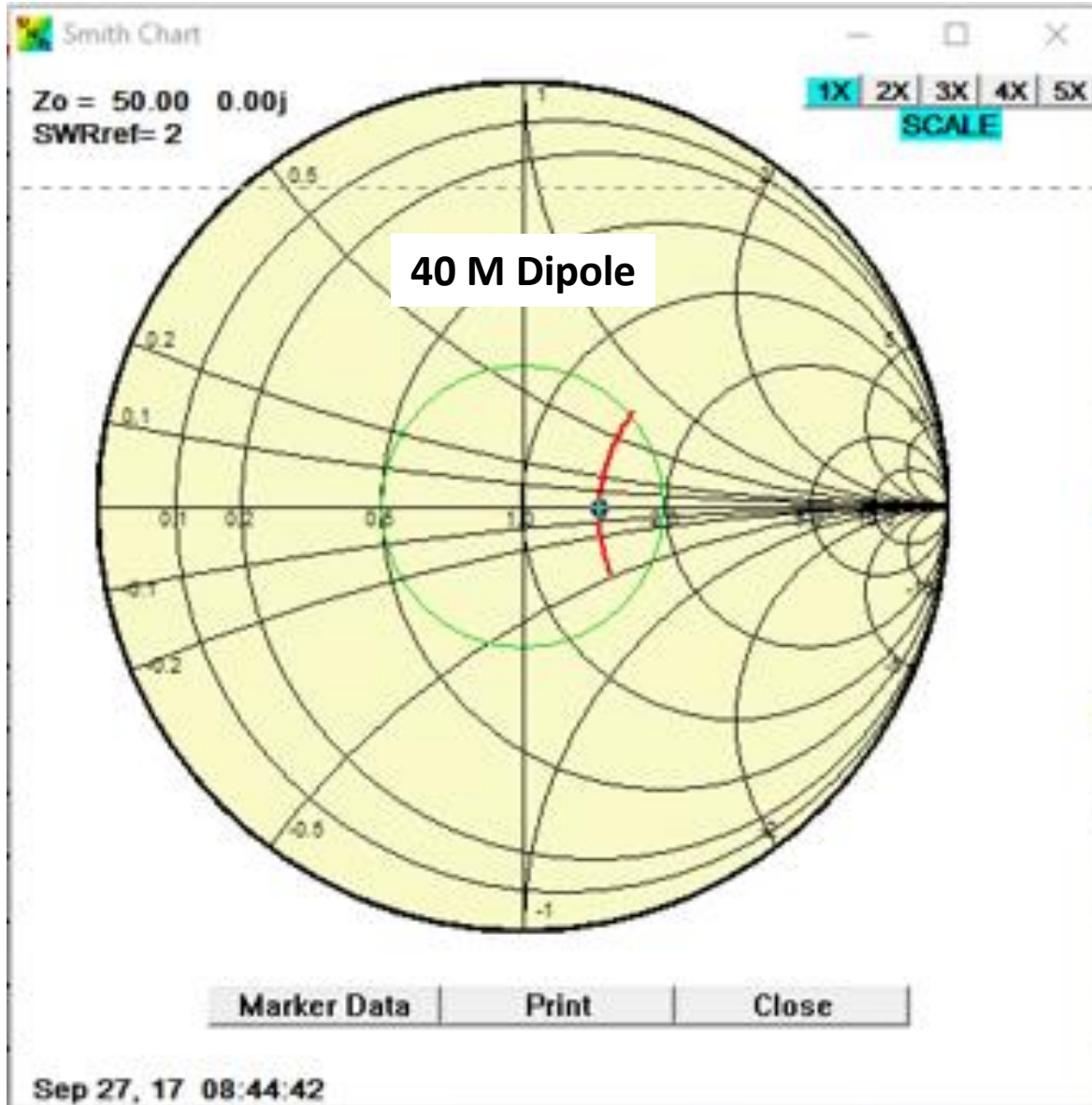




## Example 5: Antenna Tuning – cont'd

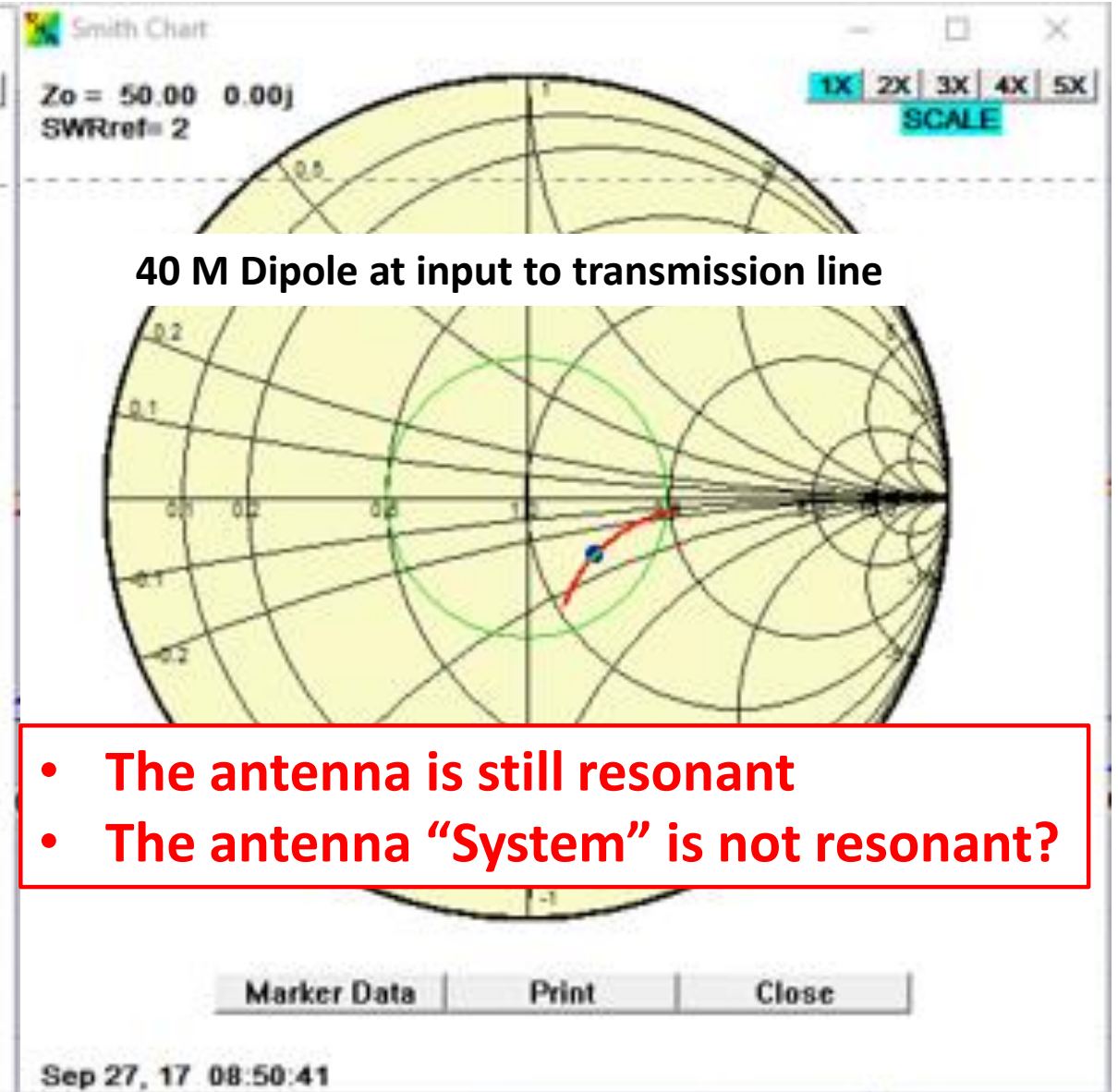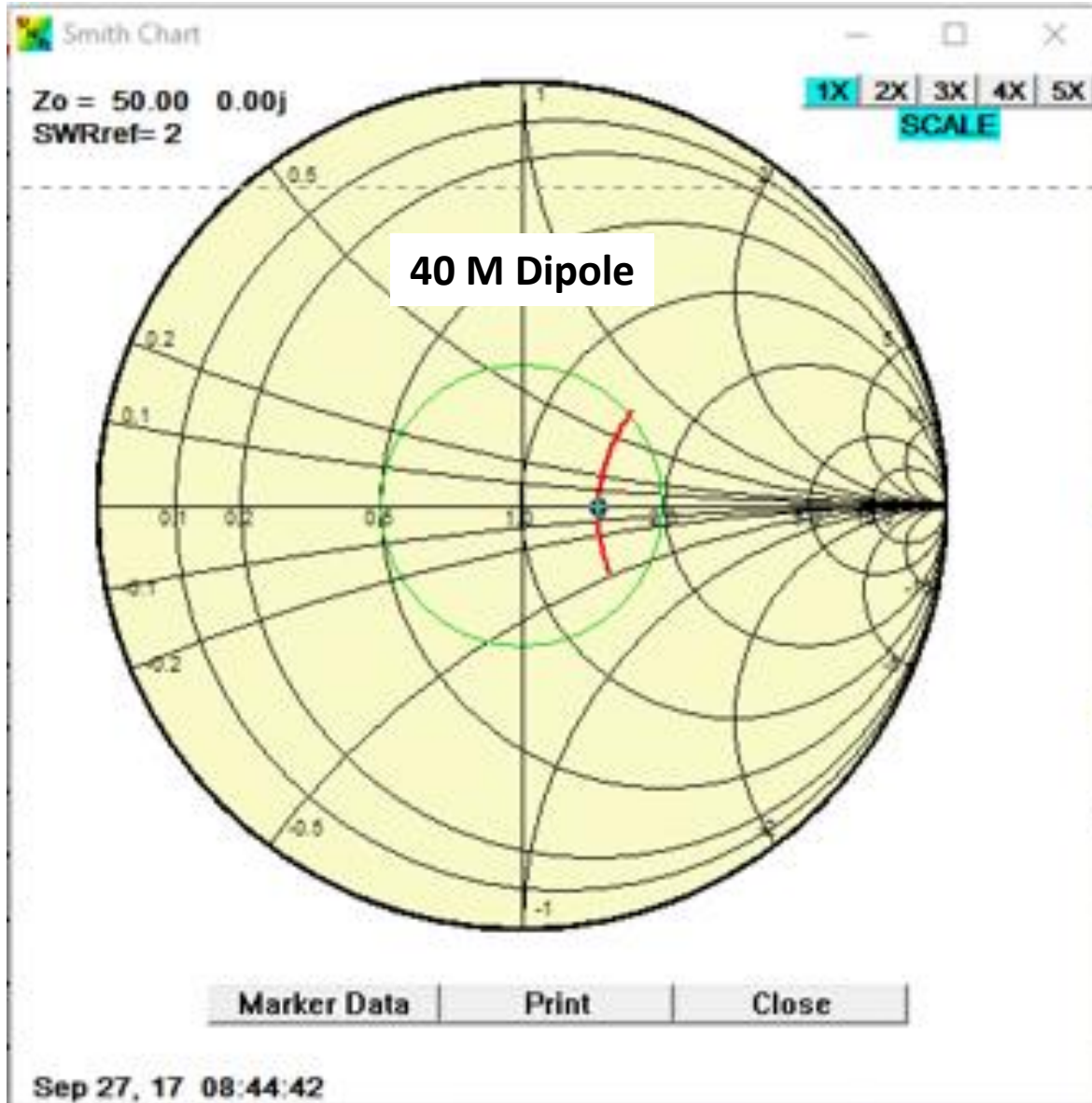


- The antenna is still resonant
- The antenna "System" is not resonant?

# Example 5: Antenna Tuning – cont'd

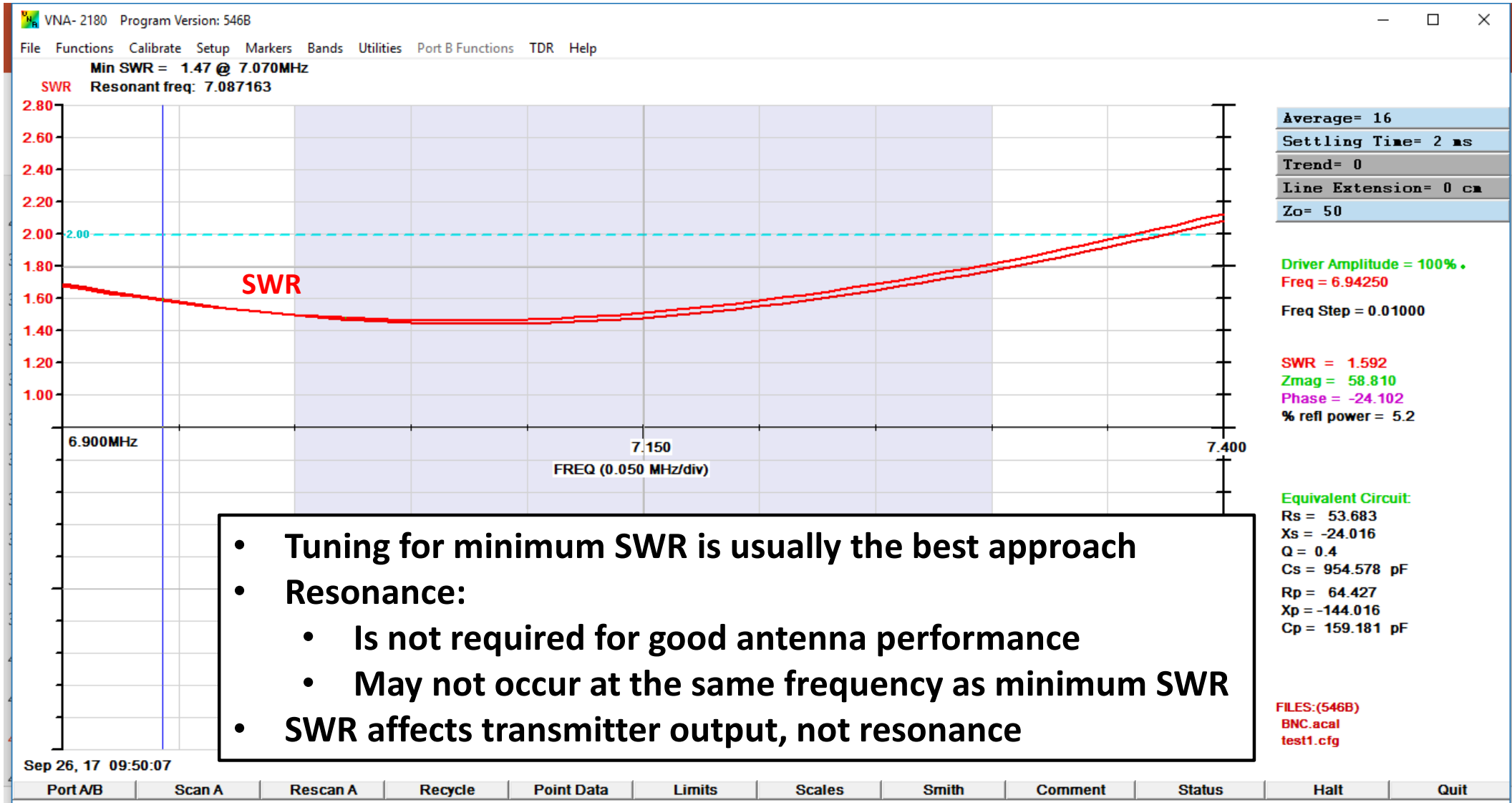

- Tuning for minimum SWR is usually the best approach
- Resonance:
  - Is not required for good antenna performance
  - May not occur at the same frequency as minimum SWR
- SWR affects transmitter output, not resonance

# SWR vs Transmission Line Loss

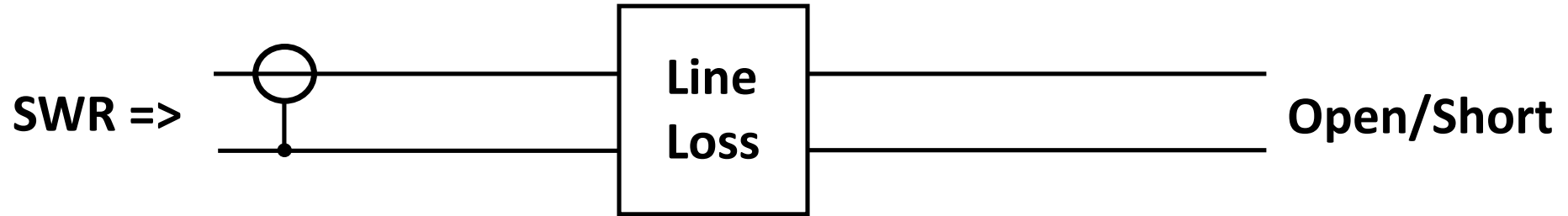

<u>Loss (dB)</u>	<u>Measured SWR</u>
0	Infinite
1	8.8
2	4.4 (75 ft RG-58A @ 28 MHz)
3	3.0
Infinite	1.0

**Transmission line loss reduces measured SWR**



# Summary

- Make sure you understand the impedance measurement you are getting from your antenna analyzer
- When  $Z_{\text{LOAD}} \neq Z_0$ , transmission lines can become impedance transformers
  - This behavior can either be helpful or harmful
- The Smith chart:
  - Is a good learning tool
  - Is not the easiest way to solve impedance problems
- Adding a short length of transmission line might help an antenna tuner achieve a match
  - Because it raises the impedance (it does not lower the SWR!)
- It is usually better to tune an antenna for best SWR rather than resonance
- Transmission line loss lowers the measured SWR